





PH 220



Lance Nelson


How does the resistance of D compare to that of A:

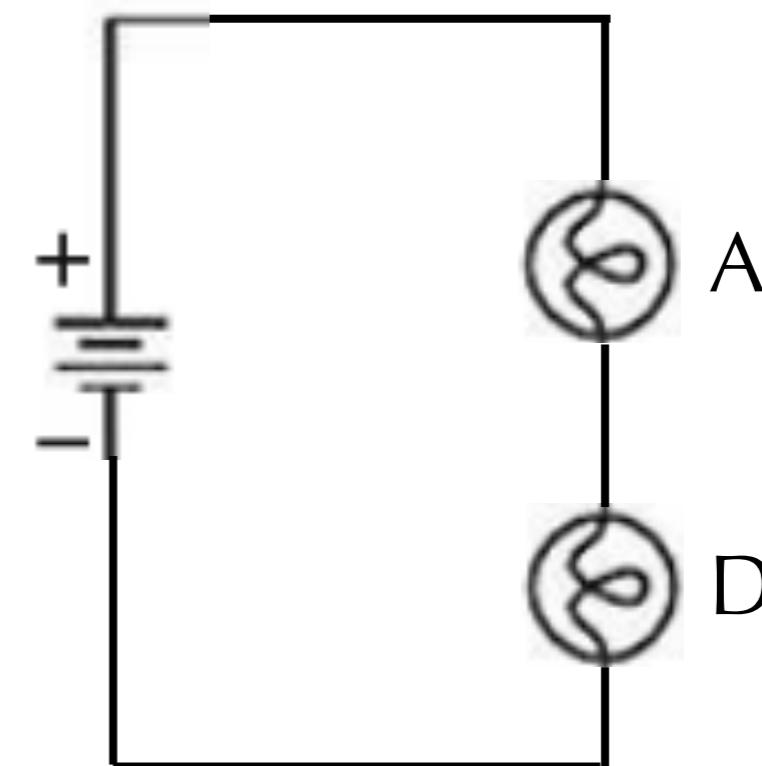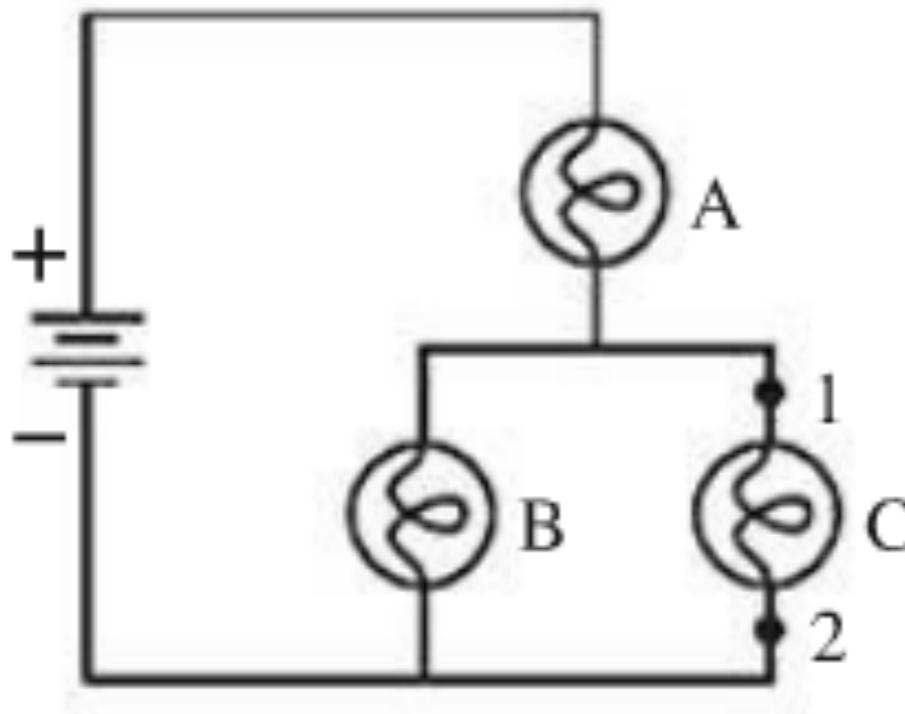- a) before the wire is placed between 1 and 2
- b) after the wire is placed between 1 and 2






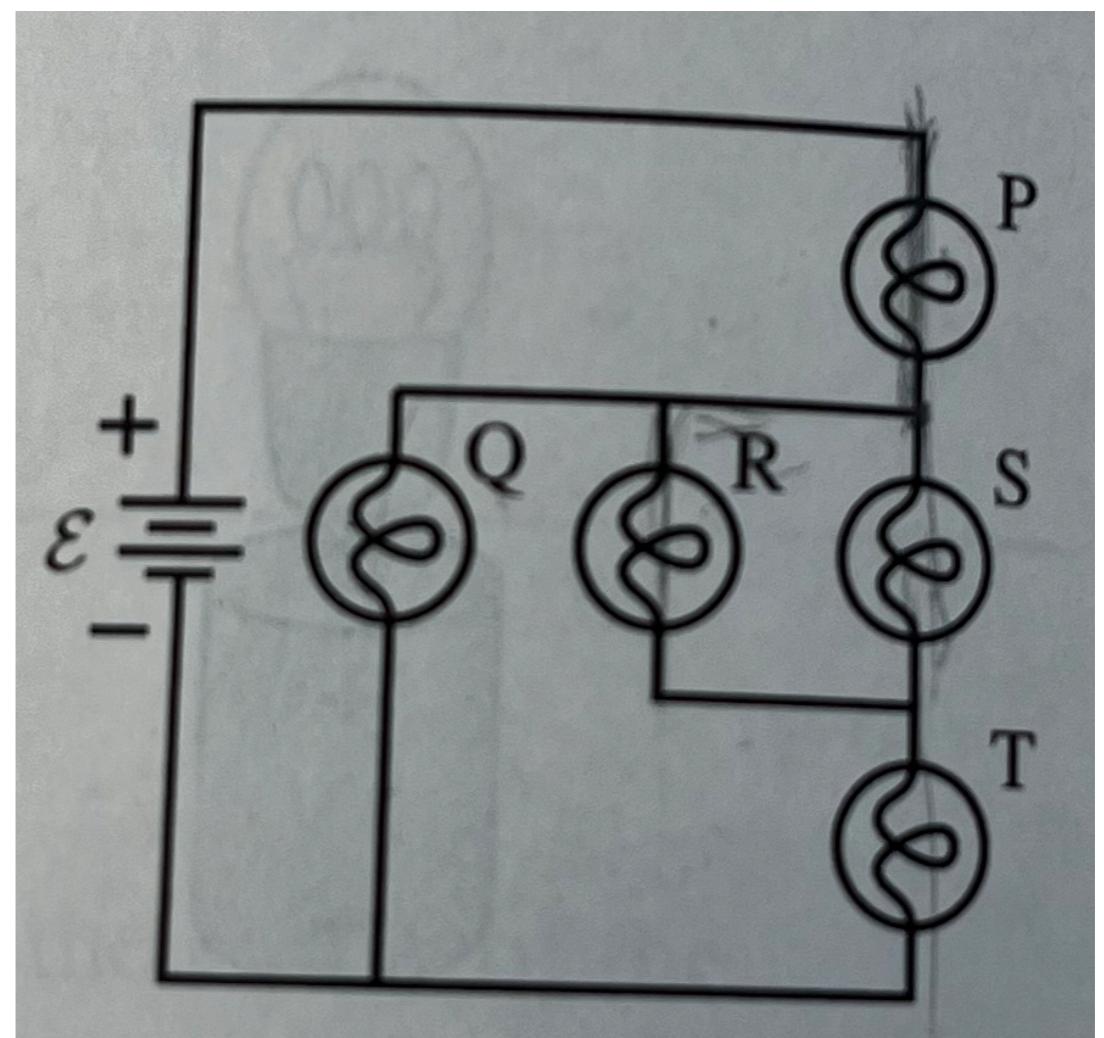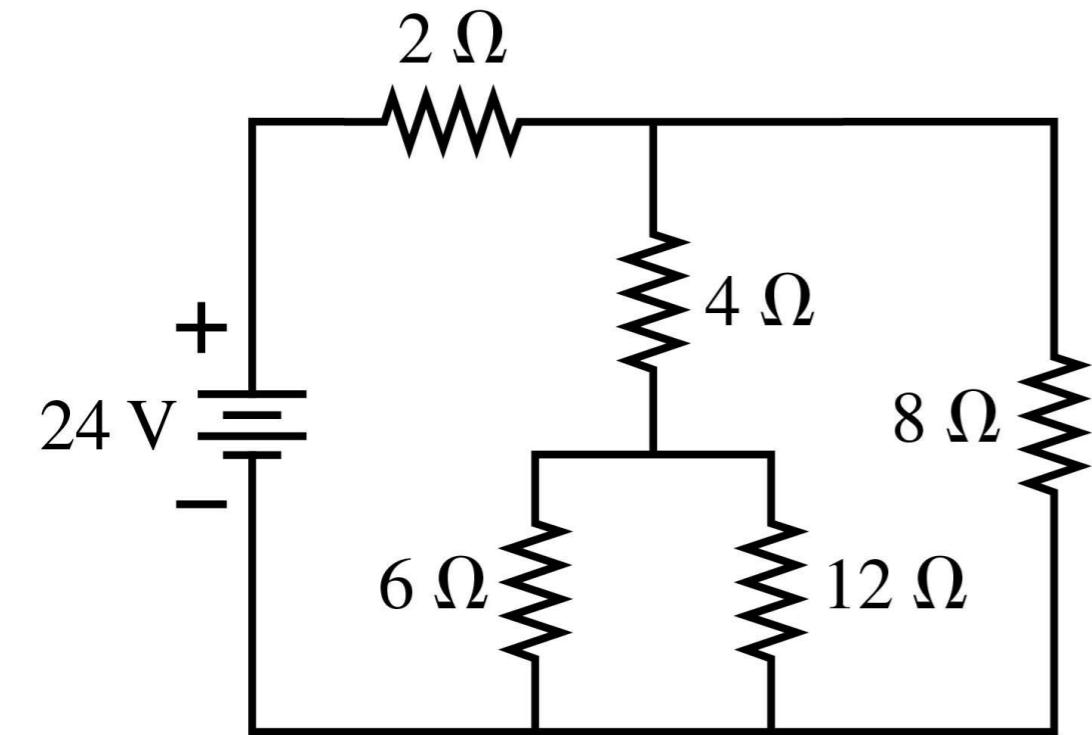Compare the current in the circuit before the short to after the short.




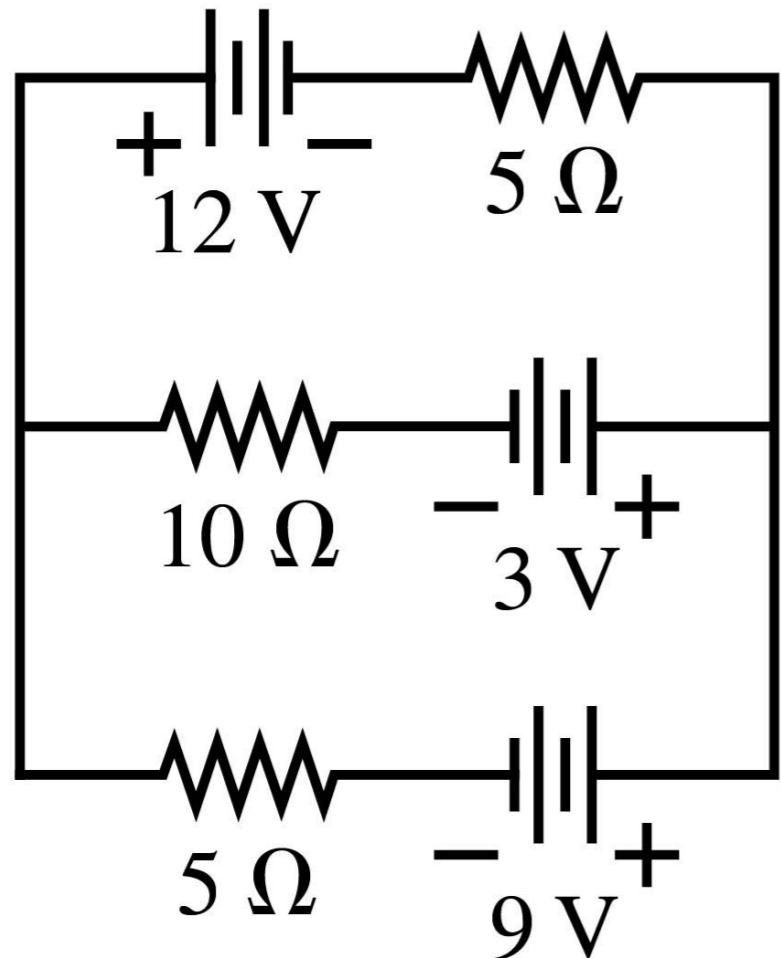

# Ammeters and Voltmeters

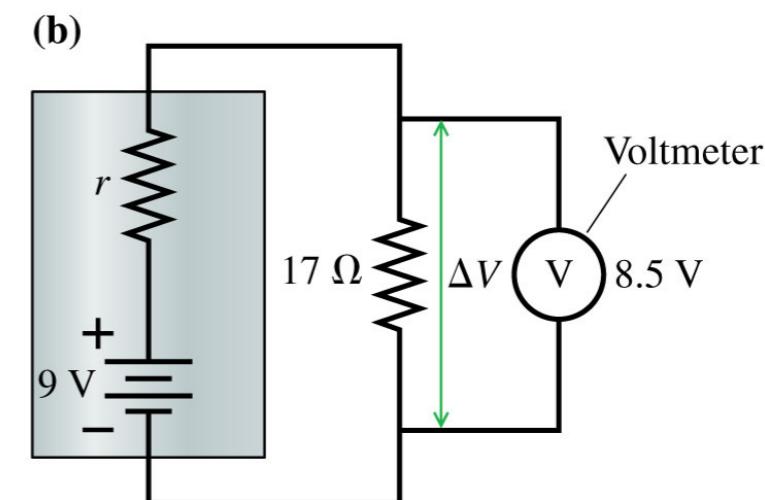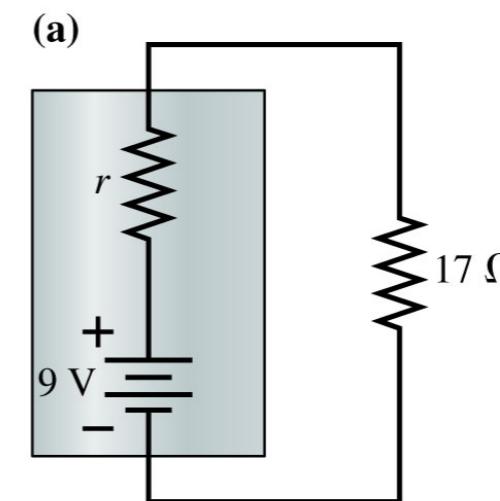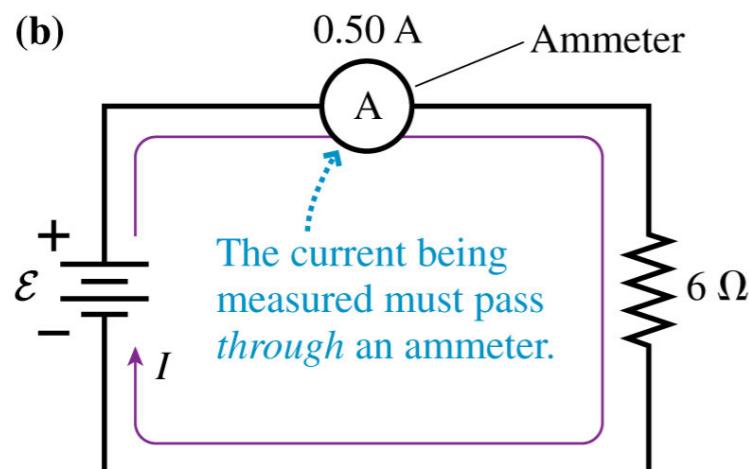


What does the voltmeter read?

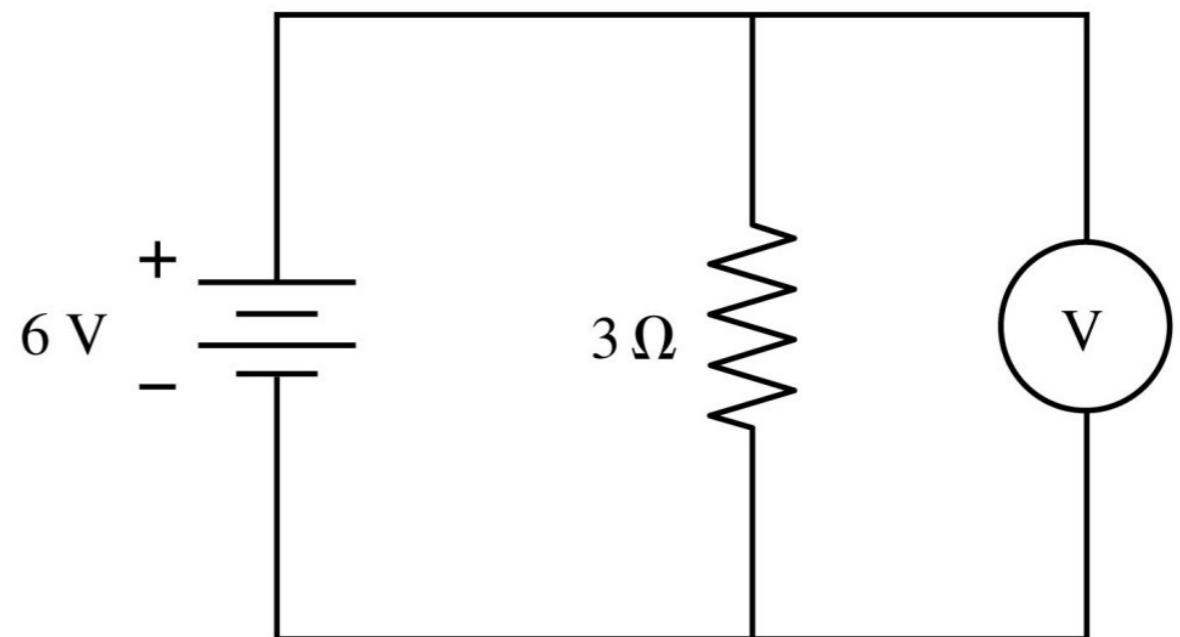


What does the voltmeter read?

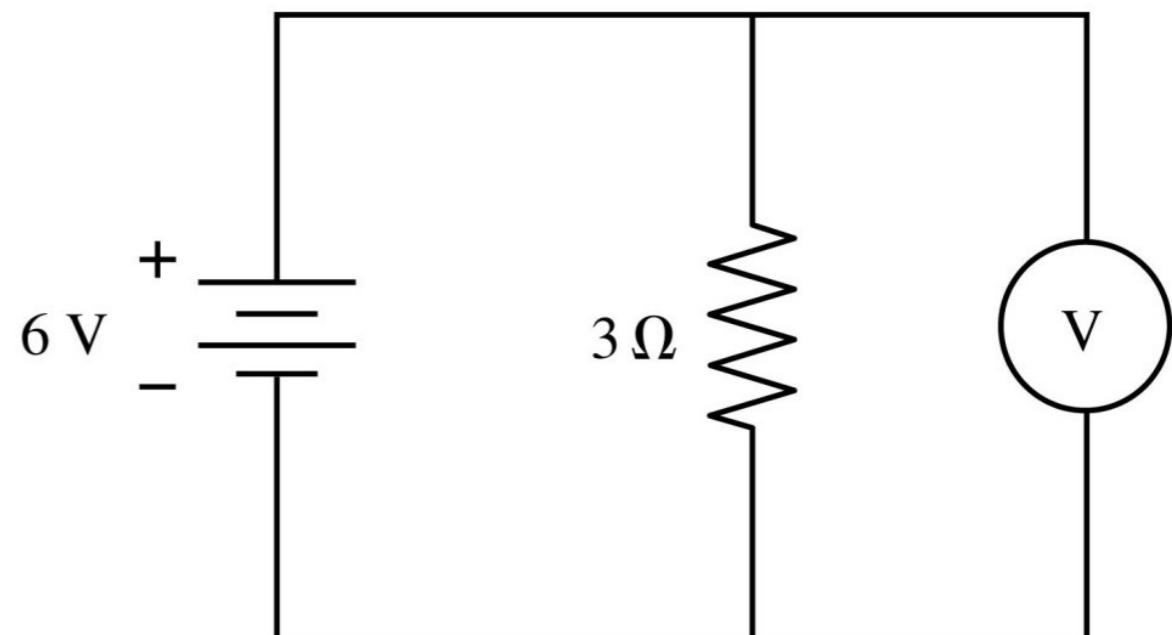- A. 6 V.
- B. 3 V.
- C. 2 V.
- D. Some other value.
- E. Nothing because this will fry the meter.




What does the ammeter read?

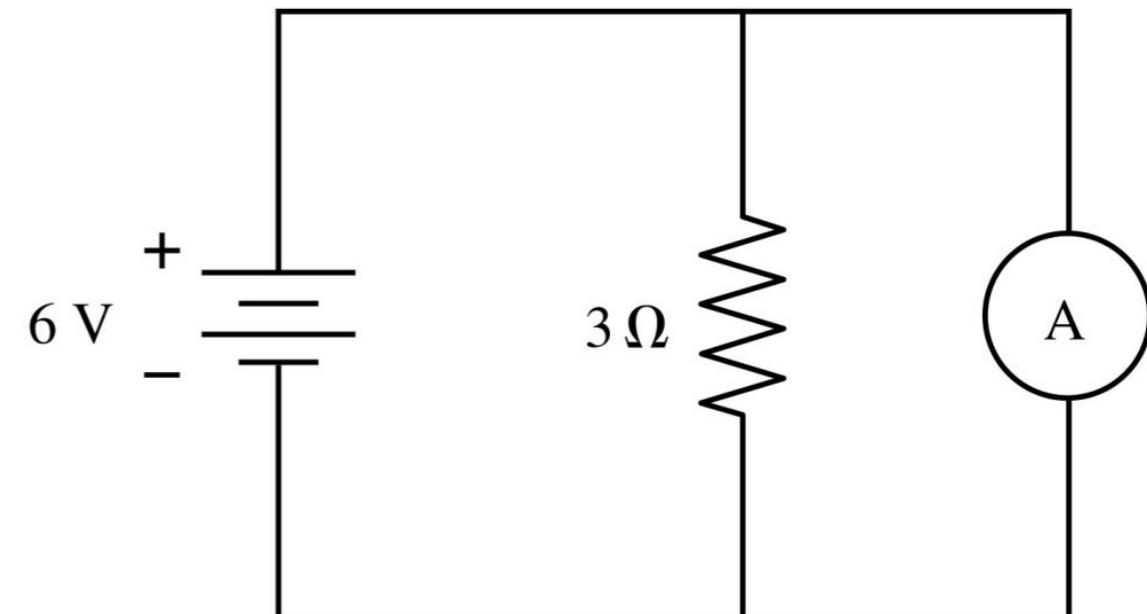- A. 6 V.
- B. 3 V.
- C. 2 V.
- D. Some other value.
- E. Nothing because this will fry the meter.




# Getting Grounded


"Ouch!"

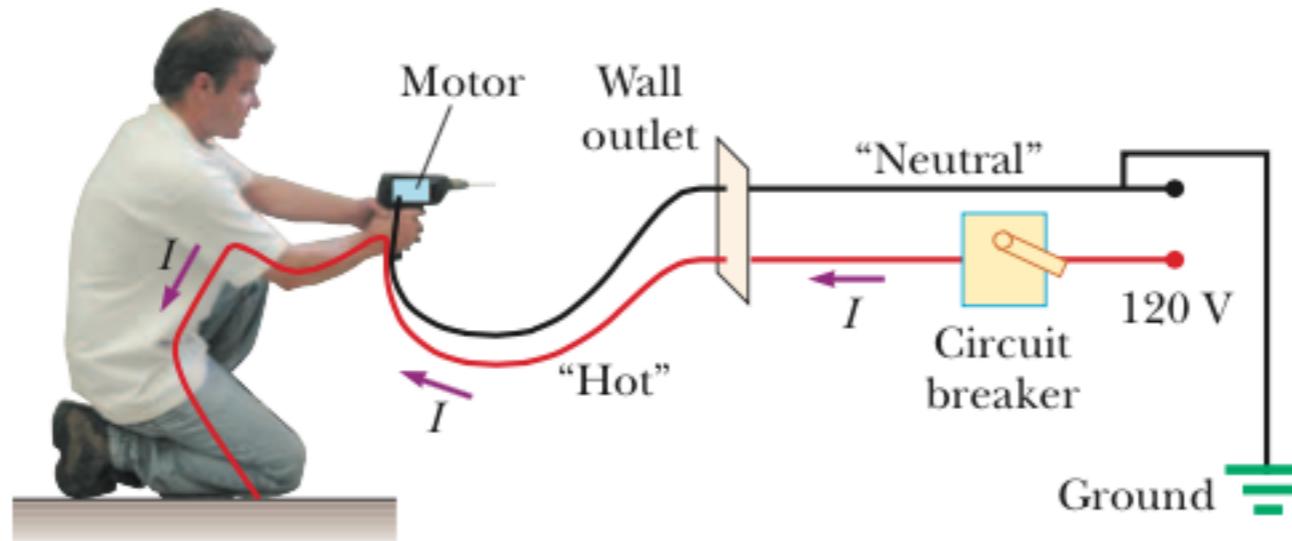

(a)

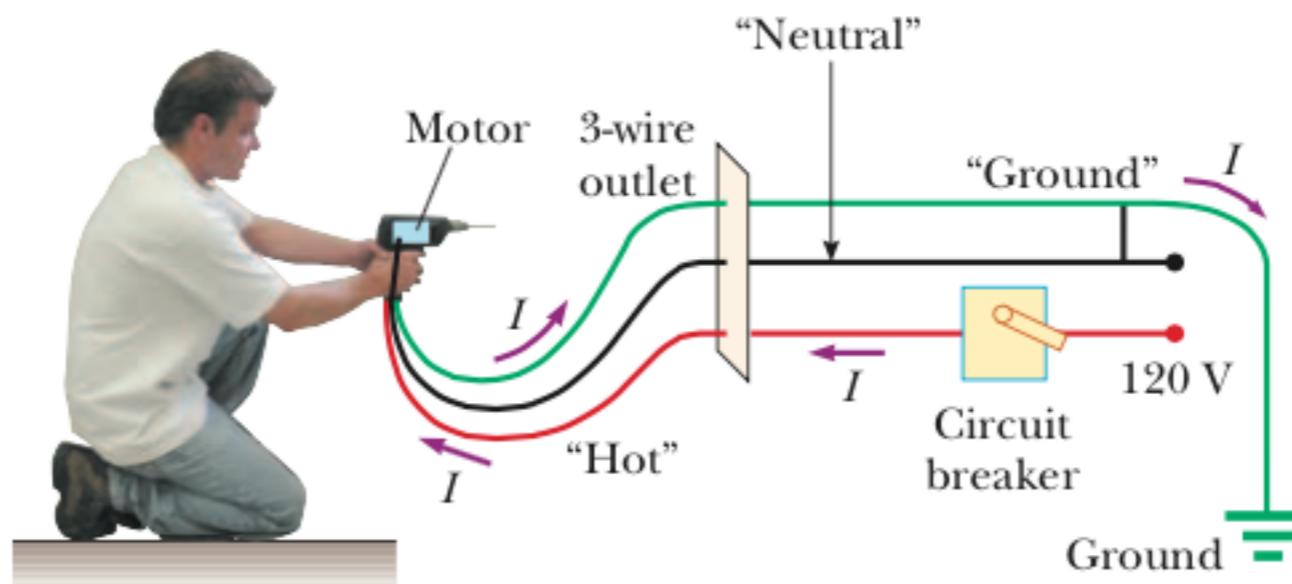


# Grounding a circuit

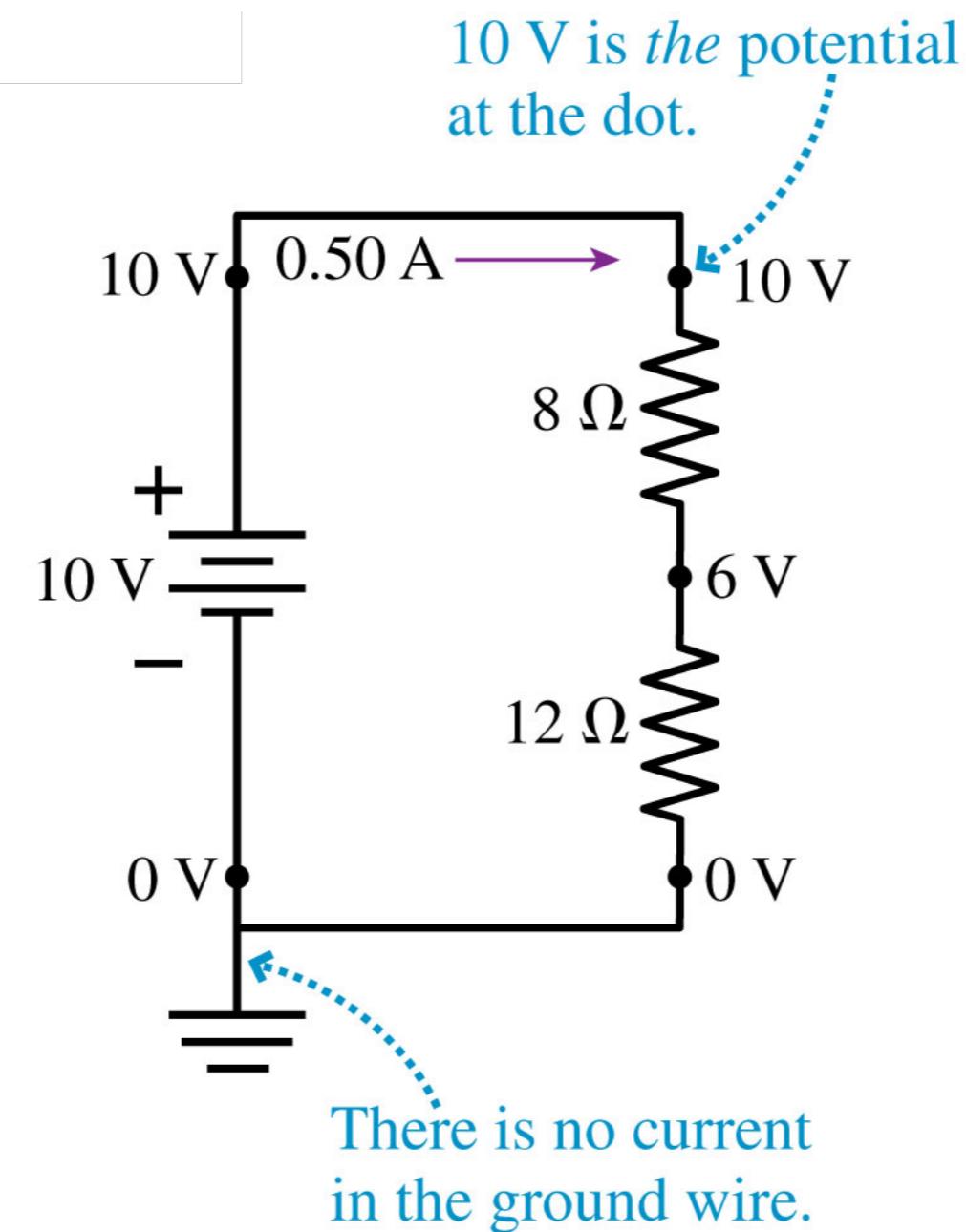

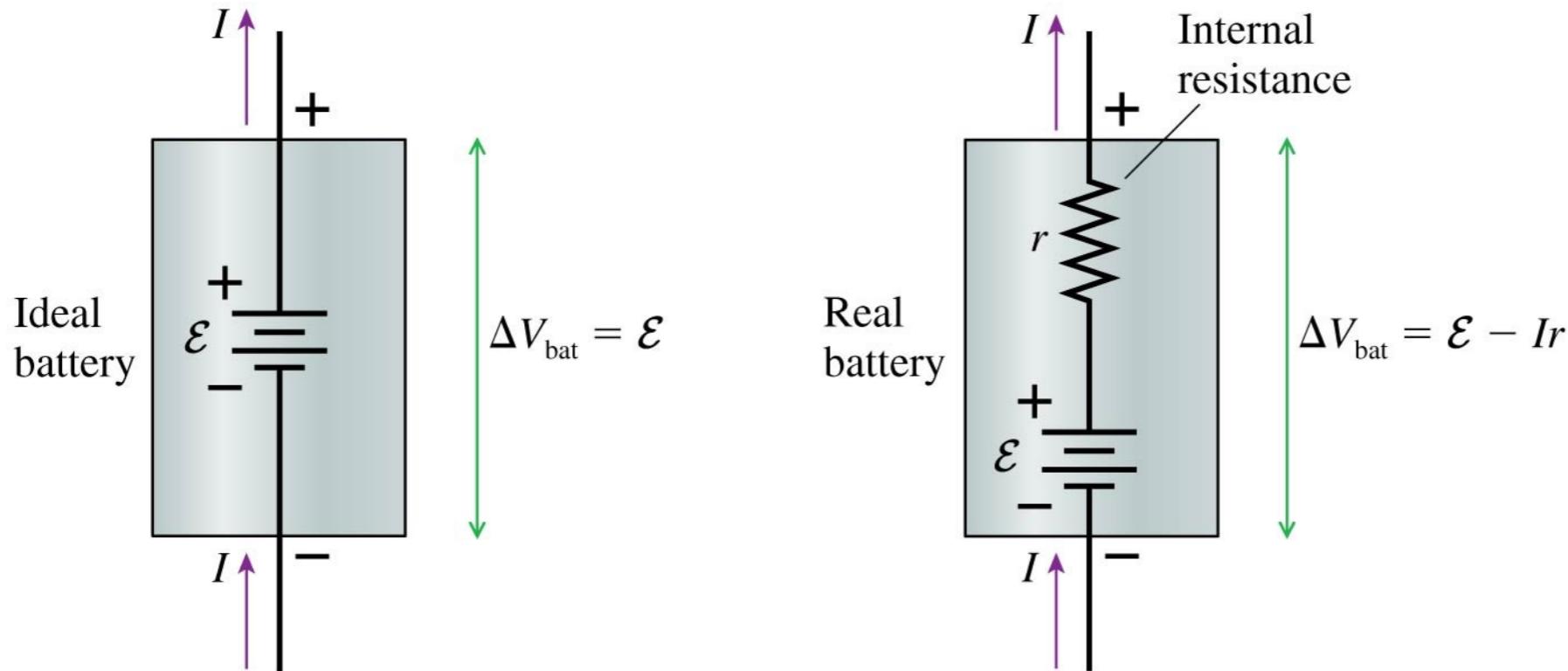
# Real Batteries


The batterie's internal resistance limits the max current.



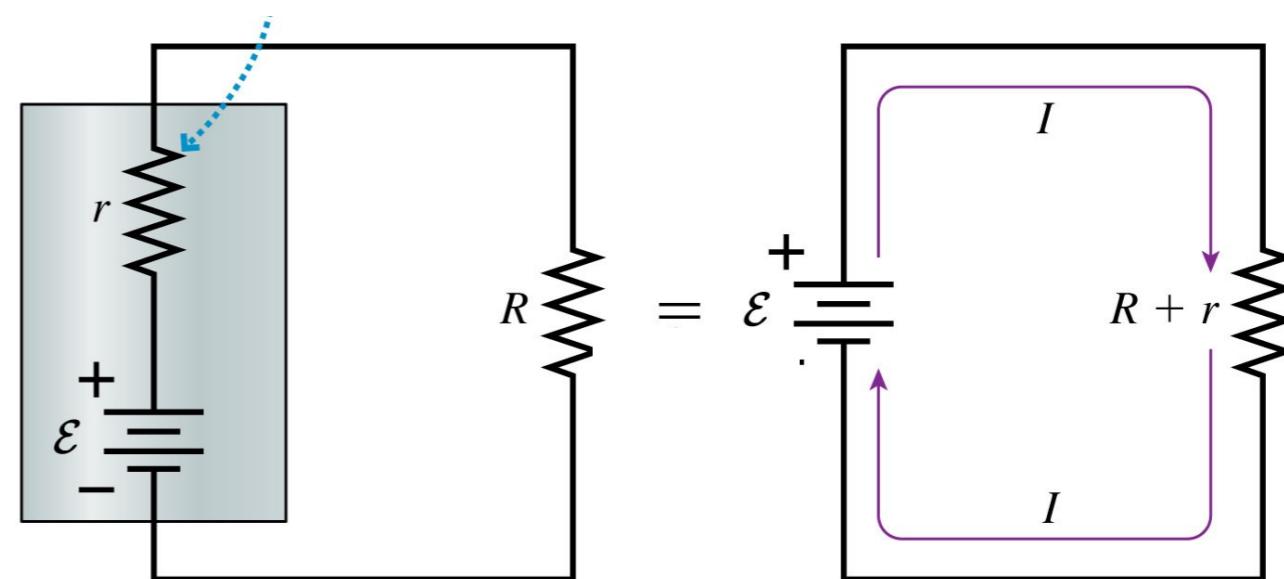
$$\Delta V_R = IR = \frac{\mathcal{E}}{R+r} R$$




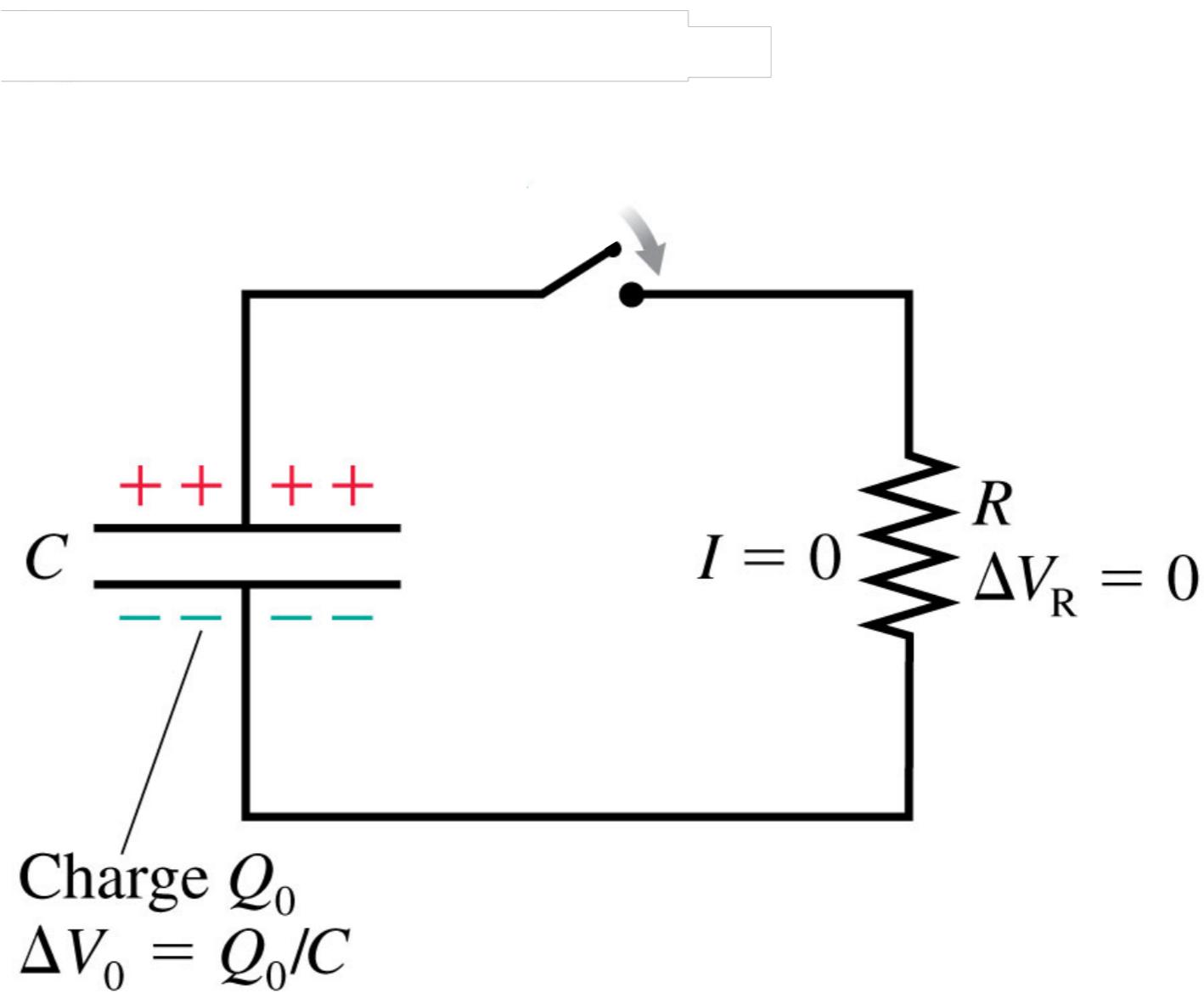Without looking in the book. Sketch the Q vs. time curve for the capacitor.



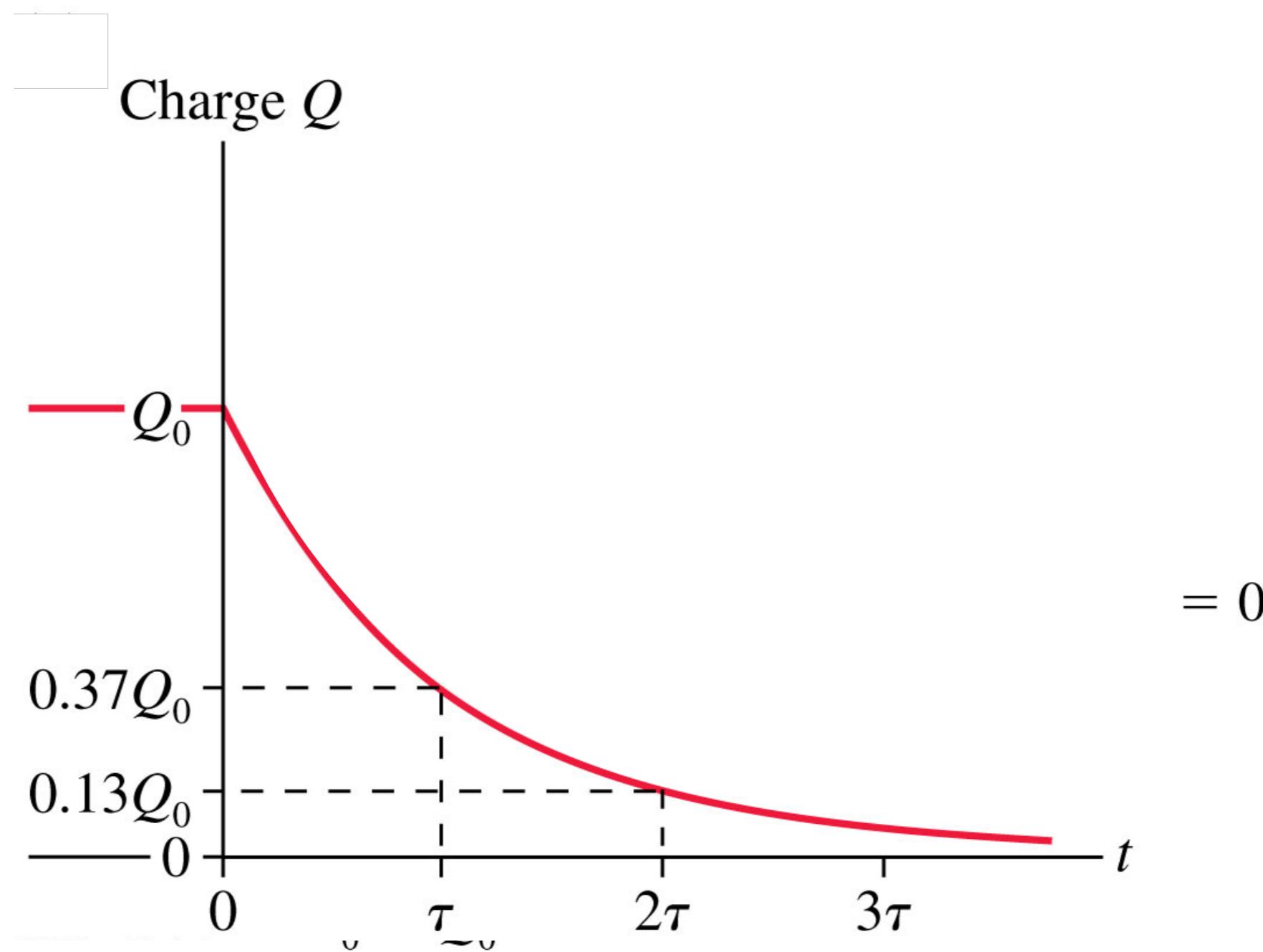
Without looking in the book. Sketch the  $Q$  vs. time curve for the capacitor.



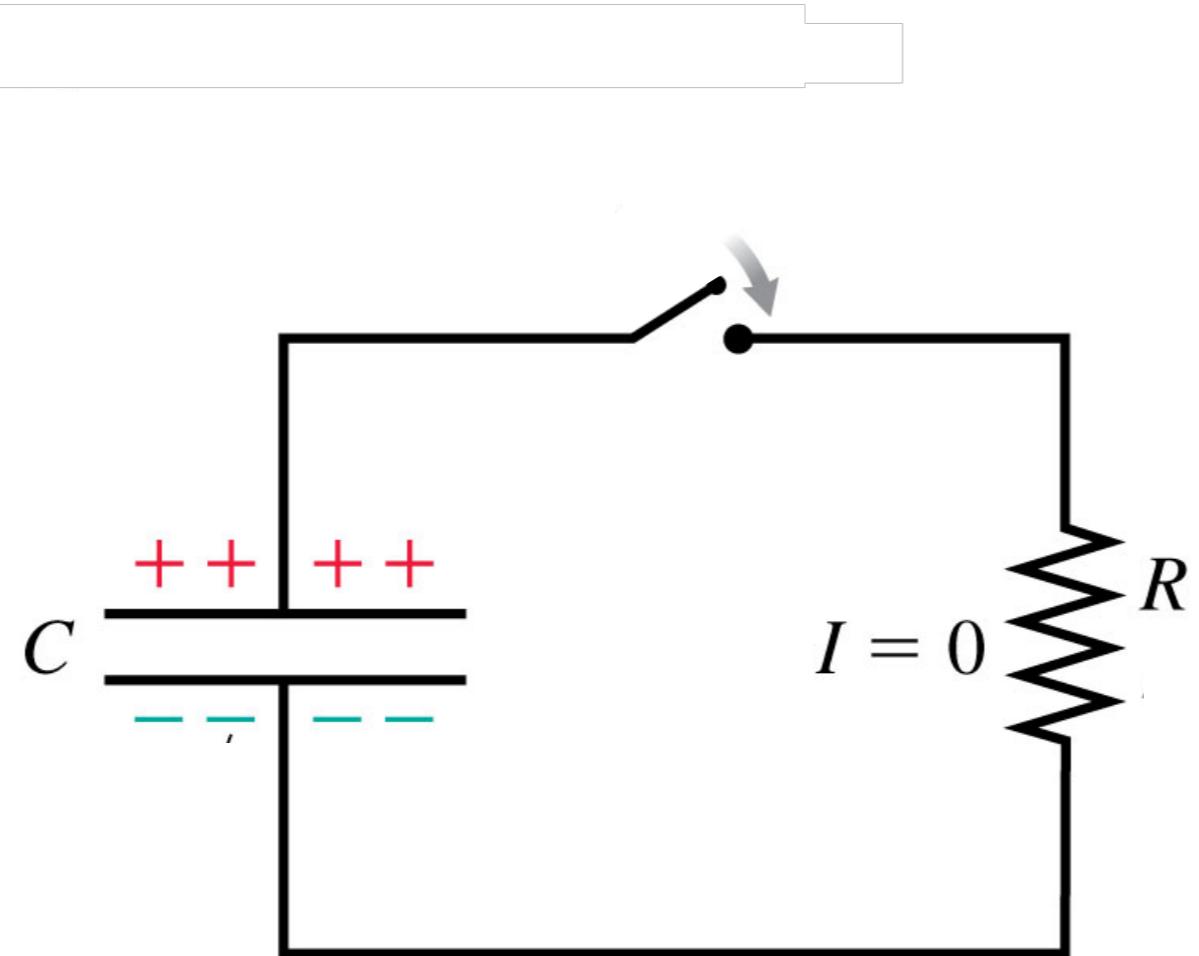
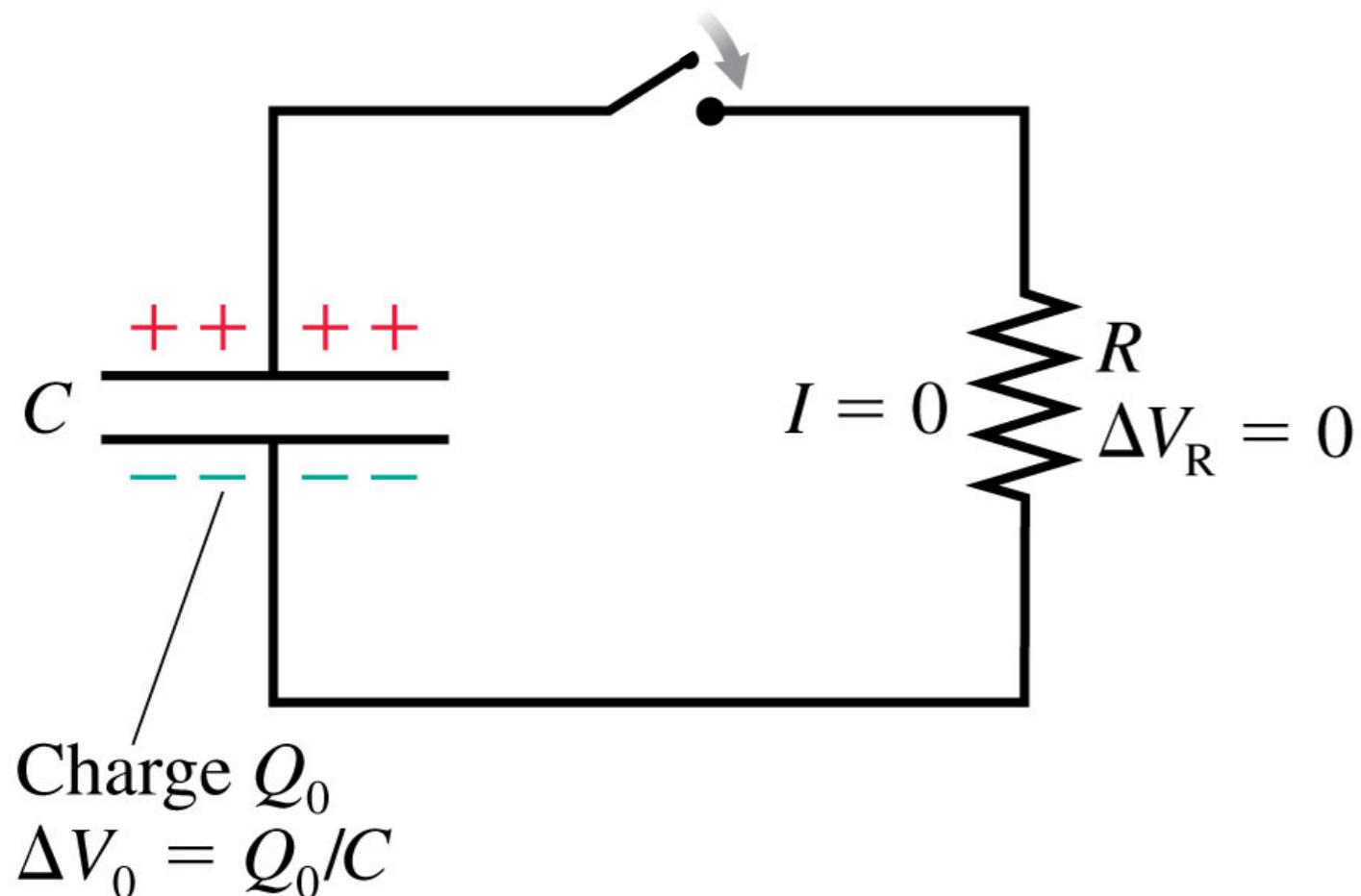
# The Math


Write down Kirchoff's  
loop rule for this circuit


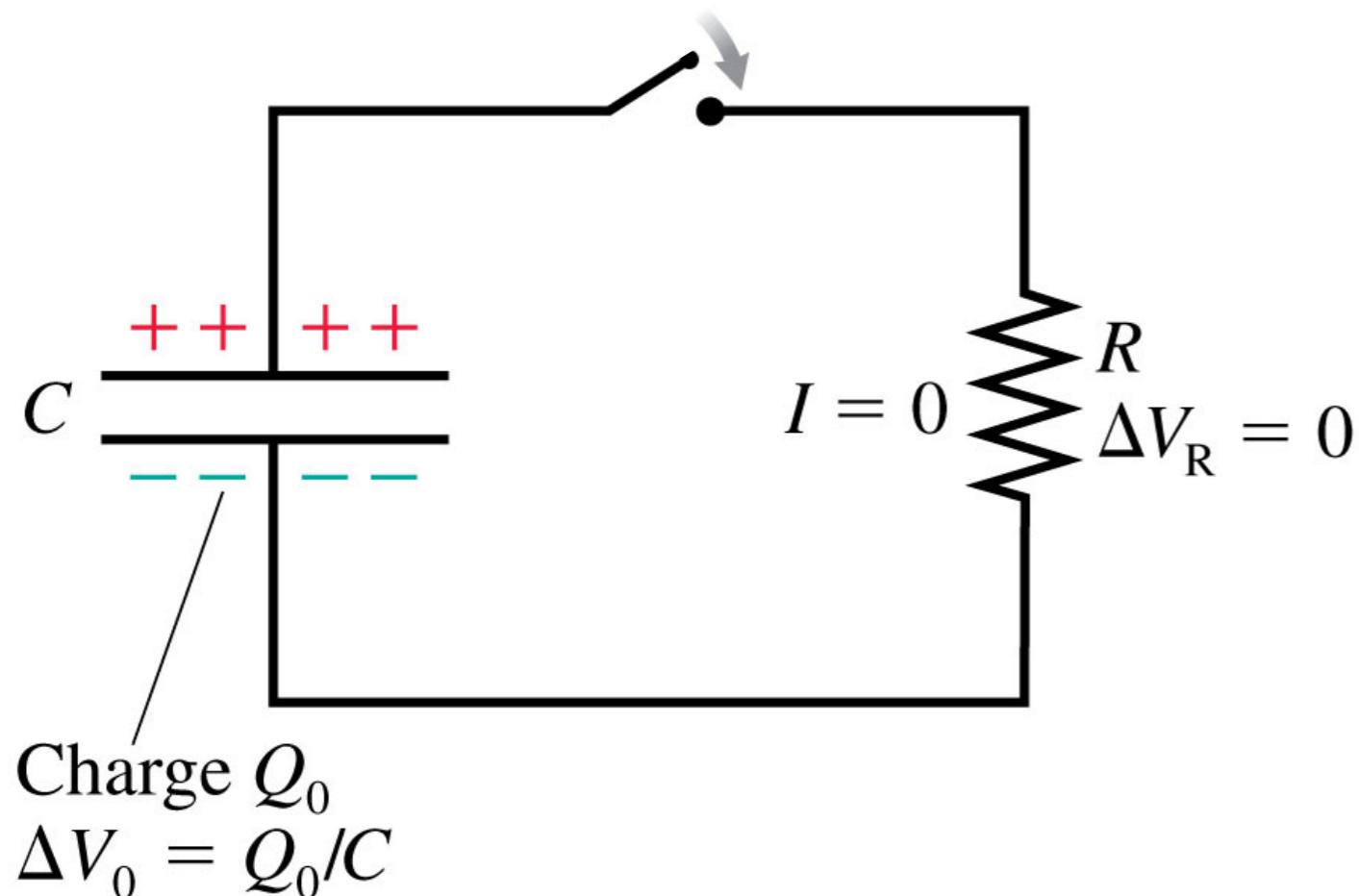
# The Math


Write down Kirchoff's loop rule for this circuit

$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$


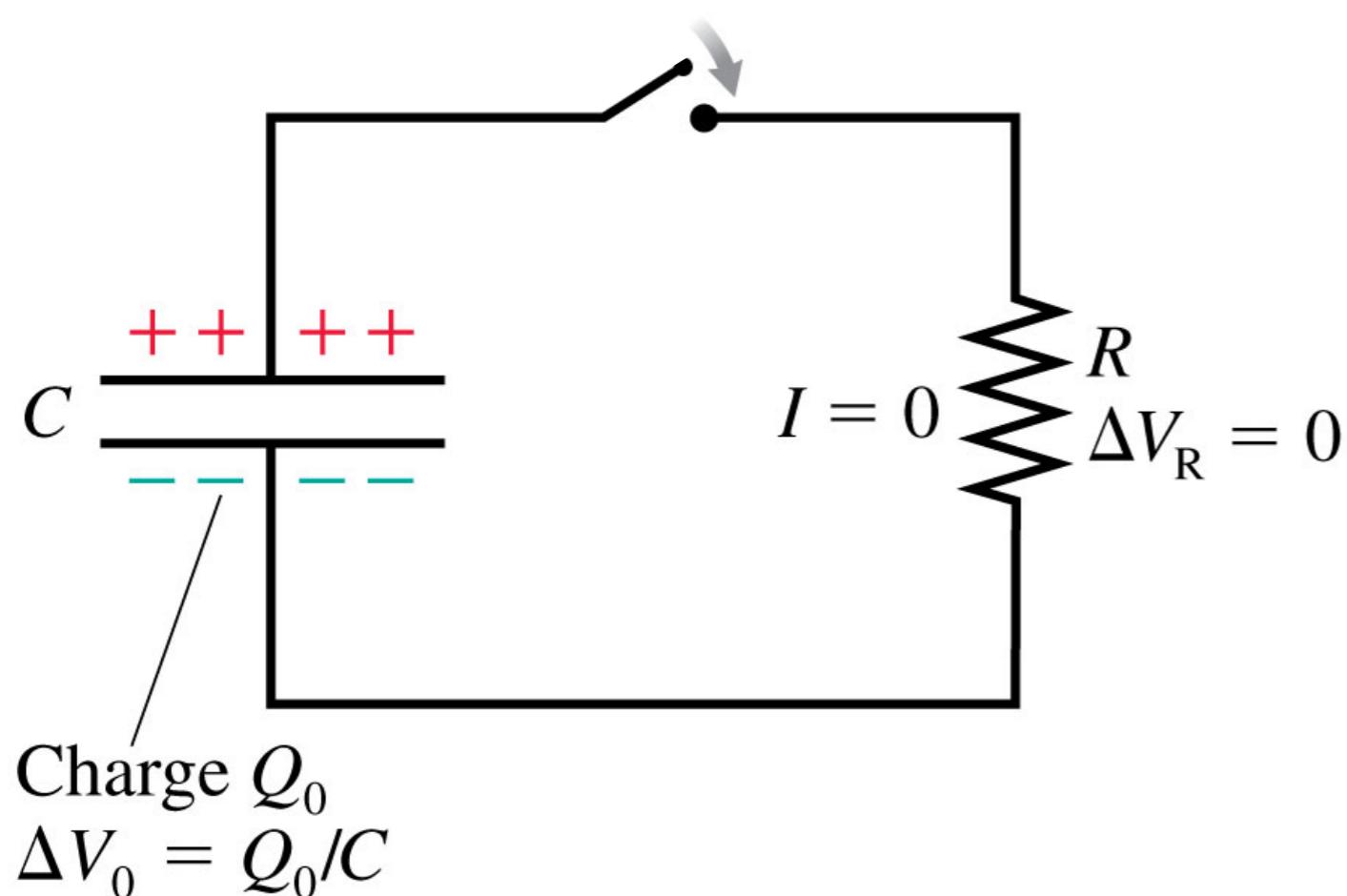
# The Math

Write down Kirchoff's loop rule for this circuit




$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$
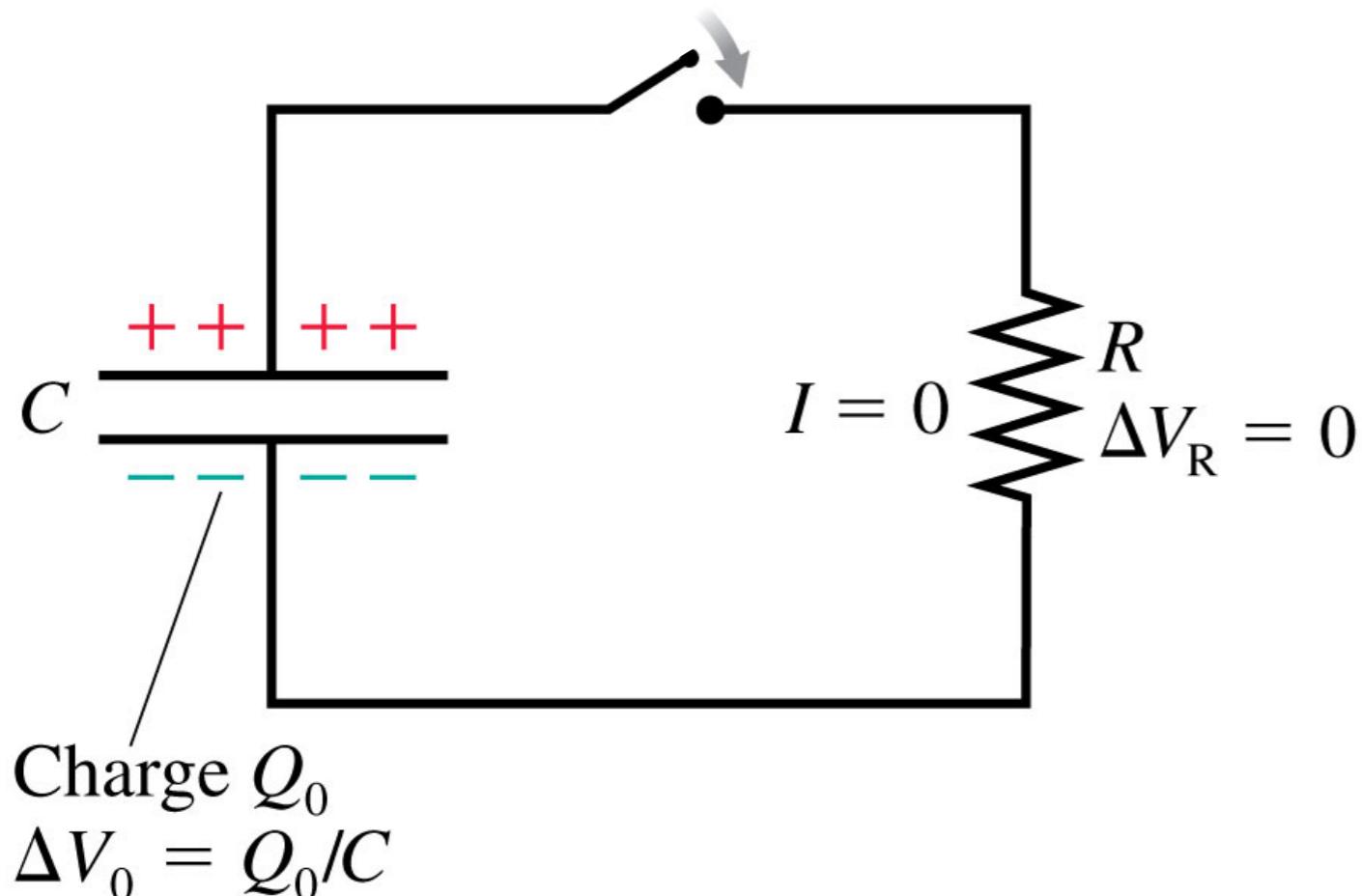
# The Math

Write down Kirchoff's loop rule for this circuit




$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$

$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$
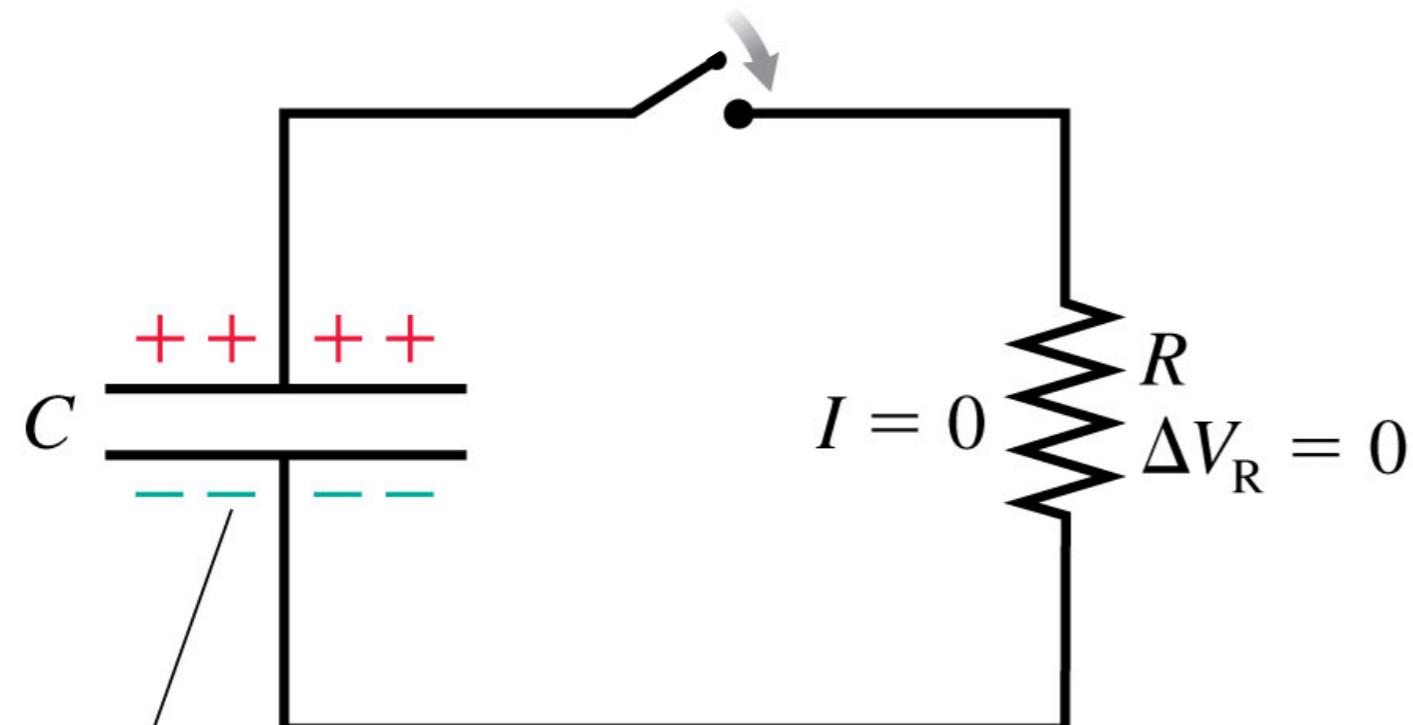
# The Math

Write down Kirchoff's loop rule for this circuit



Charge  $Q_0$   
 $\Delta V_0 = Q_0/C$

$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$


$$I = -\frac{dQ}{dt}$$

$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$

- Gather all the variables with  $Q$  in them to one side.
- Integrate both sides.
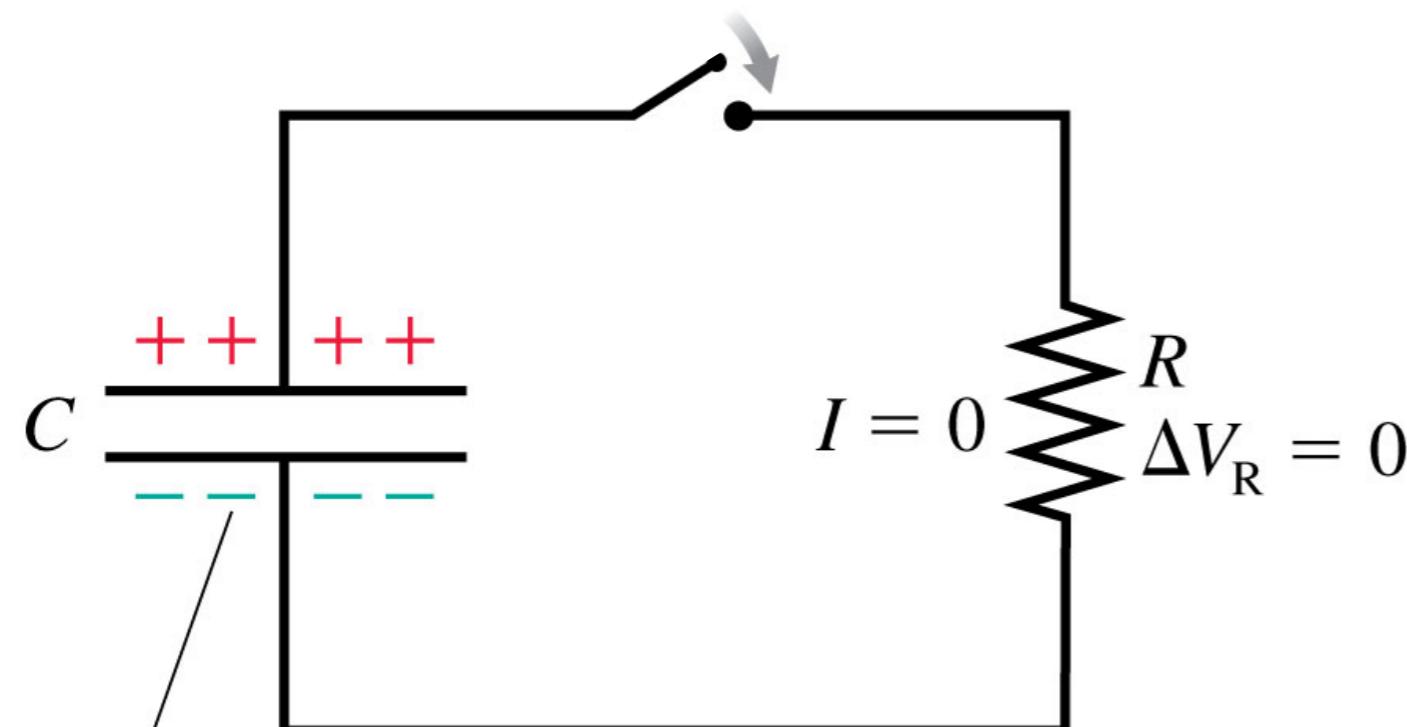
# The Math

Write down Kirchoff's loop rule for this circuit



Charge  $Q_0$   
 $\Delta V_0 = Q_0/C$

$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$


$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$

- Gather all the variables with  $Q$  in them to one side.
- Integrate both sides.

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$
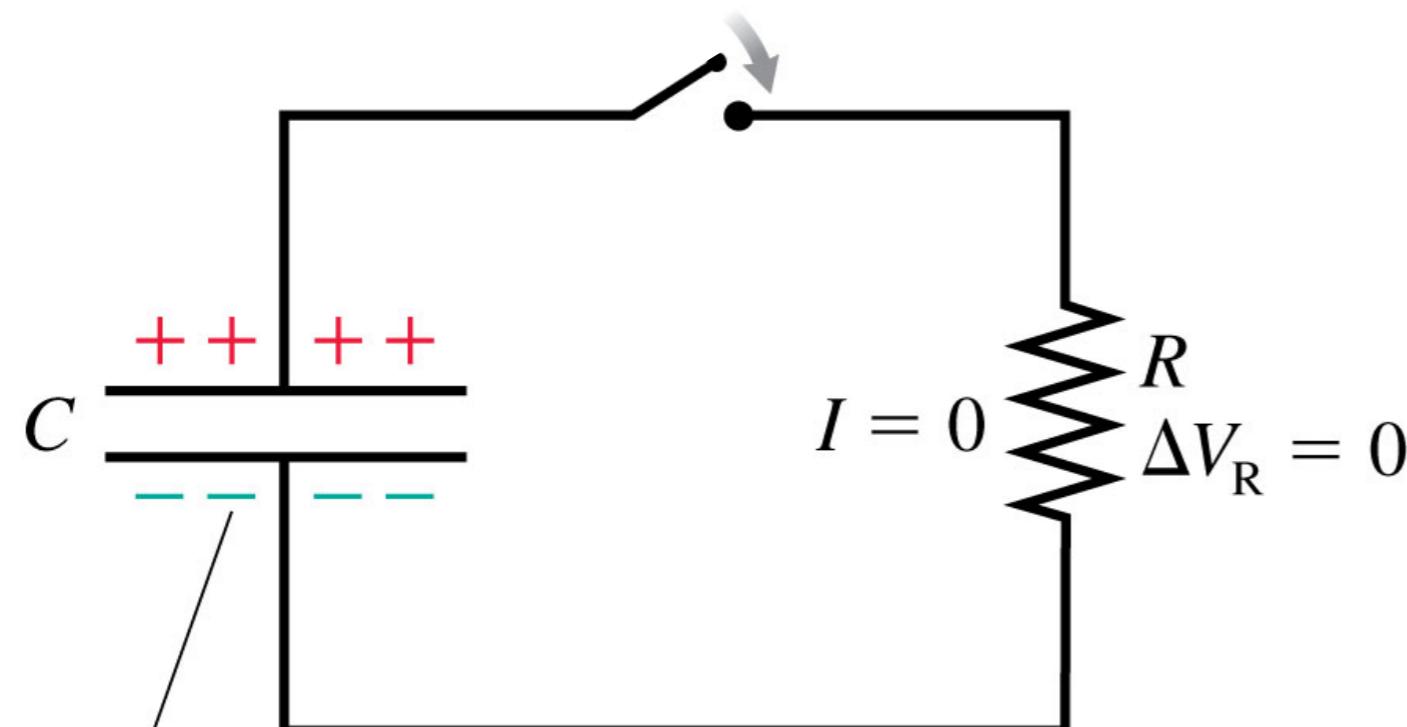
# The Math

Write down Kirchoff's loop rule for this circuit



Charge  $Q_0$   
 $\Delta V_0 = Q_0/C$

$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$

$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$

- Gather all the variables with  $Q$  in them to one side.
- Integrate both sides.

$$Q = Q_0 e^{-t/\tau}$$


$$\tau = RC$$

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$
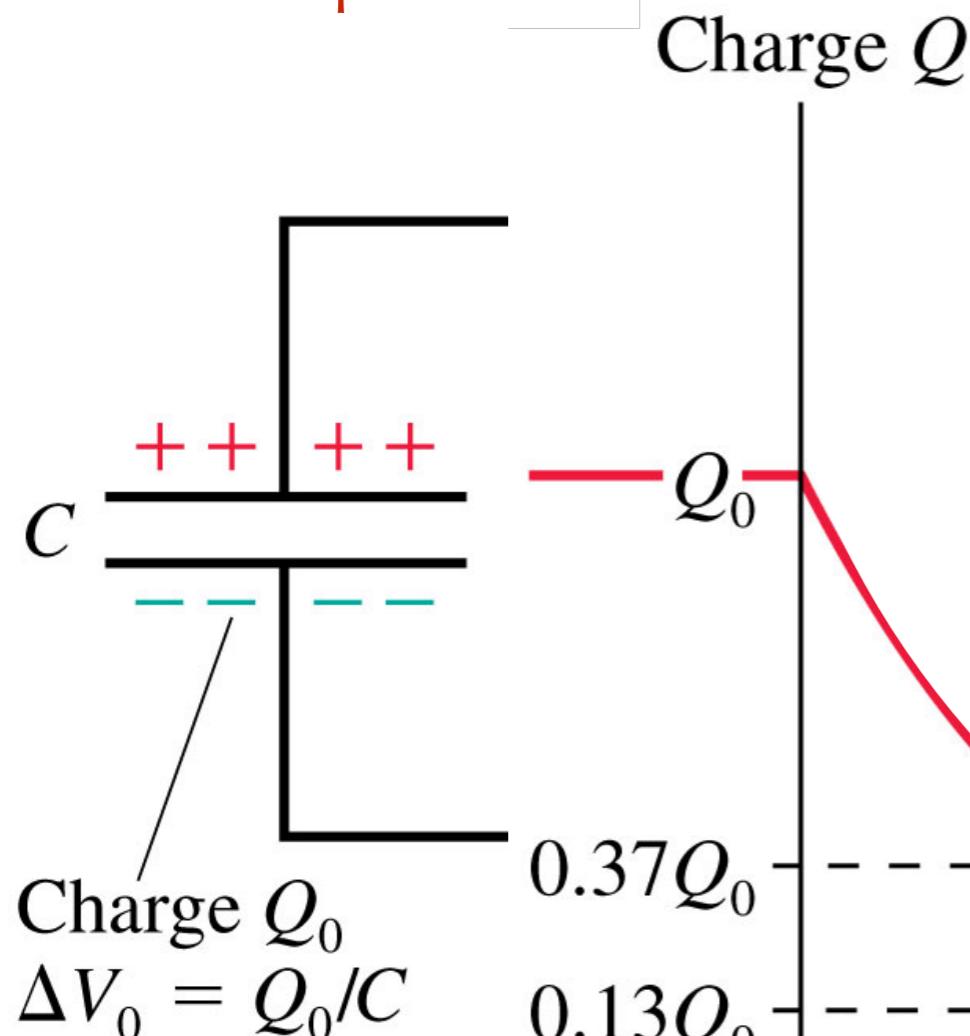
# The Math

Write down Kirchoff's  
loop rule for t

$$\Delta V_+ + \Delta V_- = \frac{Q}{C} - IR = 0$$



$$\Delta V_0 = Q_0/C$$

$$\frac{dQ}{dt}$$



$$\frac{d}{dt} = 0$$

the  
with  $Q$  in  
one side.  
on both sides.

$$\int_{Q_0}^{\infty} \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$


Which capacitor discharges more quickly after the switch is closed?

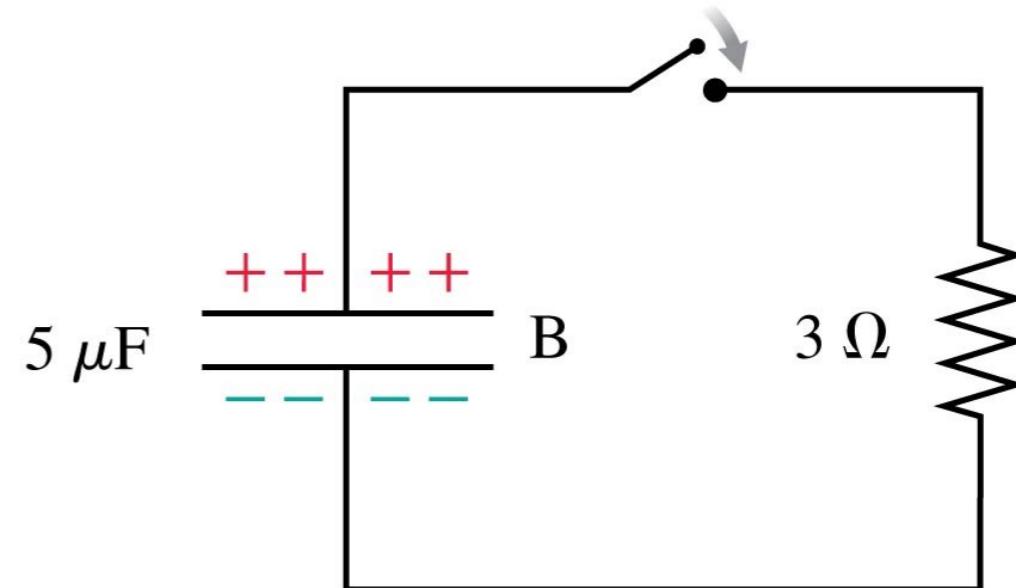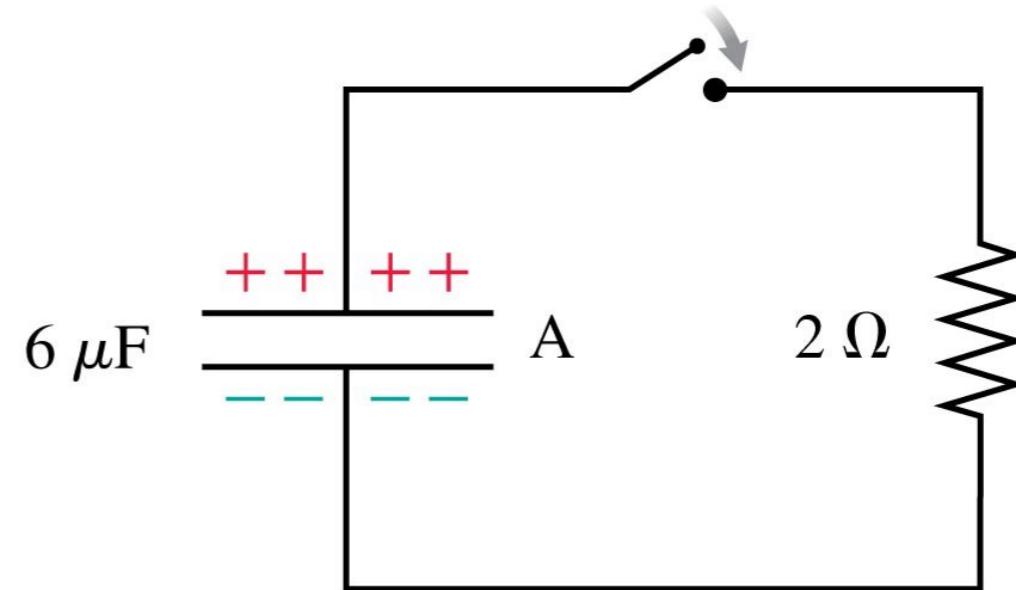- A. Capacitor A.
- B. Capacitor B.
- C. They discharge at the same rate.
- D. Can't say without knowing the initial amount of charge.




What is the time constant for this RC circuit

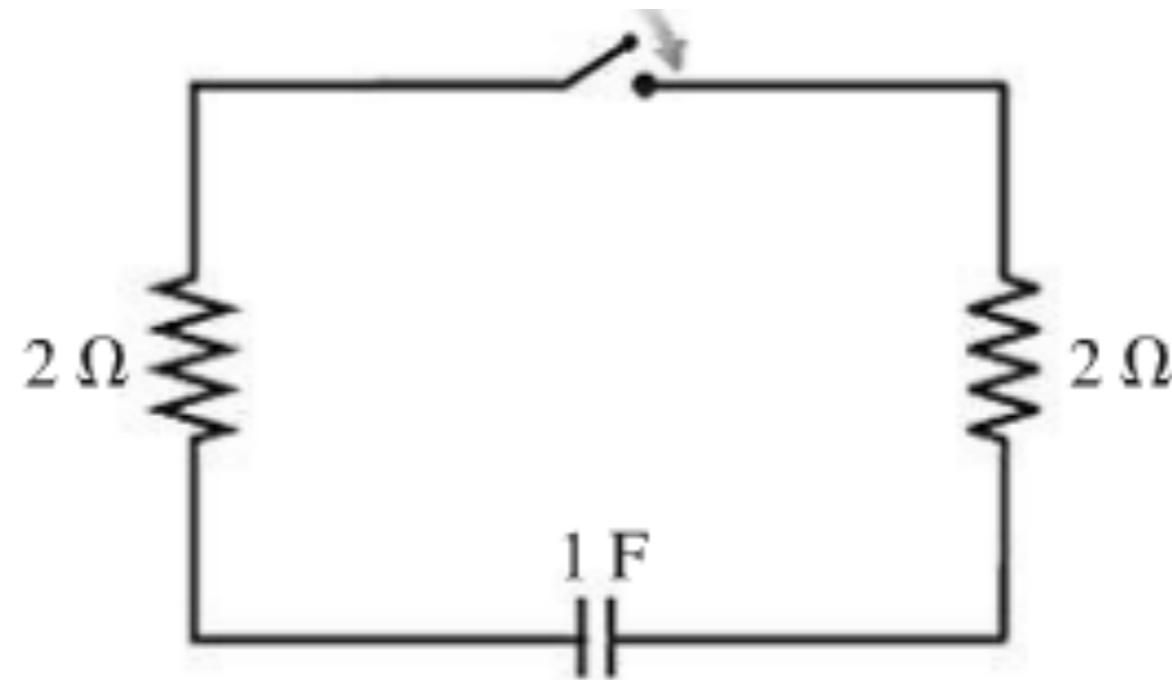- a) 5 s
- b) 4 s
- c) 3 s
- d) 2 s
- e) 1 s



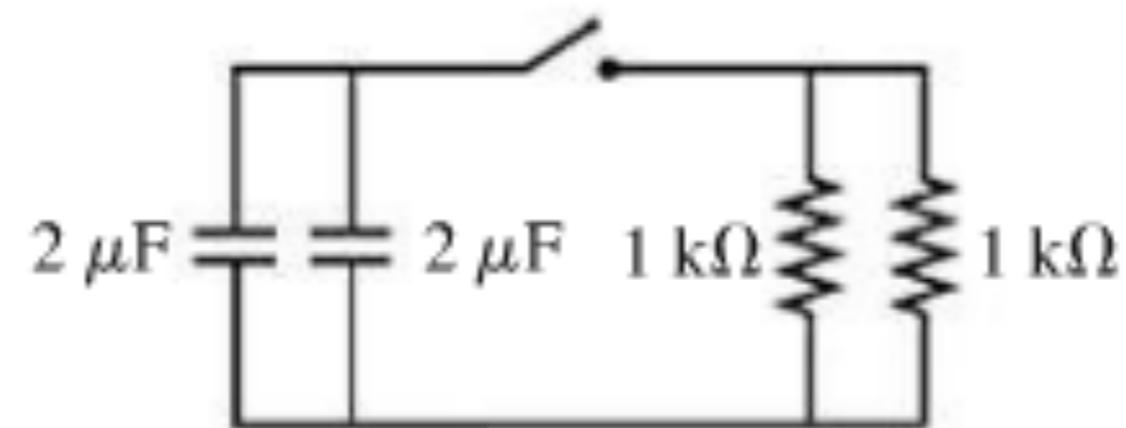What is the time constant for this RC circuit



$$Q = Q_0 e^{-t/\tau}$$

If the charge on the capacitor decays exponentially, how does the voltage on the capacitor vary with time?

$$Q = Q_0 e^{-t/\tau}$$

If the charge on the capacitor decays exponentially, how does the voltage on the capacitor vary with time?

$$\Delta V_C = \Delta V_0 e^{-t/\tau}$$

$$Q = Q_0 e^{-t/\tau}$$

If the charge on the capacitor decays exponentially, how does the voltage on the capacitor vary with time?

$$\Delta V_C = \Delta V_0 e^{-t/\tau}$$

What about the current through the resistor?

You'll need to do some math!

$$Q = Q_0 e^{-t/\tau}$$

If the charge on the capacitor decays exponentially, how does the voltage on the capacitor vary with time?

$$\Delta V_C = \Delta V_0 e^{-t/\tau}$$


What about the current through the resistor?

You'll need to do some math!

$$I = -\frac{dQ}{dt} = \frac{Q_0}{\tau} e^{-t/\tau} = \frac{Q_0}{RC} e^{-t/\tau} = \frac{\Delta V_0}{R} e^{-t/\tau} = I_0 e^{-t/\tau}$$


The capacitor is initially uncharged.  
Immediately after the switch closes,  
the capacitor voltage is

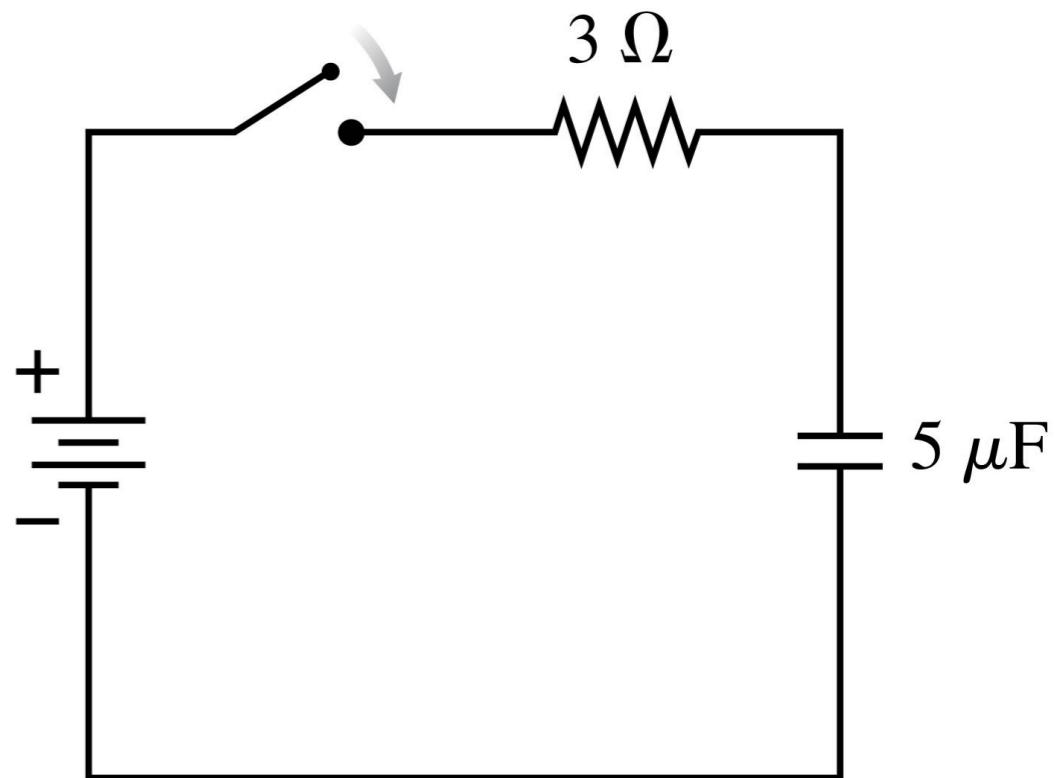- A. 0 V.
- B. Somewhere between 0 V and 6 V.
- C. 6 V.
- D. Undefined.





Without looking in your book, draw the Q vs. t curve for the capacitor.

Switch closes at  $t = 0$  s.

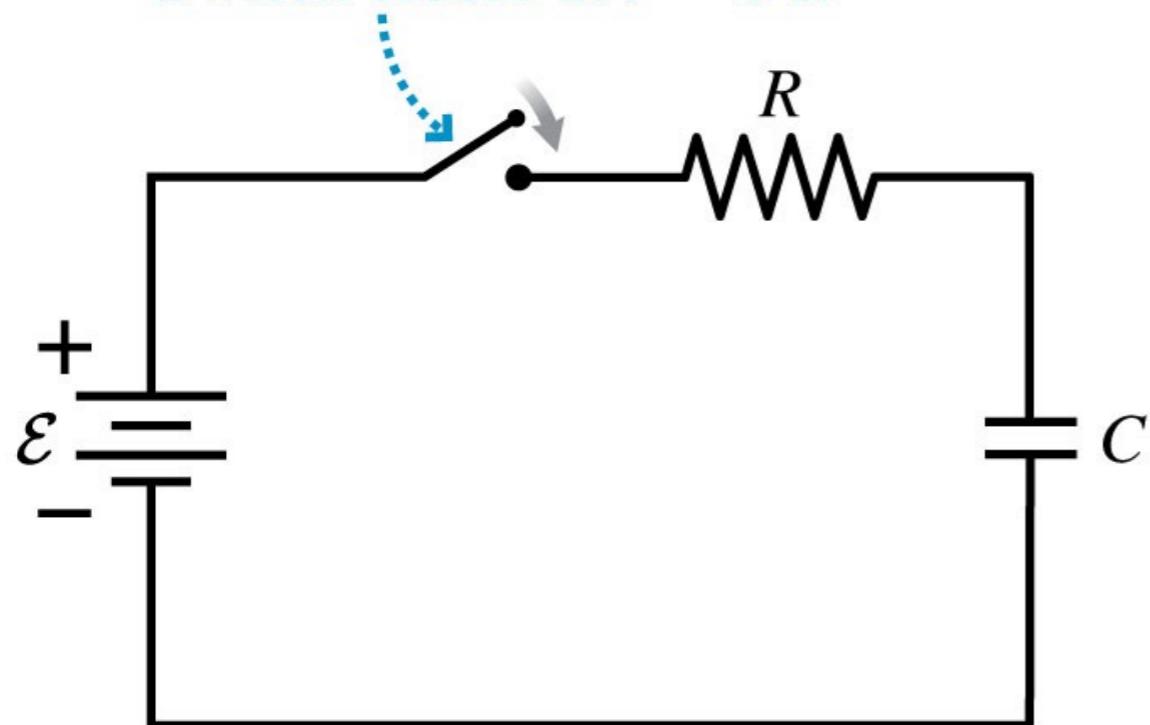

Without looking in your book, draw the  $Q$  vs.  $t$  curve for the capacitor.


Switch closes at  $t = 0$  s.

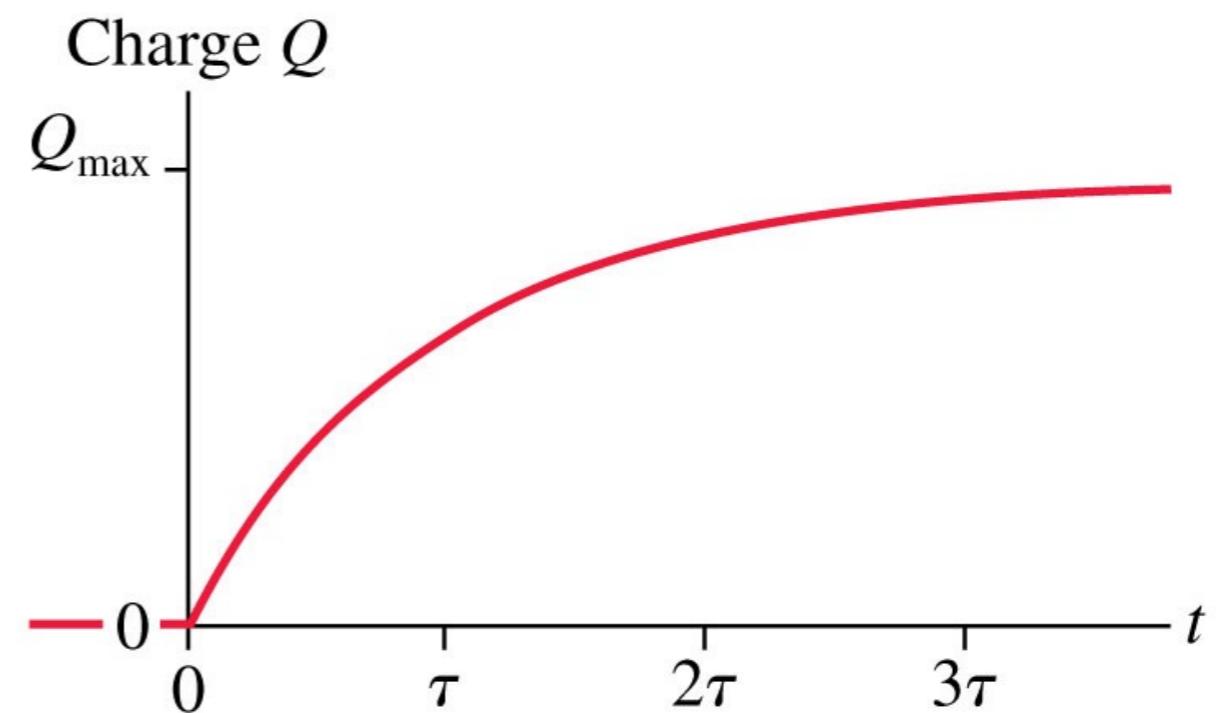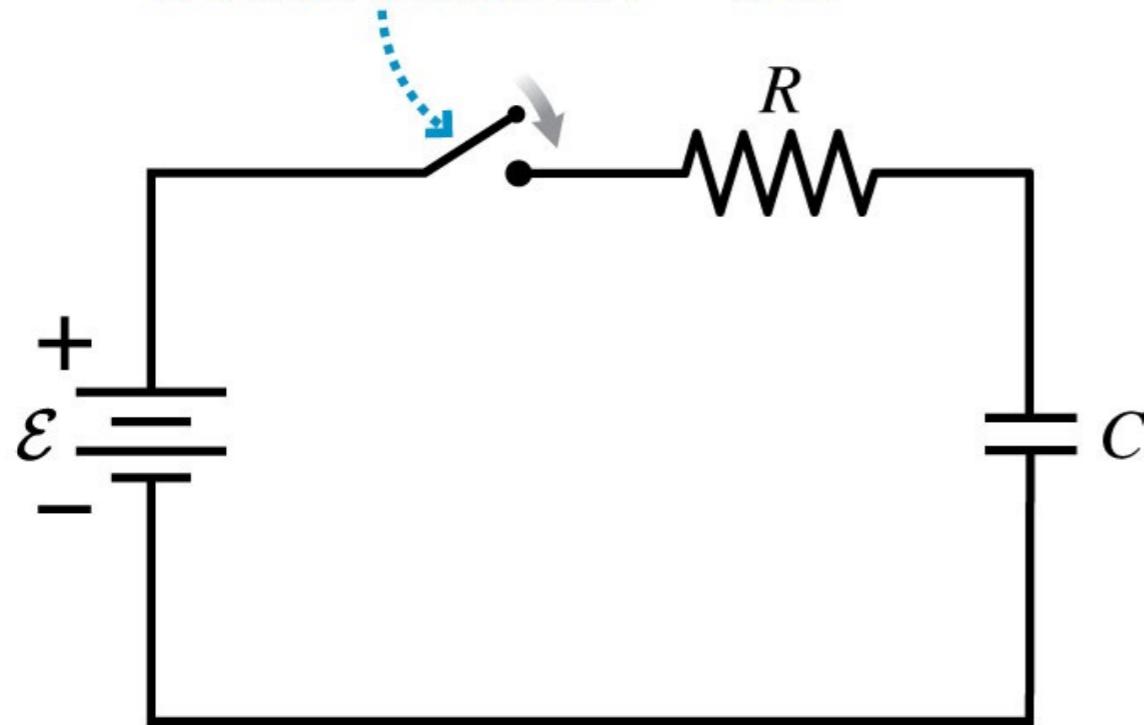

# The Math

Write down Kirchoff's loop rule for this circuit

Switch closes at  $t = 0$  s.

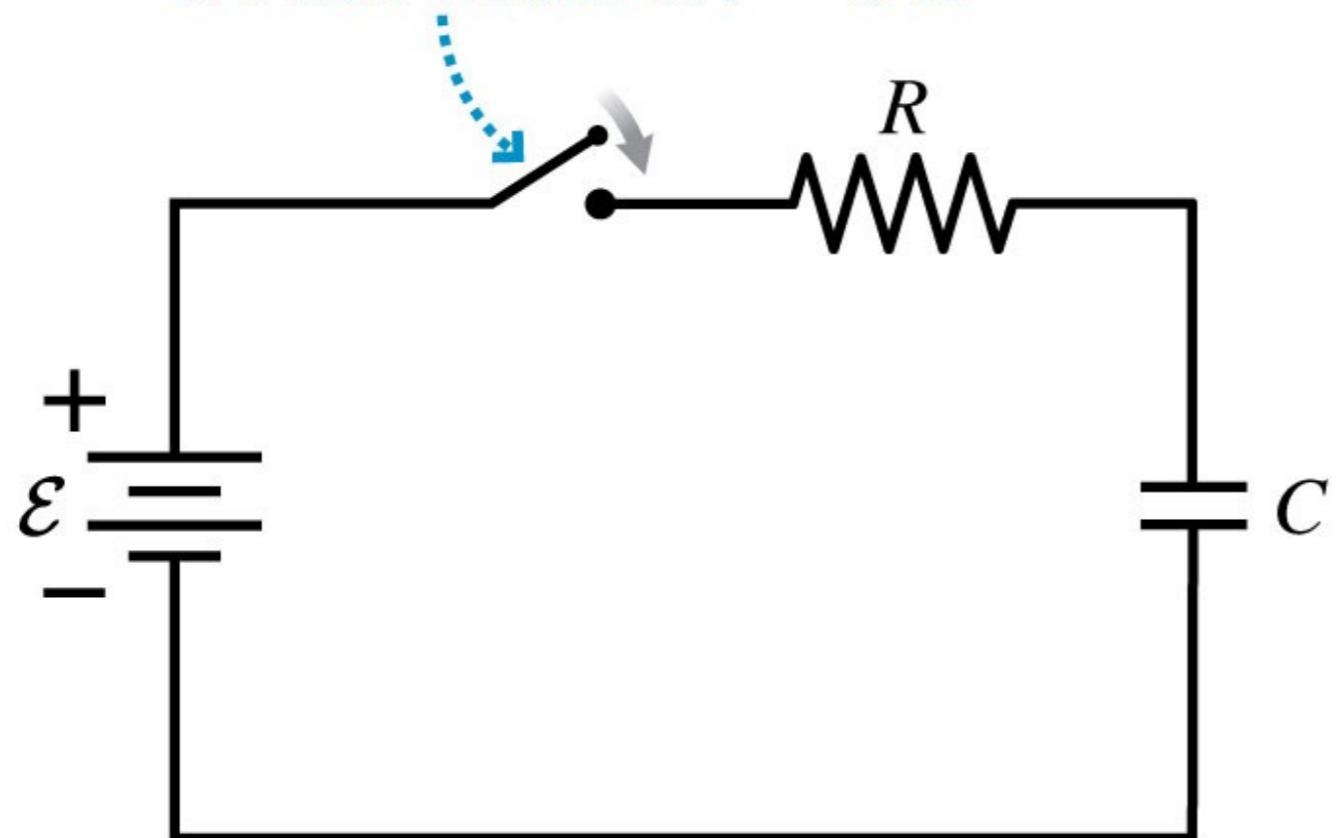


# The Math

Write down Kirchoff's loop rule for this circuit

$$\epsilon - IR - \frac{q}{C} = 0$$

Switch closes at  $t = 0$  s.

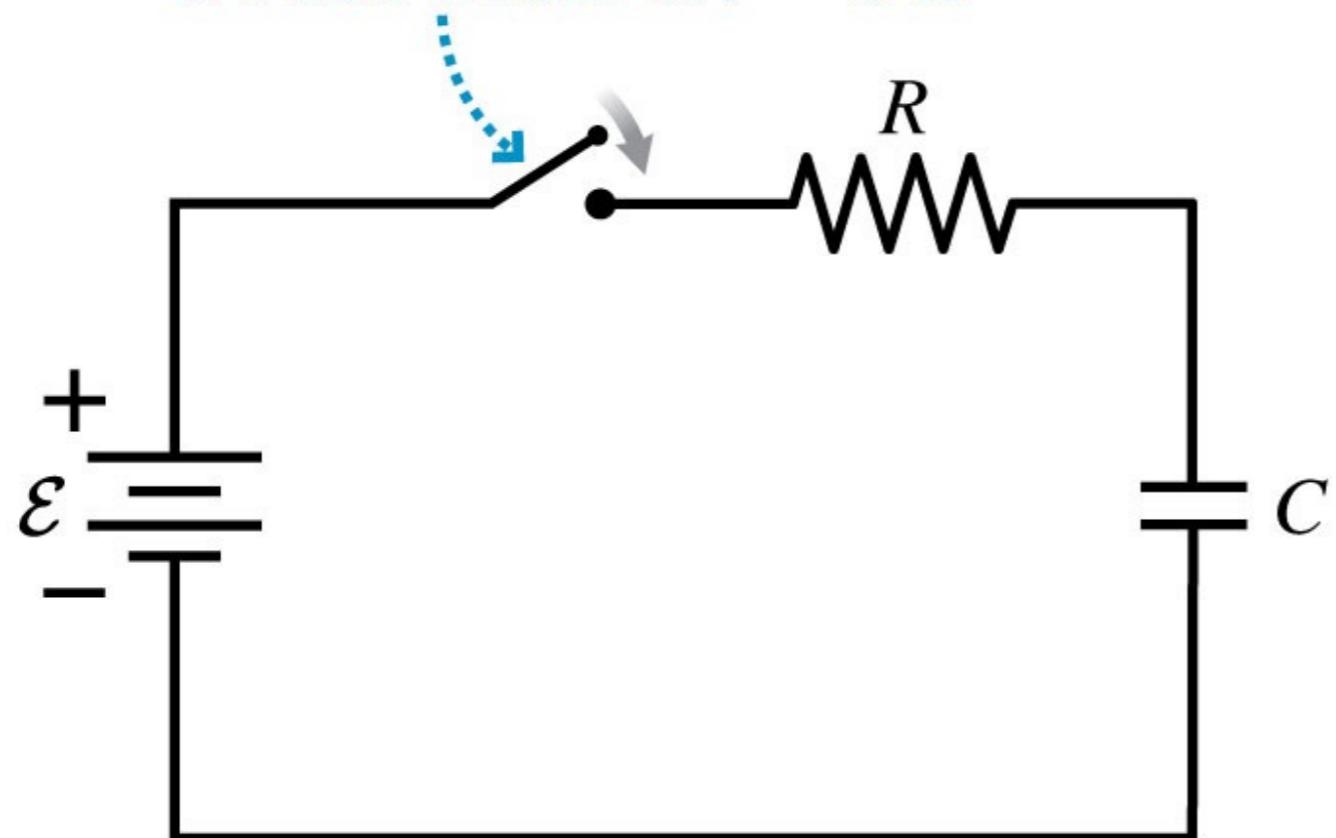


# The Math

Write down Kirchoff's loop rule for this circuit

$$\epsilon - IR - \frac{q}{C} = 0$$

Switch closes at  $t = 0$  s.

$$I = \frac{dq}{dt}$$

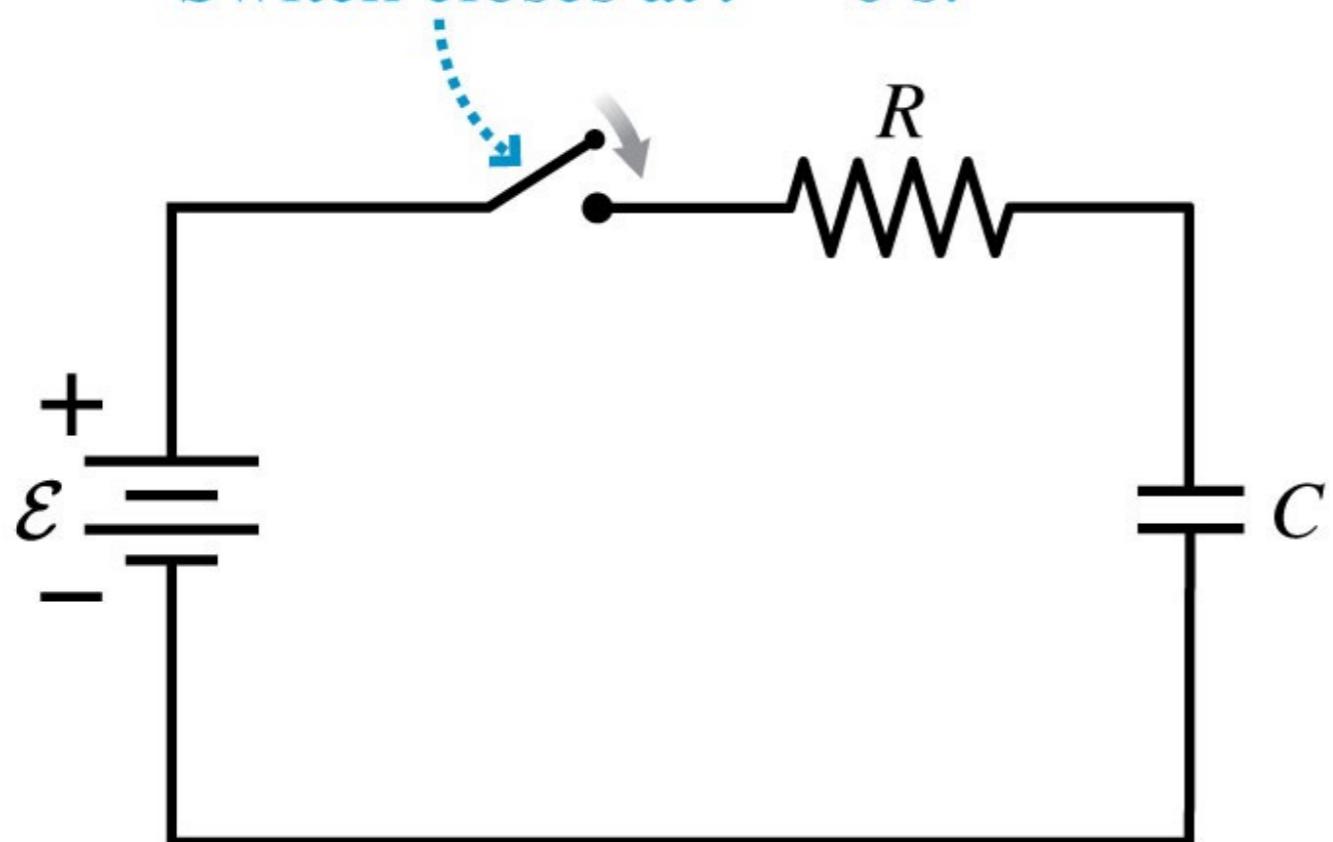


# The Math

Write down Kirchoff's loop rule for this circuit

$$\epsilon - IR - \frac{q}{C} = 0$$

Switch closes at  $t = 0$  s.

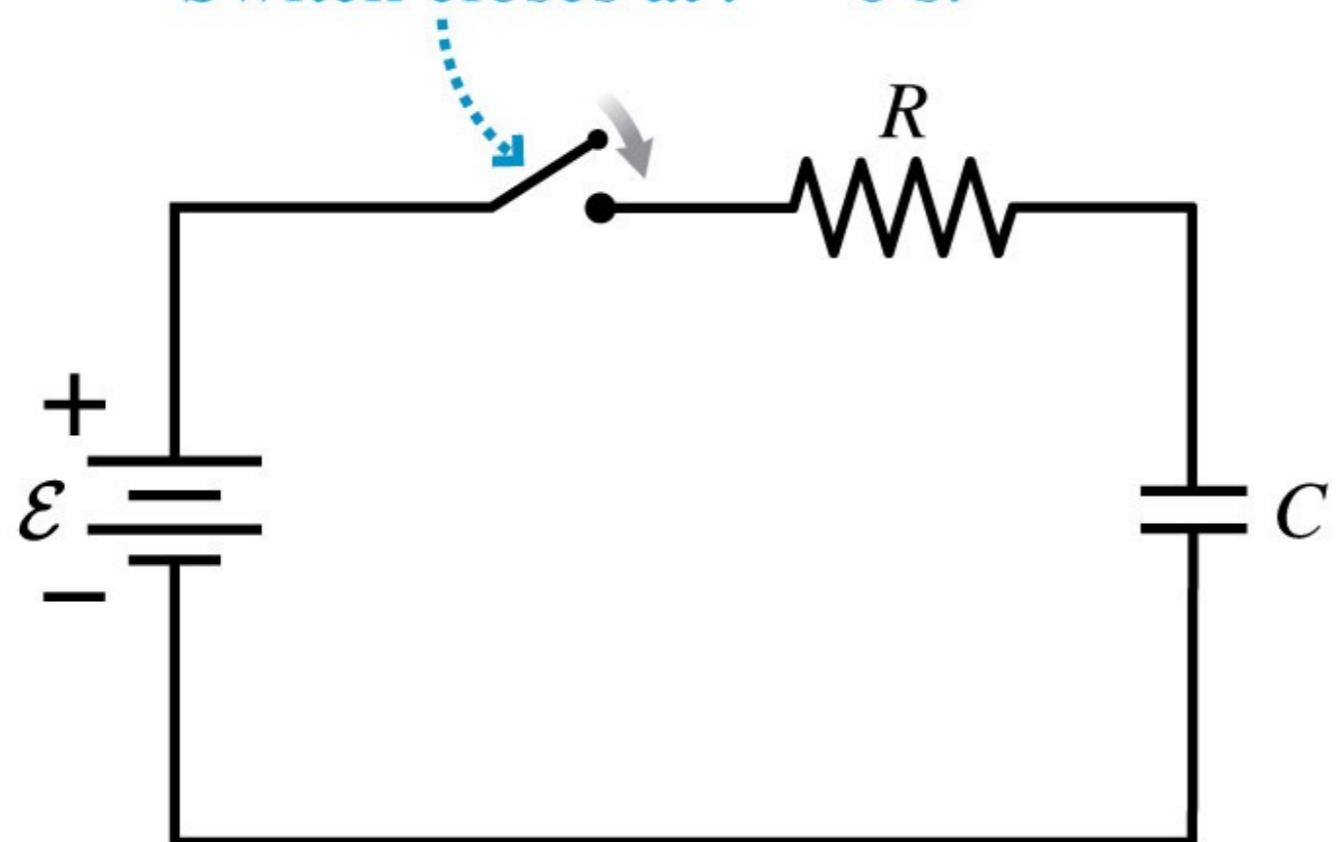

$$I = \frac{dq}{dt}$$


$$\epsilon - \frac{dq}{dt}R - \frac{q}{C} = 0$$

# The Math

Write down Kirchoff's loop rule for this circuit

$$\epsilon - IR - \frac{q}{C} = 0$$

Switch closes at  $t = 0$  s.

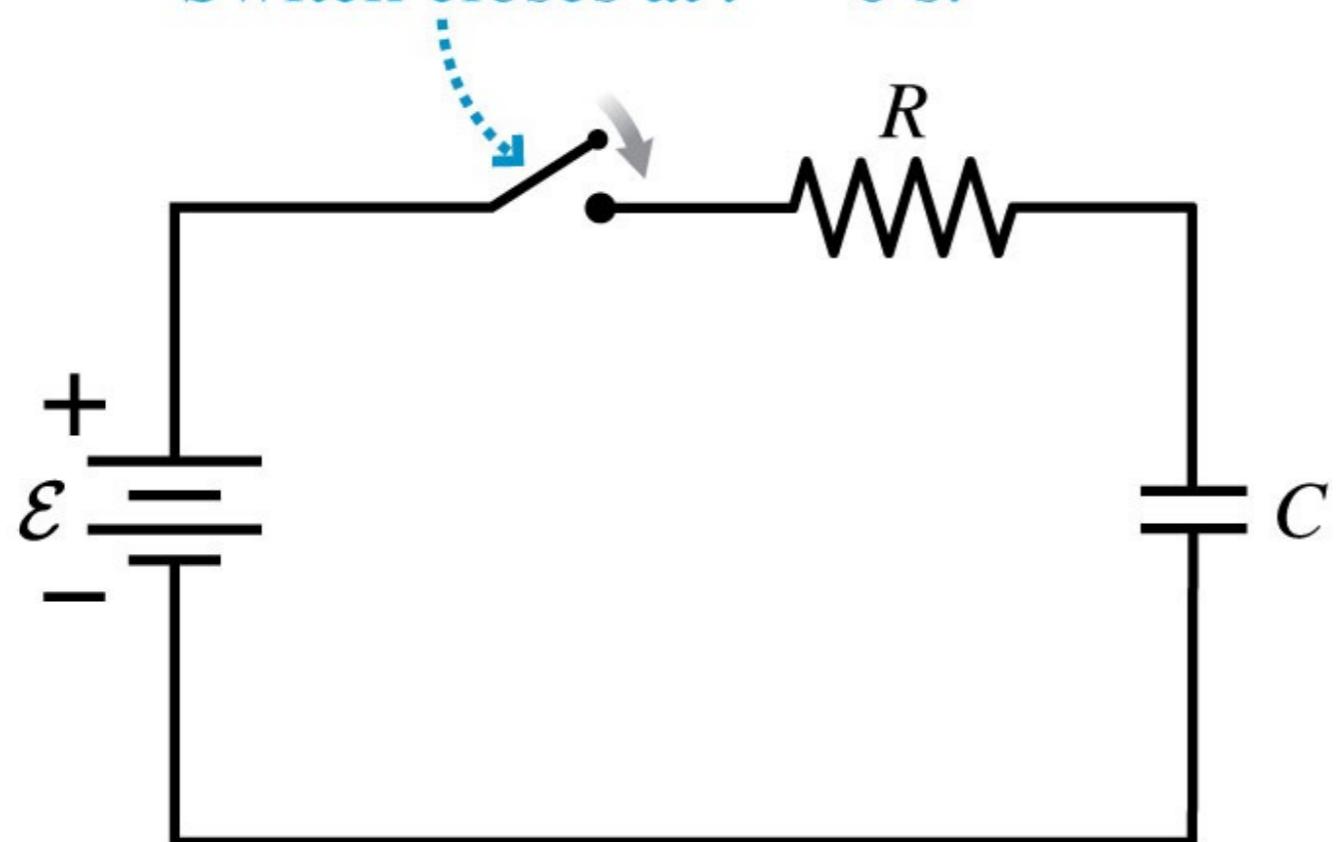

$$I = \frac{dq}{dt}$$

$$\epsilon - \frac{dq}{dt}R - \frac{q}{C} = 0$$


- a) Gather all the variables with  $Q$  in them to one side.
- b) Integrate both sides.

# The Math

Write down Kirchoff's loop rule for this circuit

$$\epsilon - IR - \frac{q}{C} = 0$$

Switch closes at  $t = 0$  s.

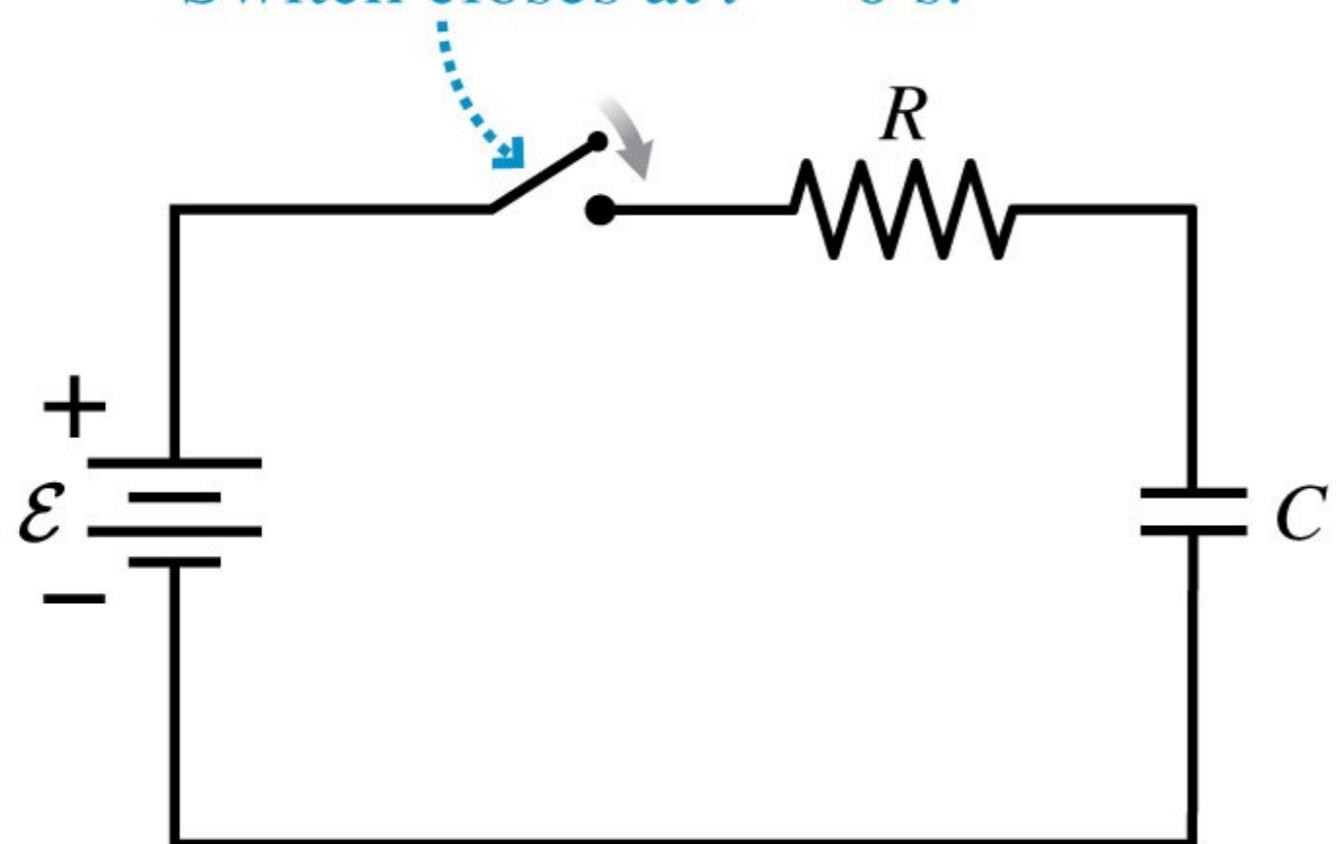

$$I = \frac{dq}{dt}$$

$$\epsilon - \frac{dq}{dt}R - \frac{q}{C} = 0$$

- Gather all the variables with  $Q$  in them to one side.
- Integrate both sides.


$$\int_0^Q \frac{dq}{\epsilon c - q} = \int_0^t \frac{dt}{RC}$$

# The Math

Write down Kirchoff's loop rule for this circuit

$$\epsilon - IR - \frac{q}{C} = 0$$

Switch closes at  $t = 0$  s.

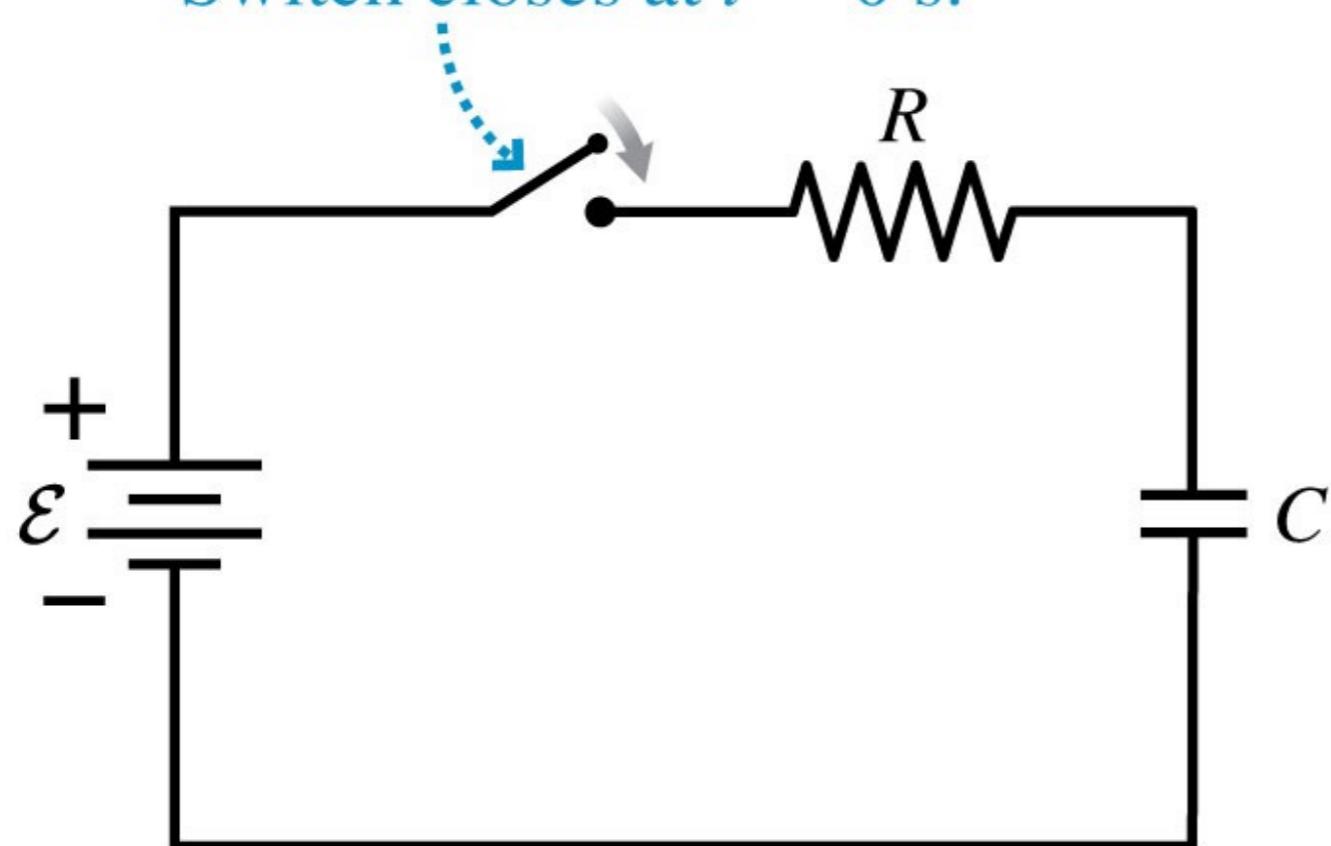

$$I = \frac{dq}{dt}$$

$$\epsilon - \frac{dq}{dt}R - \frac{q}{C} = 0$$

- Gather all the variables with Q in them to one side.
- Integrate both sides.

$$Q = Q_{\max}(1 - e^{-t/\tau})$$


$$\tau = RC$$

$$\int_0^Q \frac{dq}{\epsilon c - q} = \int_0^t \frac{dt}{RC}$$

# The Math

Write down Kirchoff's

$$\epsilon - IR - \frac{q}{C} = 0$$

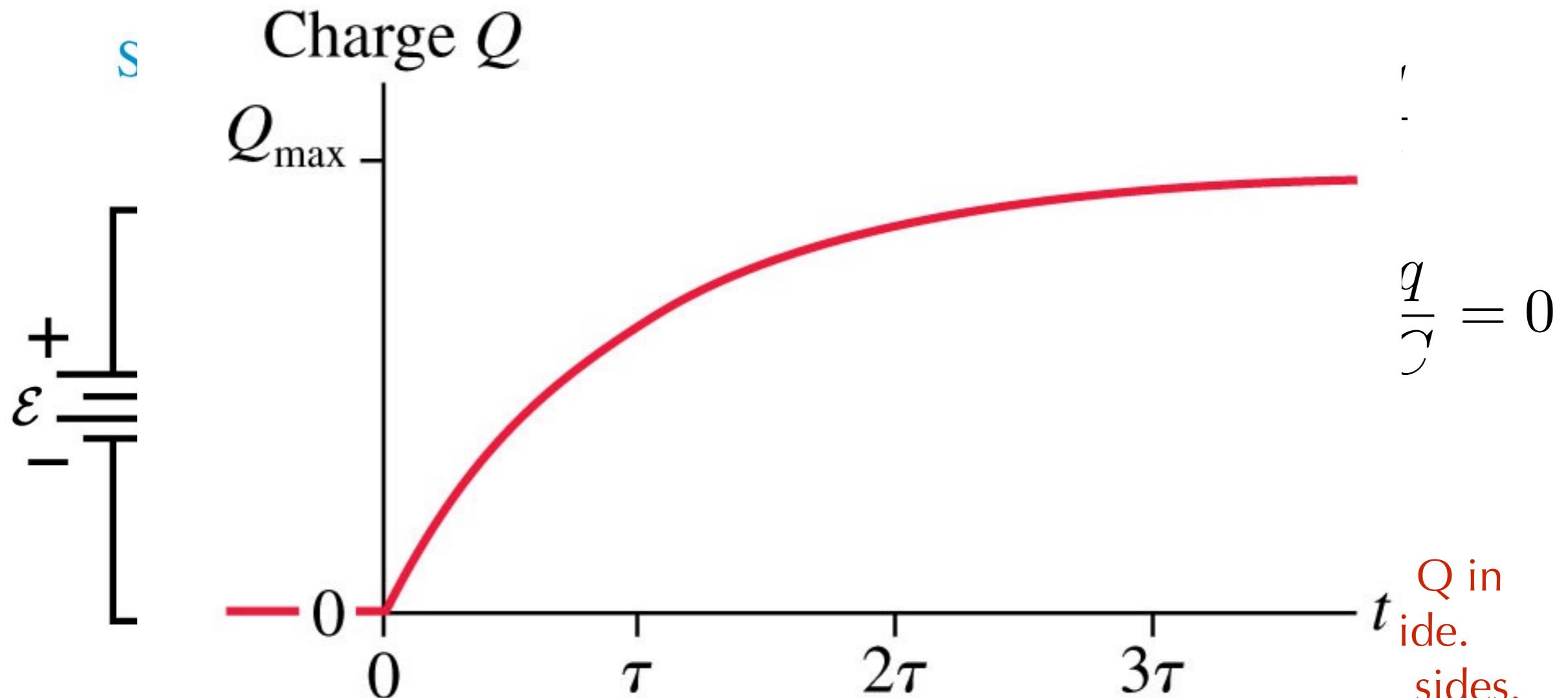

$$\int_0^Q \frac{dq}{\epsilon c - q} = \int_0^t \frac{dt}{RC}$$