





PH 220


Lance Nelson


How does the resistance of D compare to that of A:

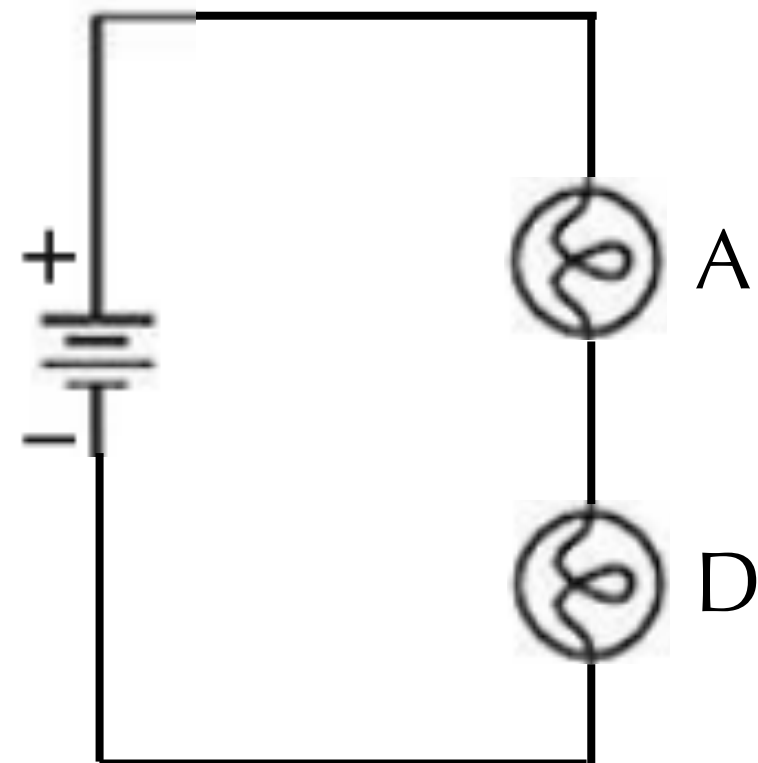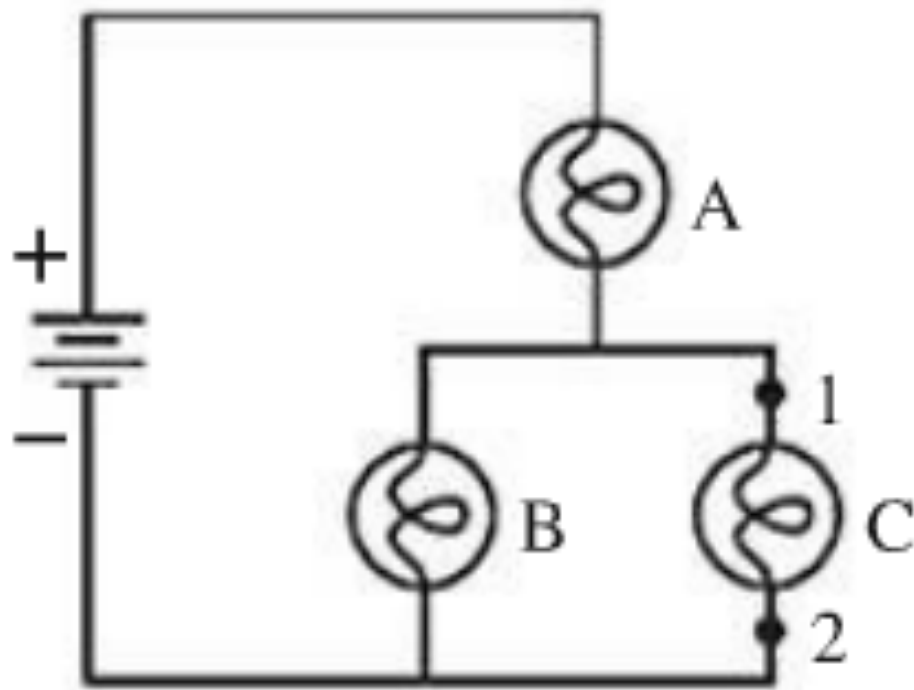- a) before the wire is placed between 1 and 2
- b) after the wire is placed between 1 and 2



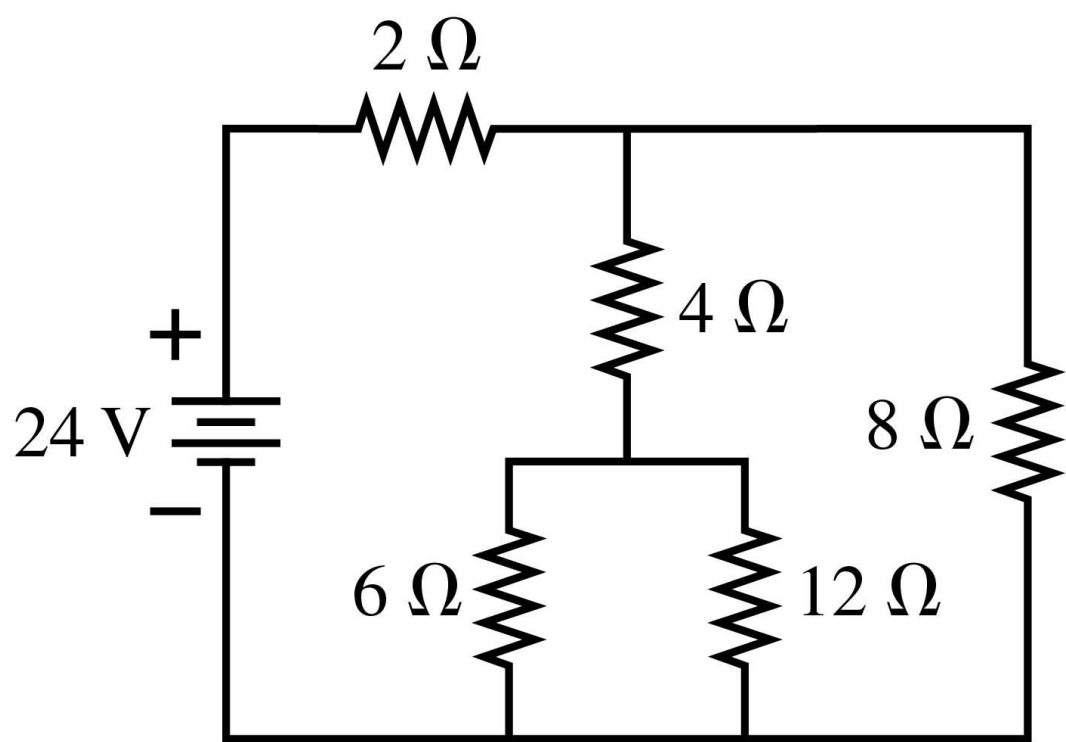Compare the current in the circuit before the short to after the short.



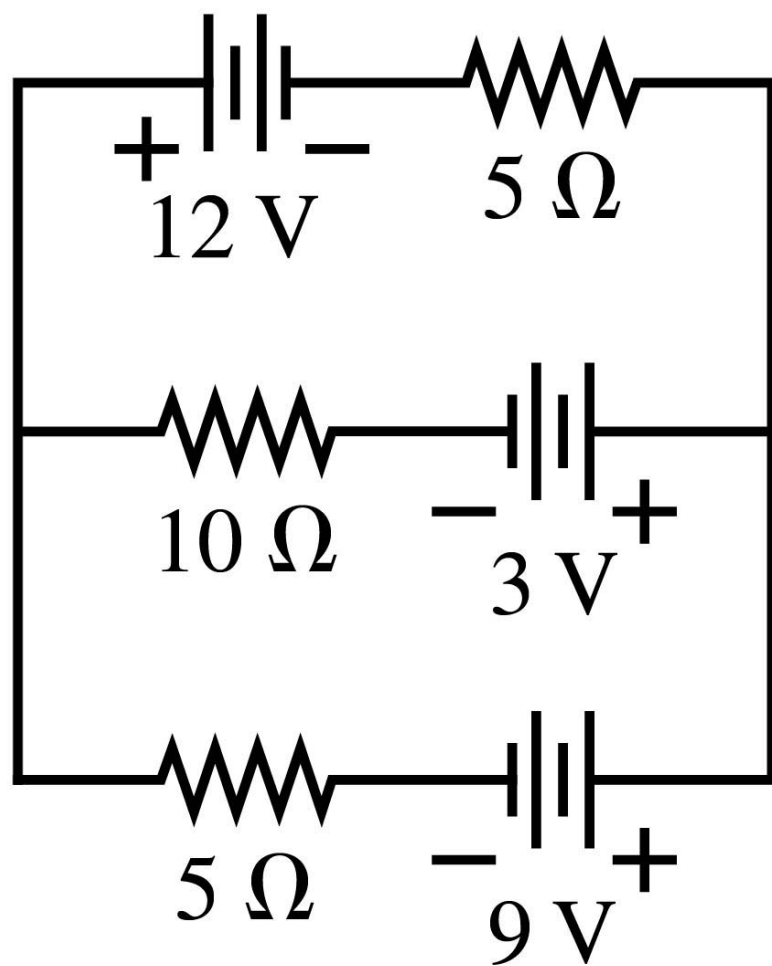


Ammeters and Voltmeters


(a)




(b)

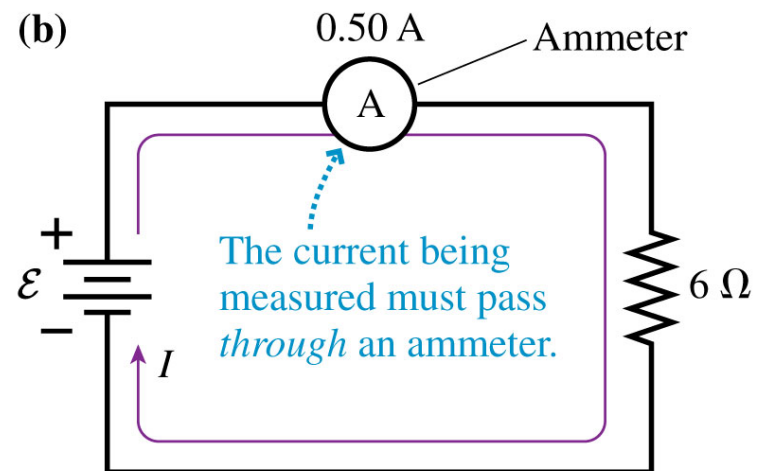


(a)

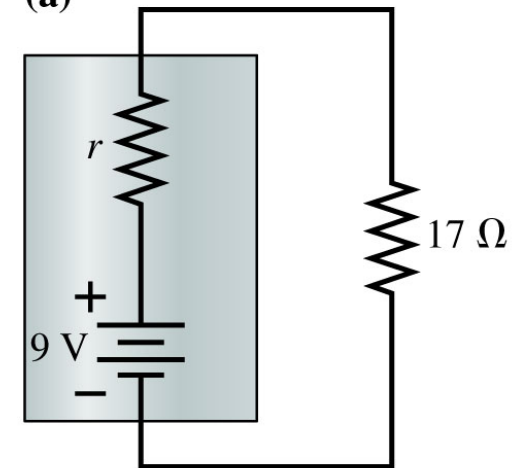

(b)

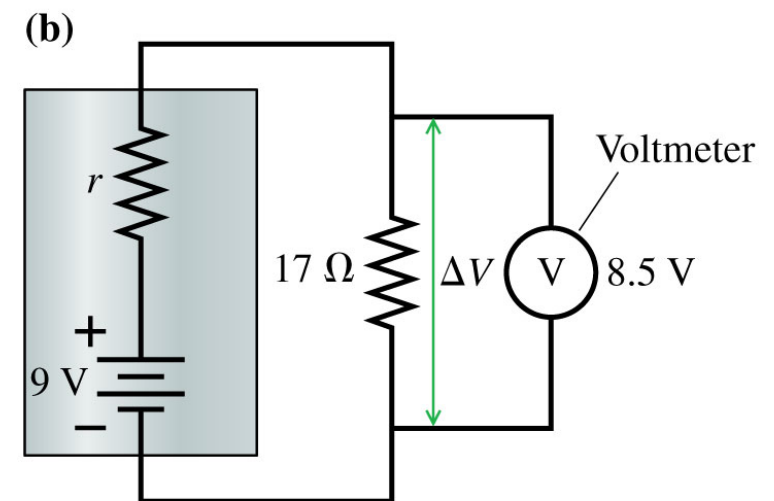


What does the voltmeter read?

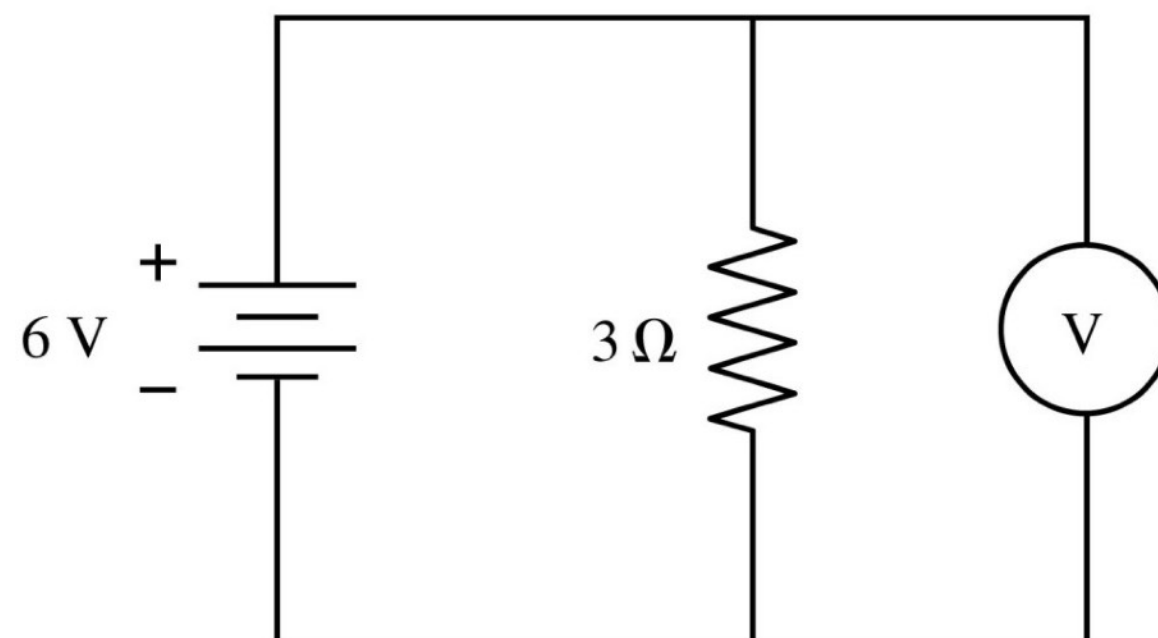


What does the voltmeter read?

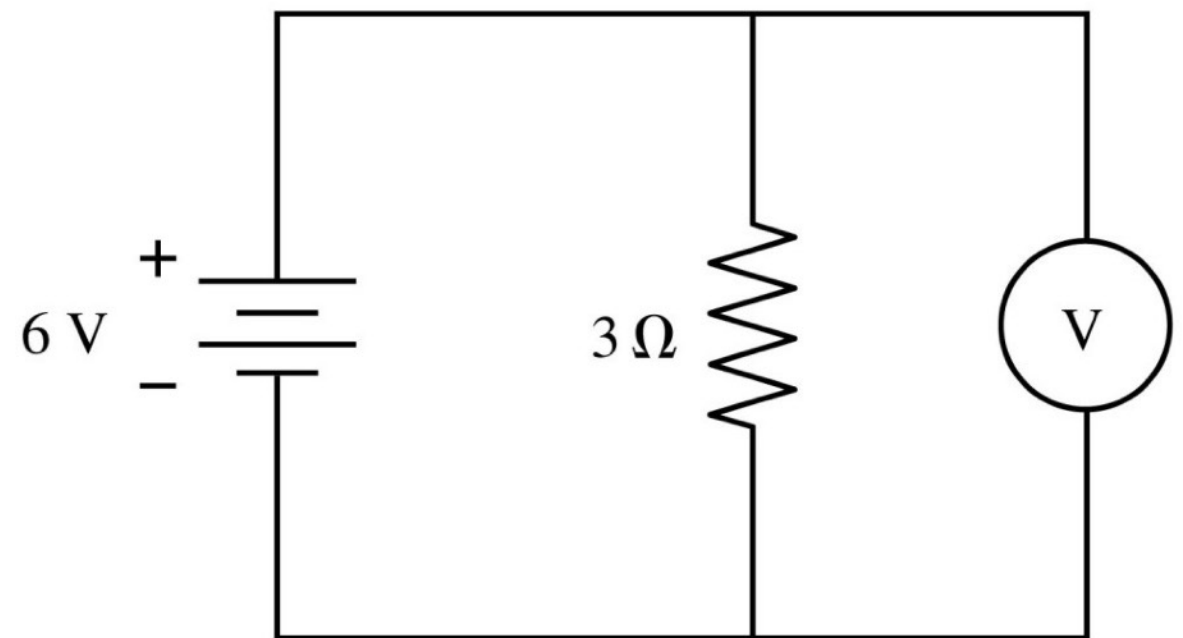- A. 6 V.
- B. 3 V.
- C. 2 V.
- D. Some other value.
- E. Nothing because this will fry the meter.




What does the ammeter read?

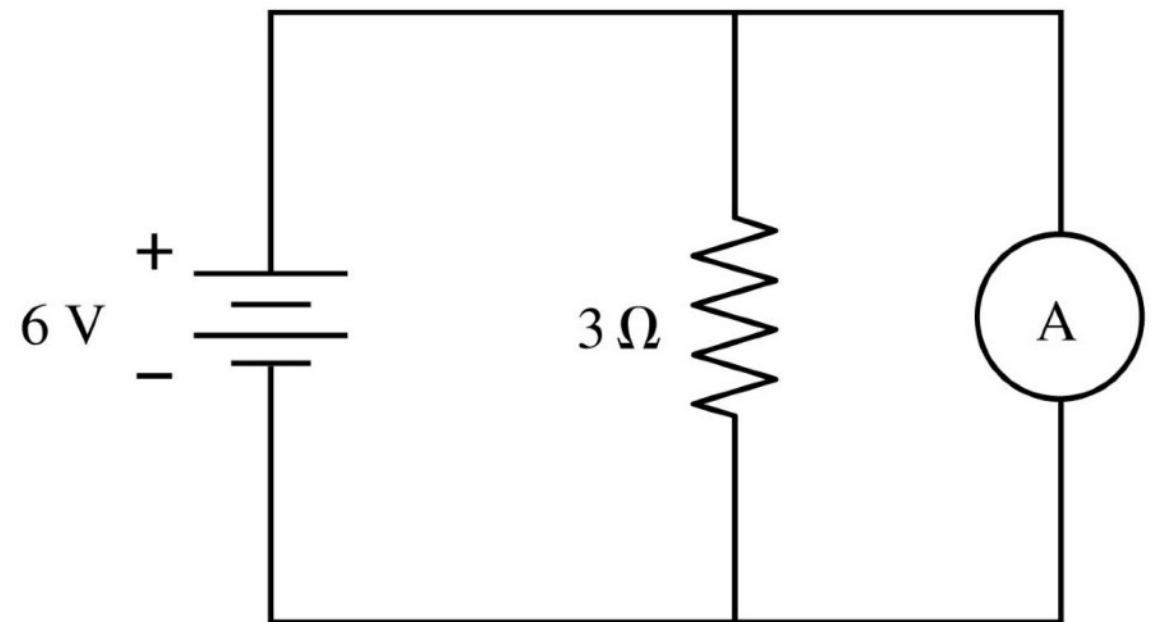
- A. 6 V.
- B. 3 V.
- C. 2 V.
- D. Some other value.
- E. Nothing because this will fry the meter.




Getting Grounded

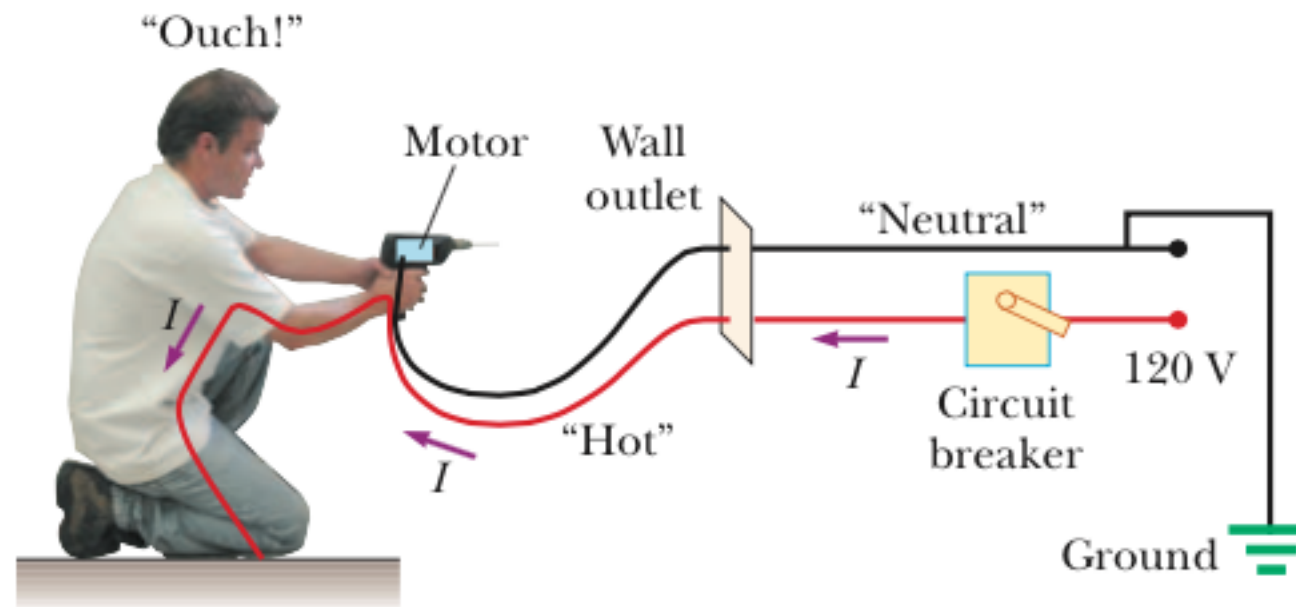

(a)


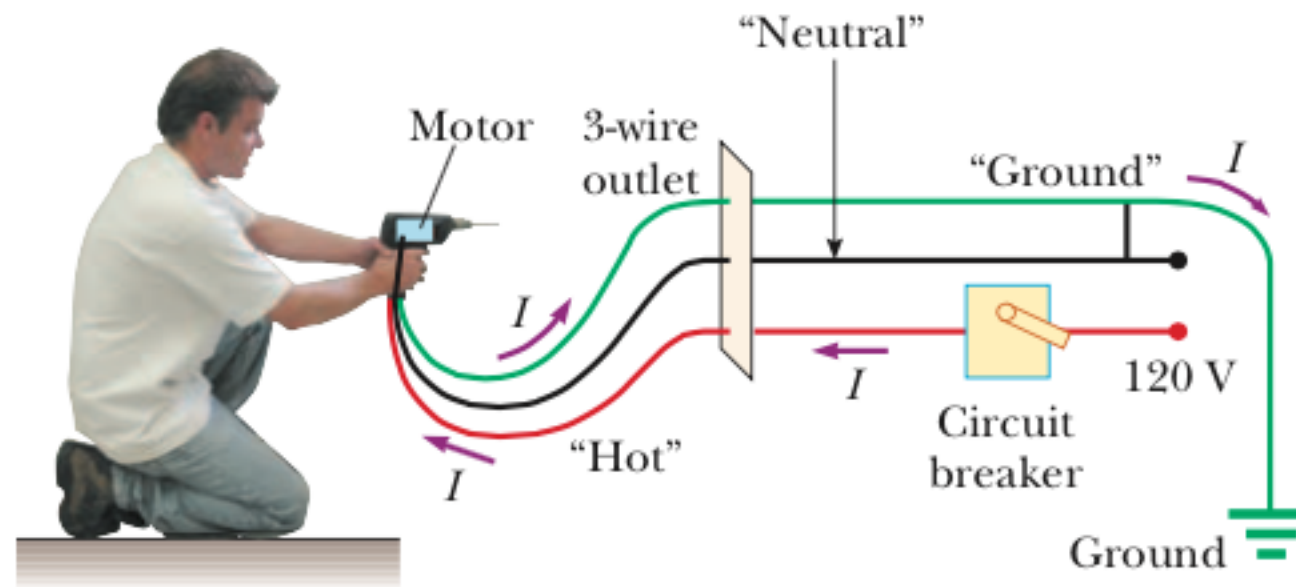


Grounding a circuit

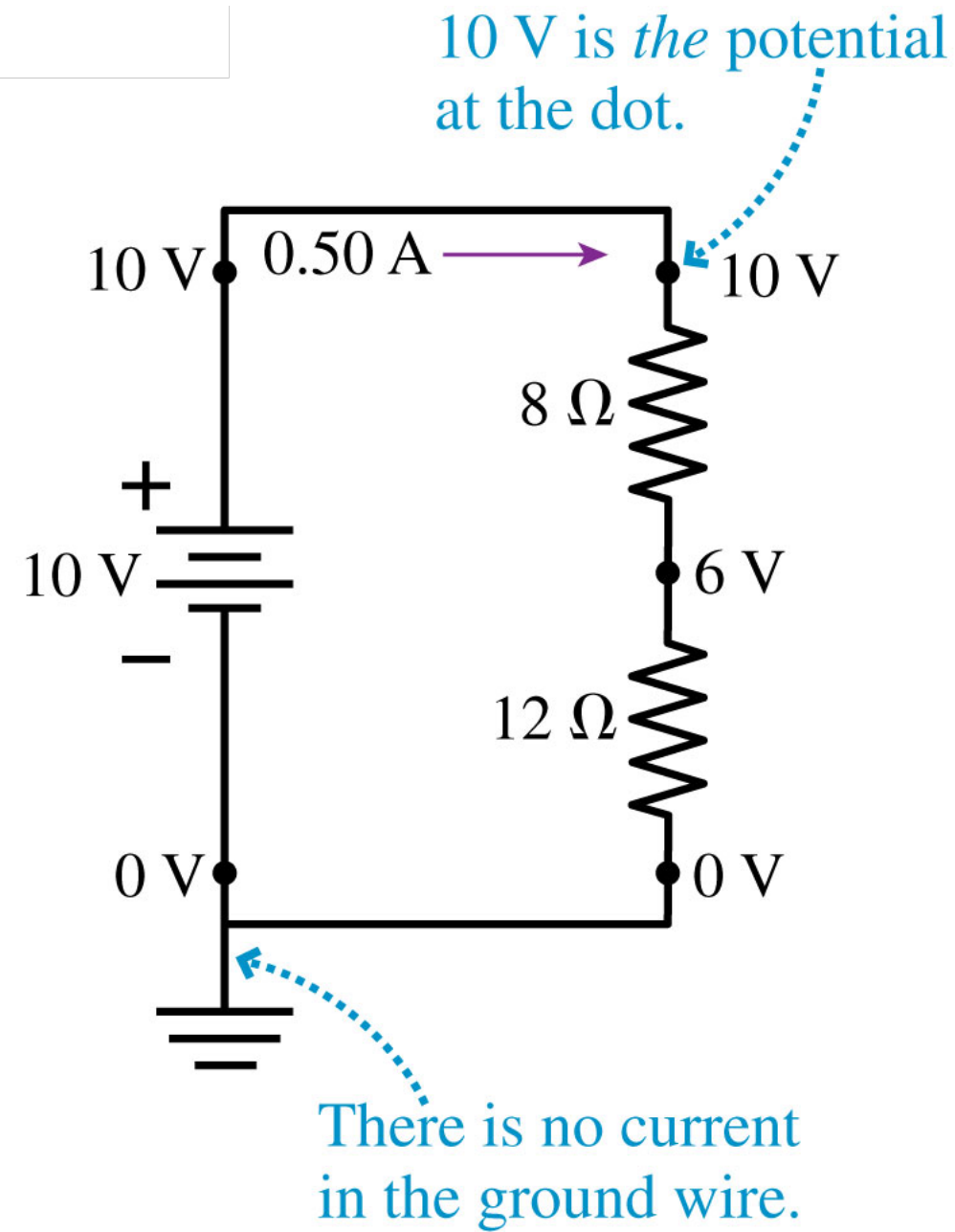


Real Batteries

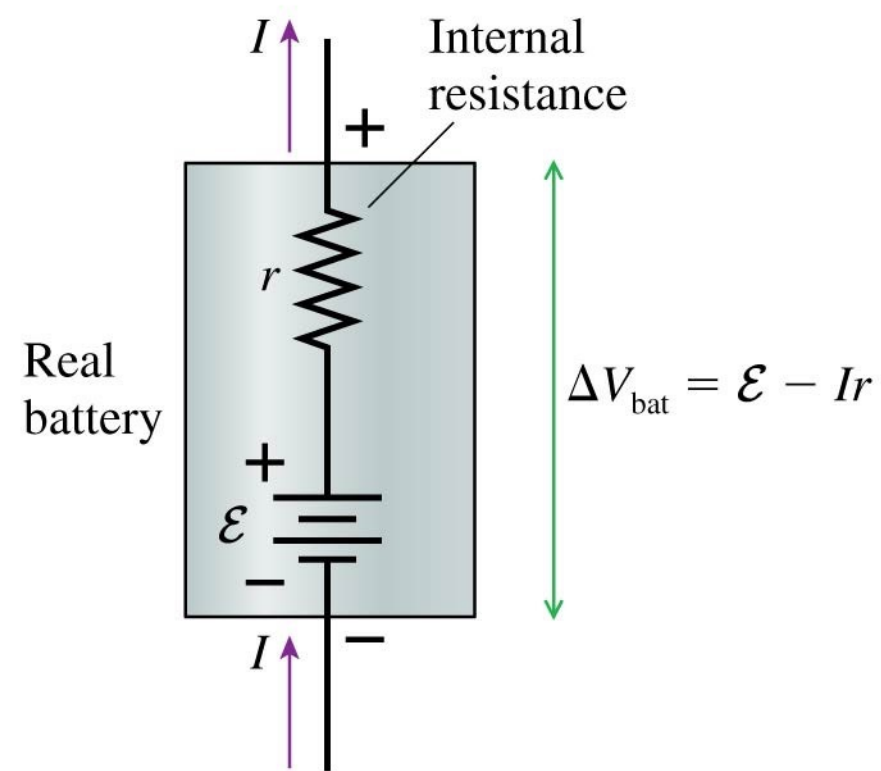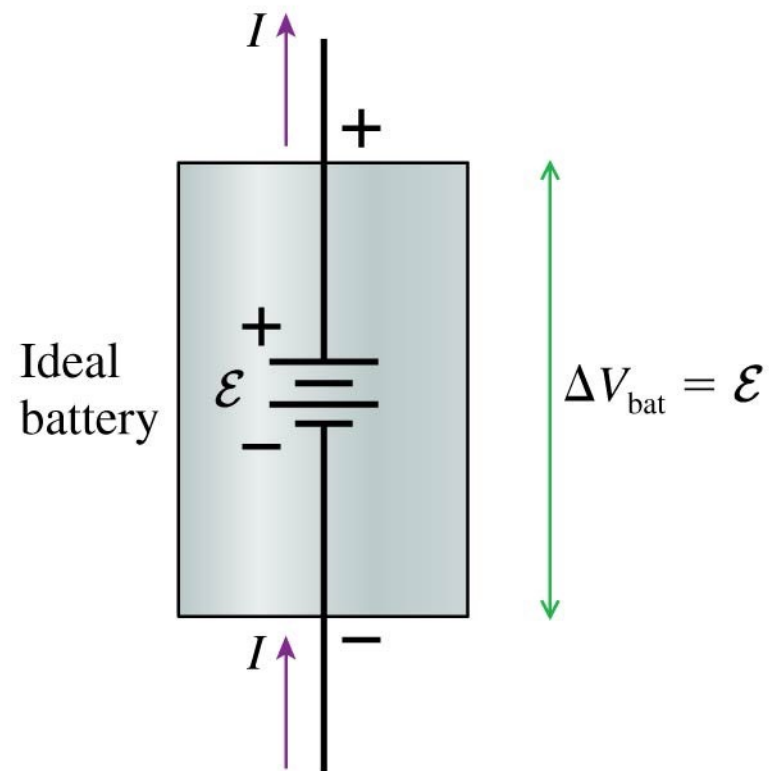
The batterie's internal resistance limits the max current.



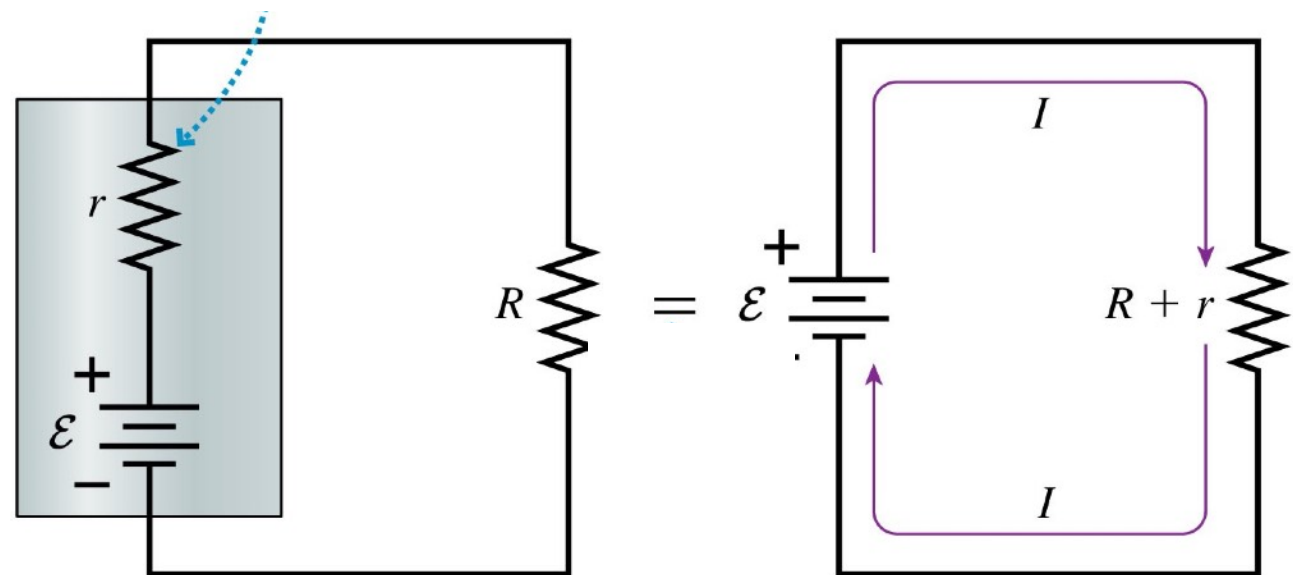
$$\Delta V_R = IR = \frac{\mathcal{E}}{R + r} R$$




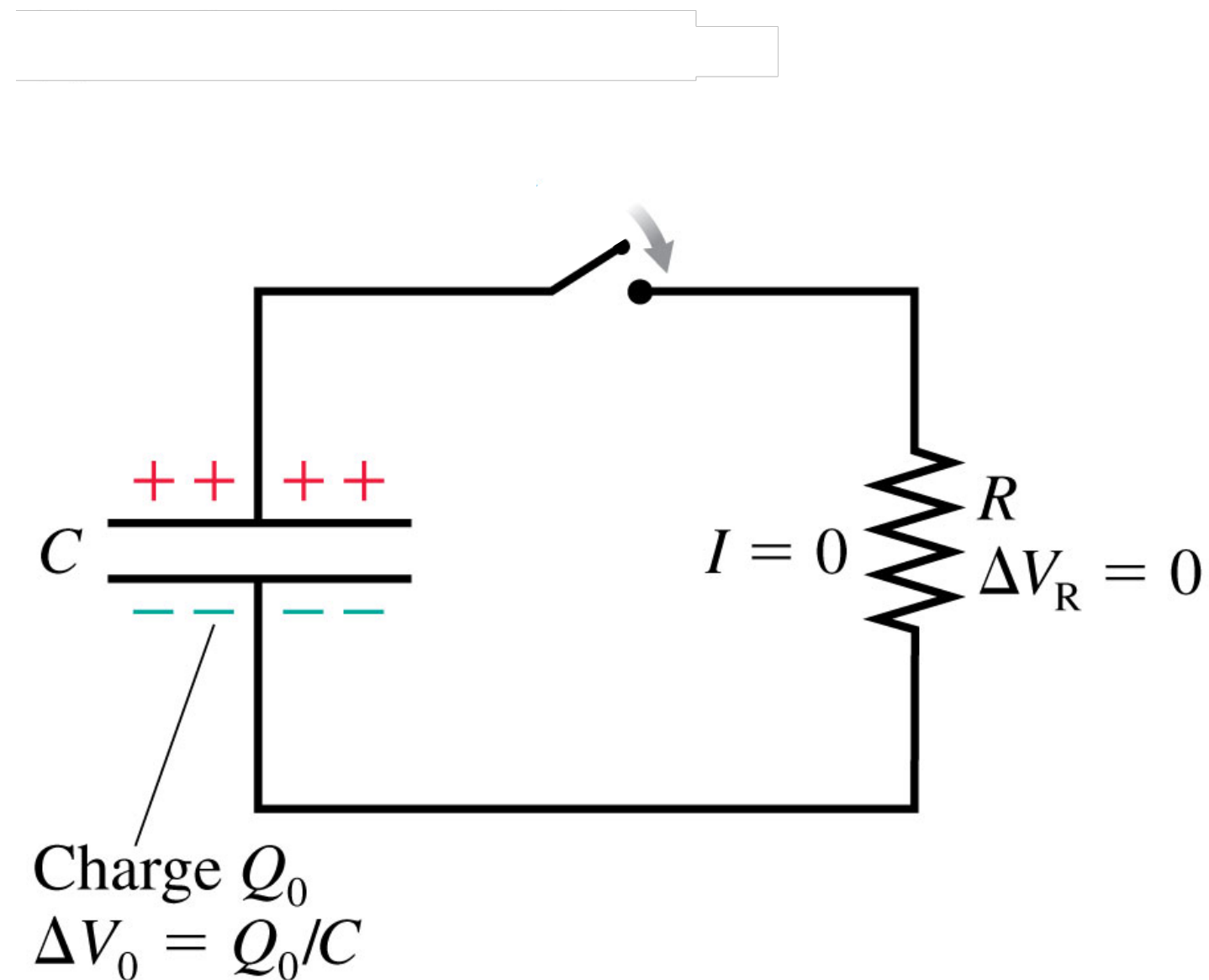Without looking in the book. Sketch the Q vs. time curve for the capacitor.



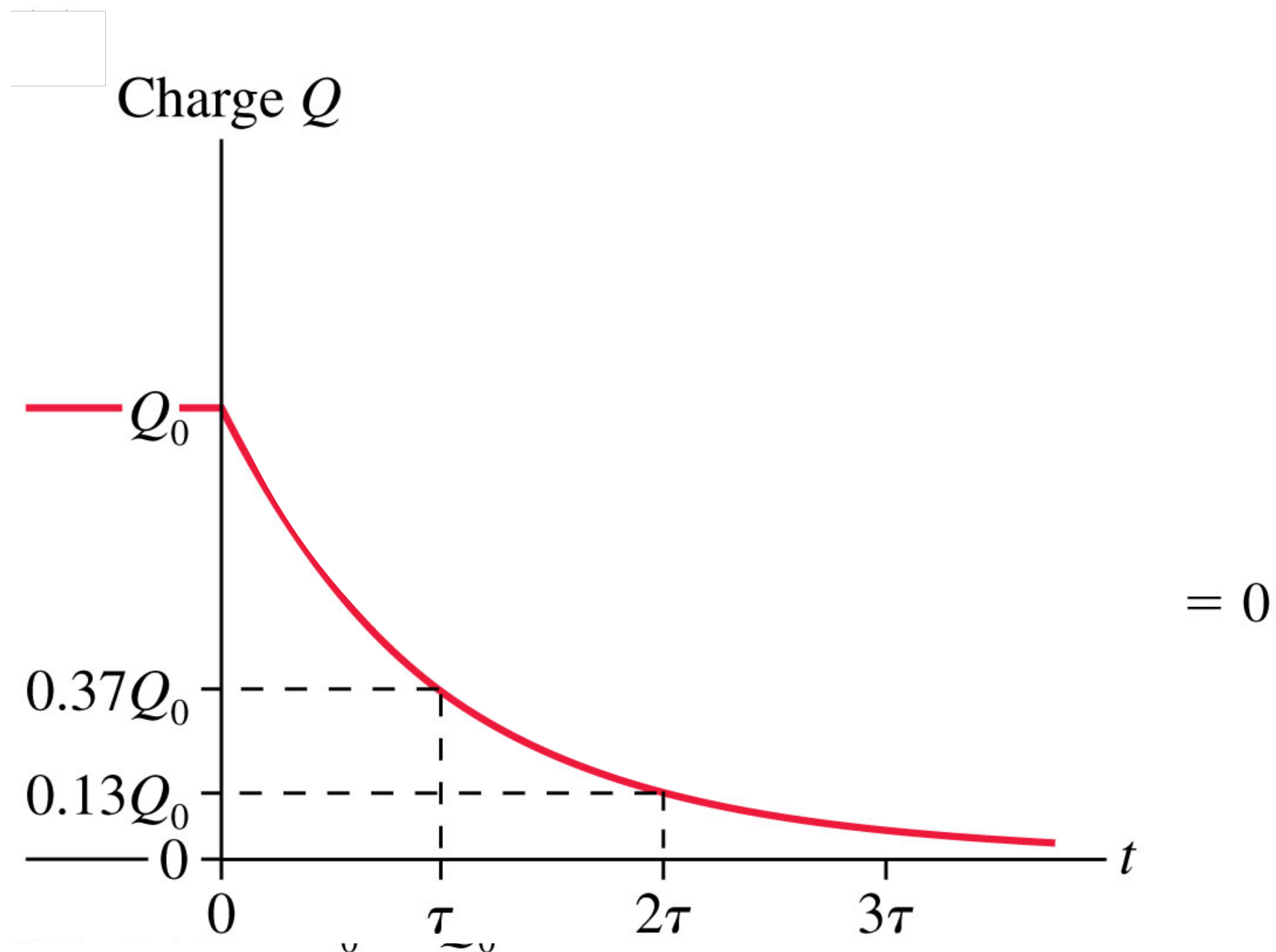
Without looking in the book. Sketch the Q vs. time curve for the capacitor.



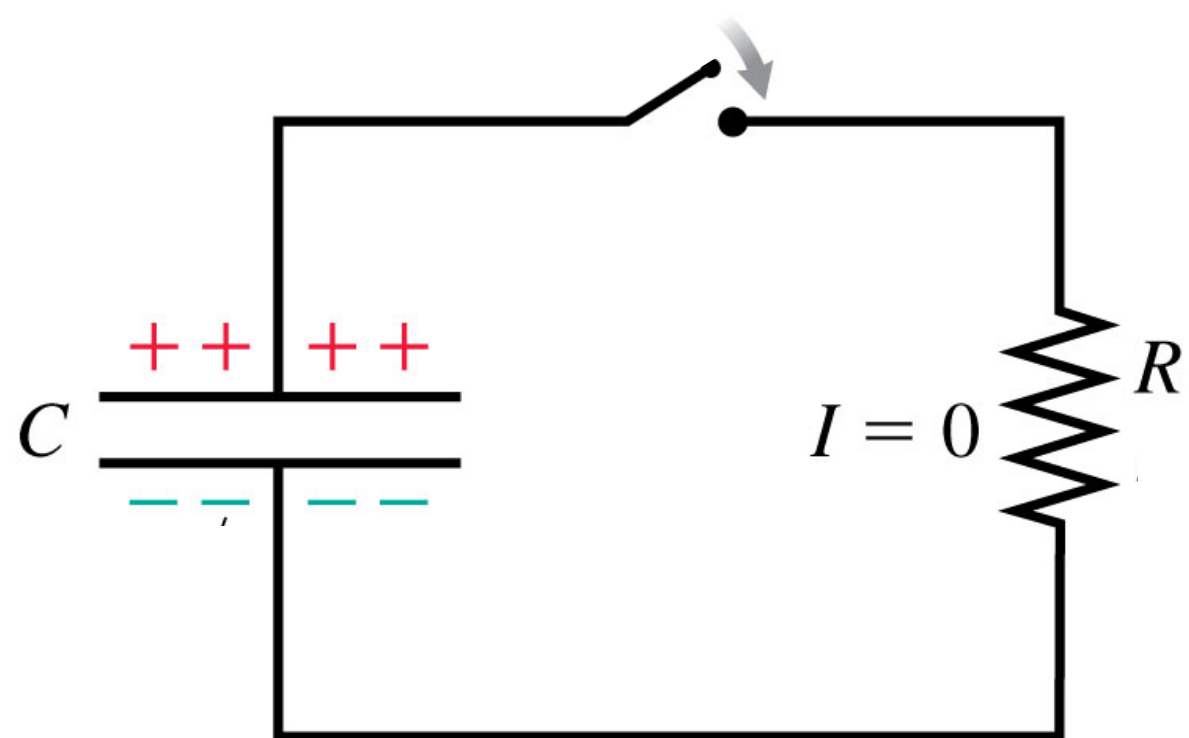

The Math

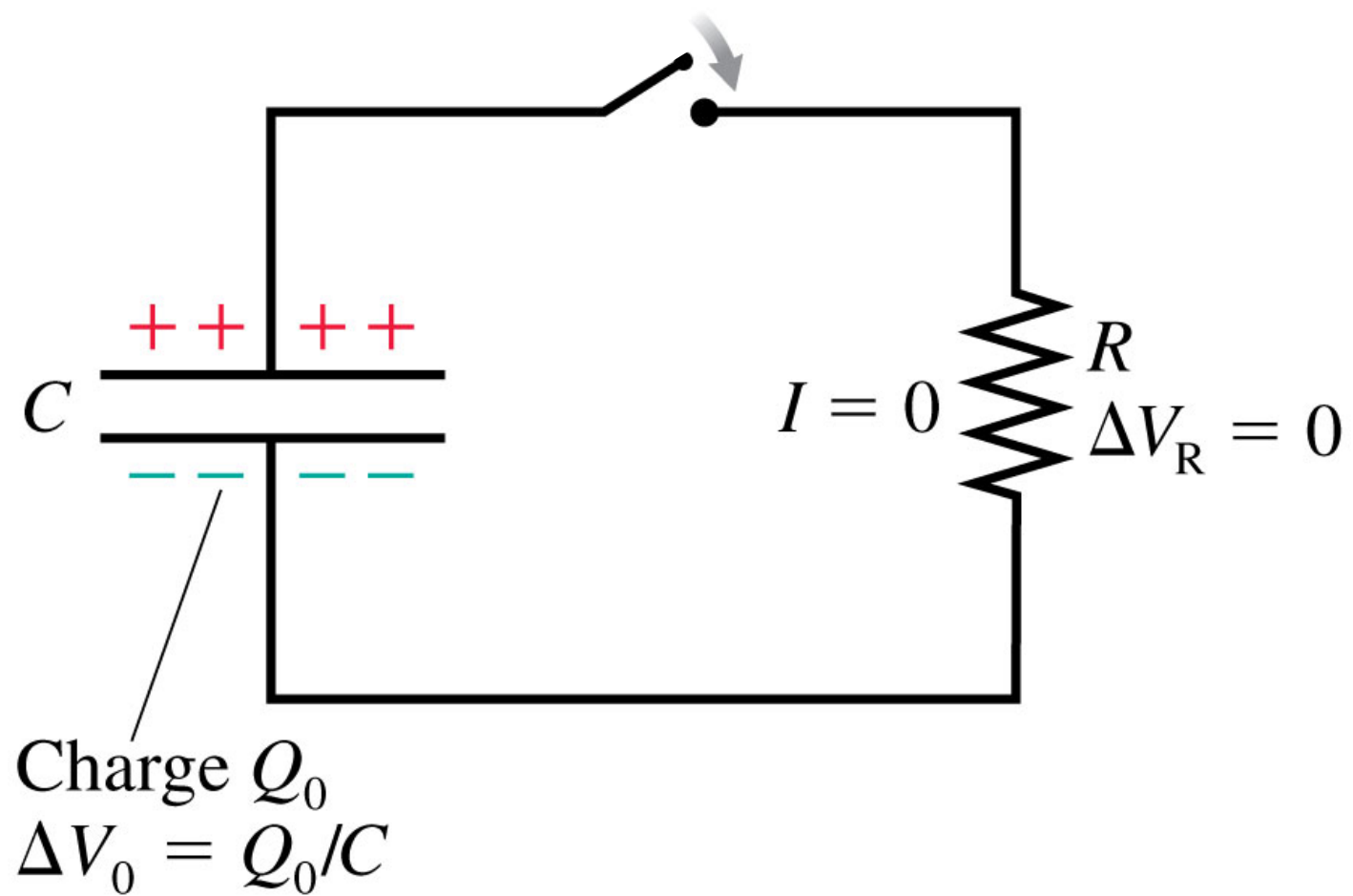
Write down Kirchhoff's
loop rule for this circuit



The Math


Write down Kirchoff's
loop rule for this circuit
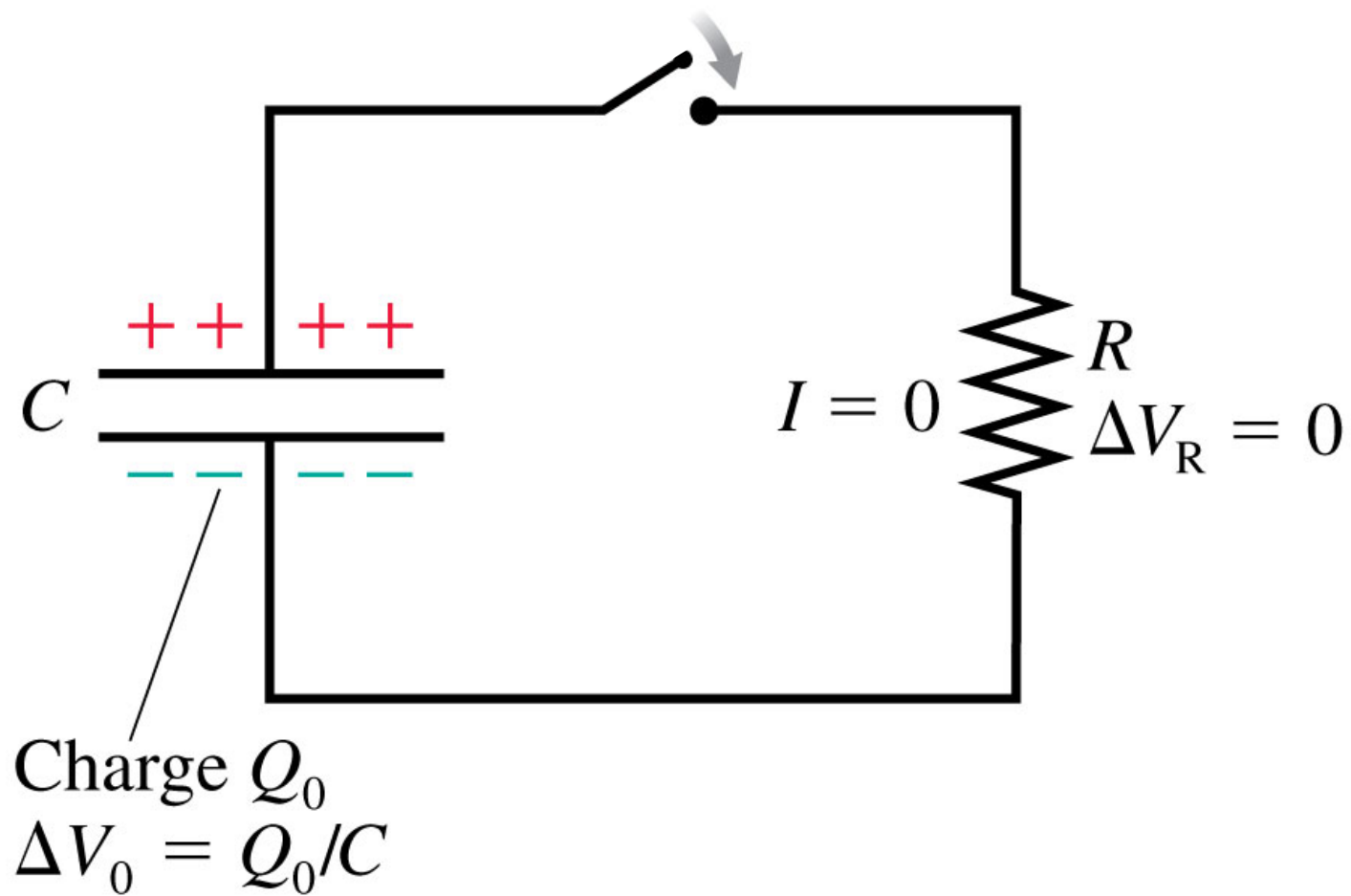
$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$



The Math

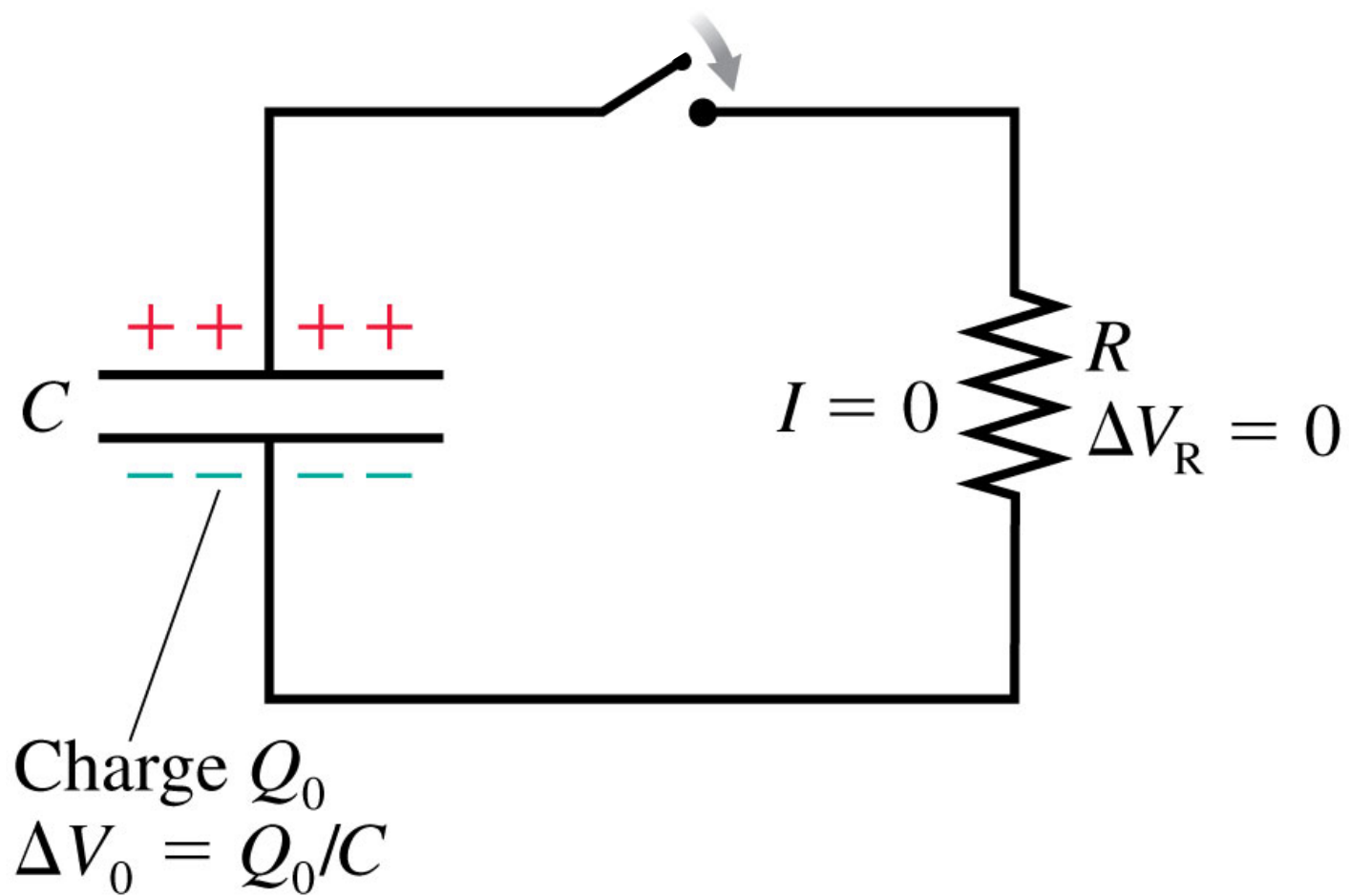Write down Kirchoff's
loop rule for this circuit




$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$

The Math

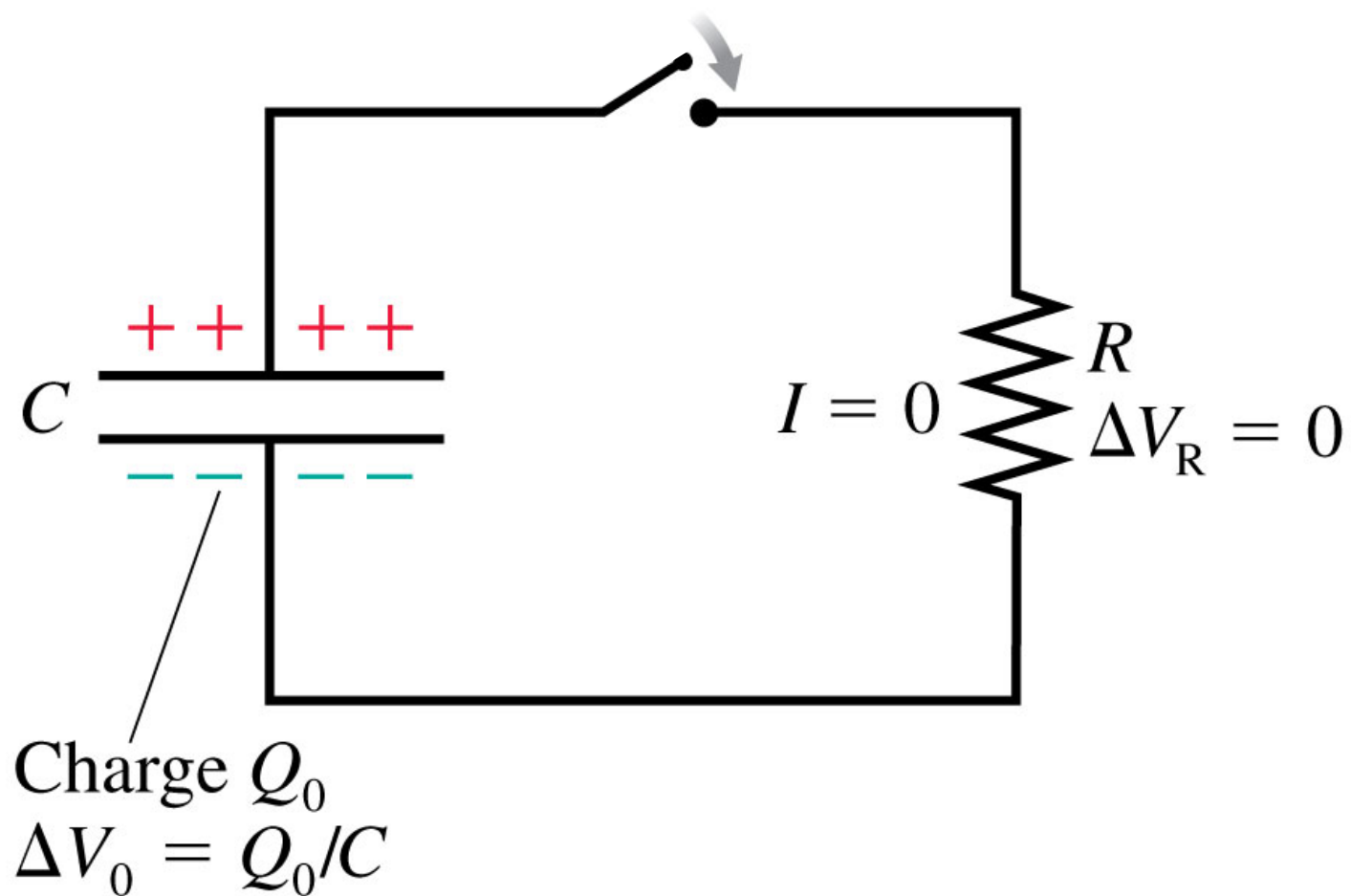Write down Kirchoff's
loop rule for this circuit




$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$

$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$

The Math

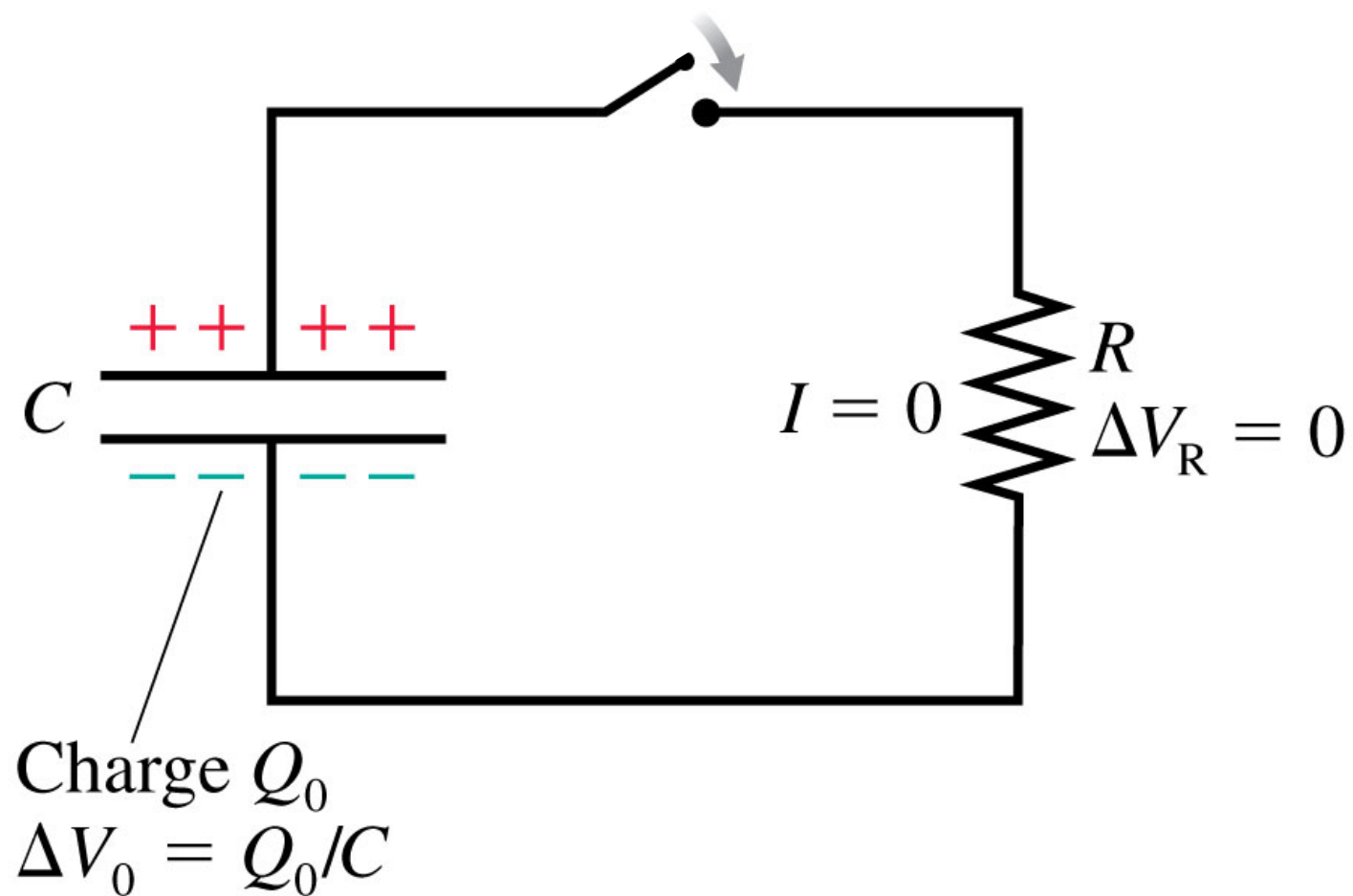Write down Kirchoff's loop rule for this circuit



$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$


$$I = -\frac{dQ}{dt}$$

$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$

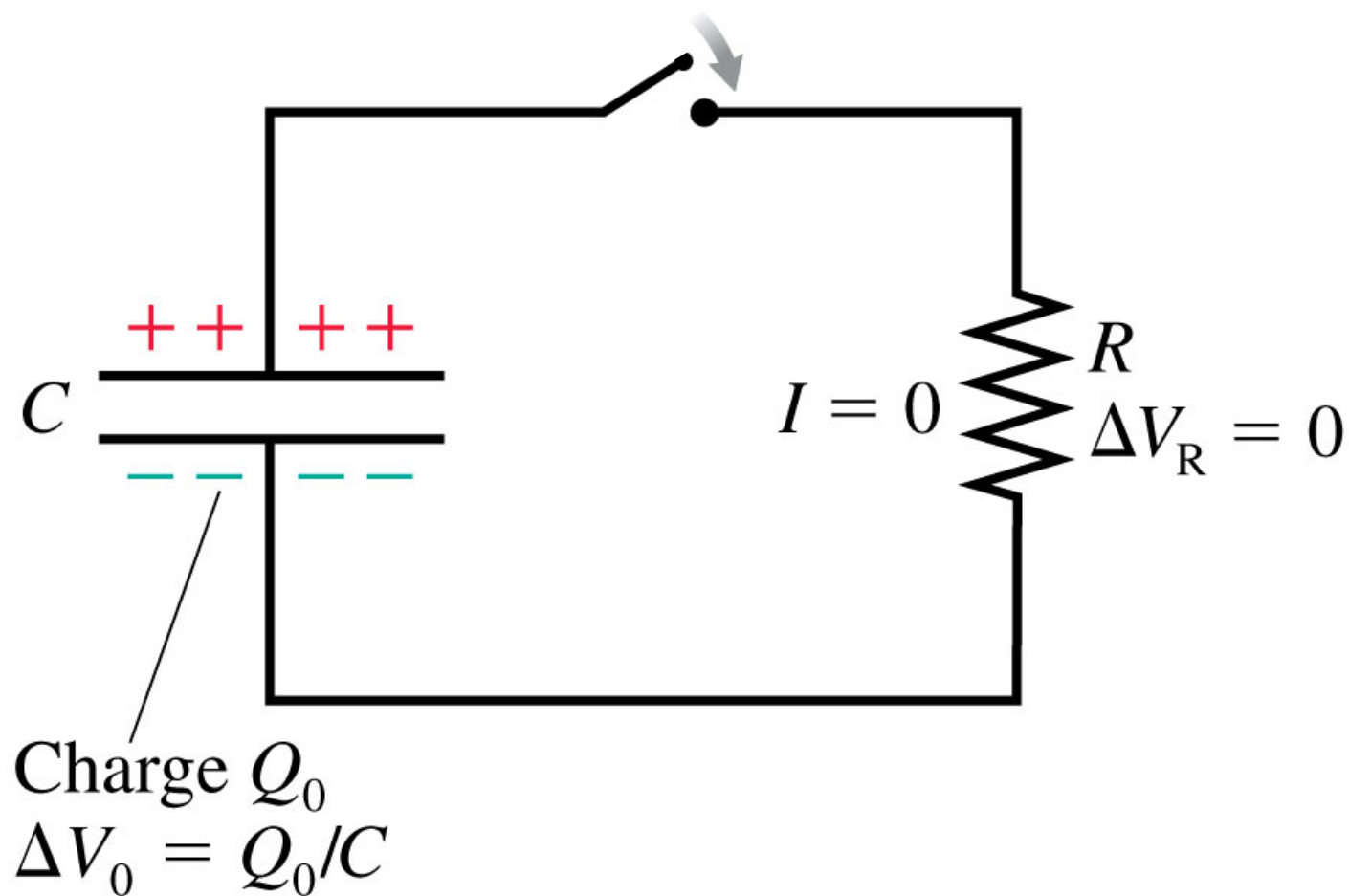- a) Gather all the variables with Q in them to one side.
- b) Integrate both sides.

The Math

Write down Kirchoff's loop rule for this circuit



$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$


$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$

- a) Gather all the variables with Q in them to one side.
- b) Integrate both sides.

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$

The Math

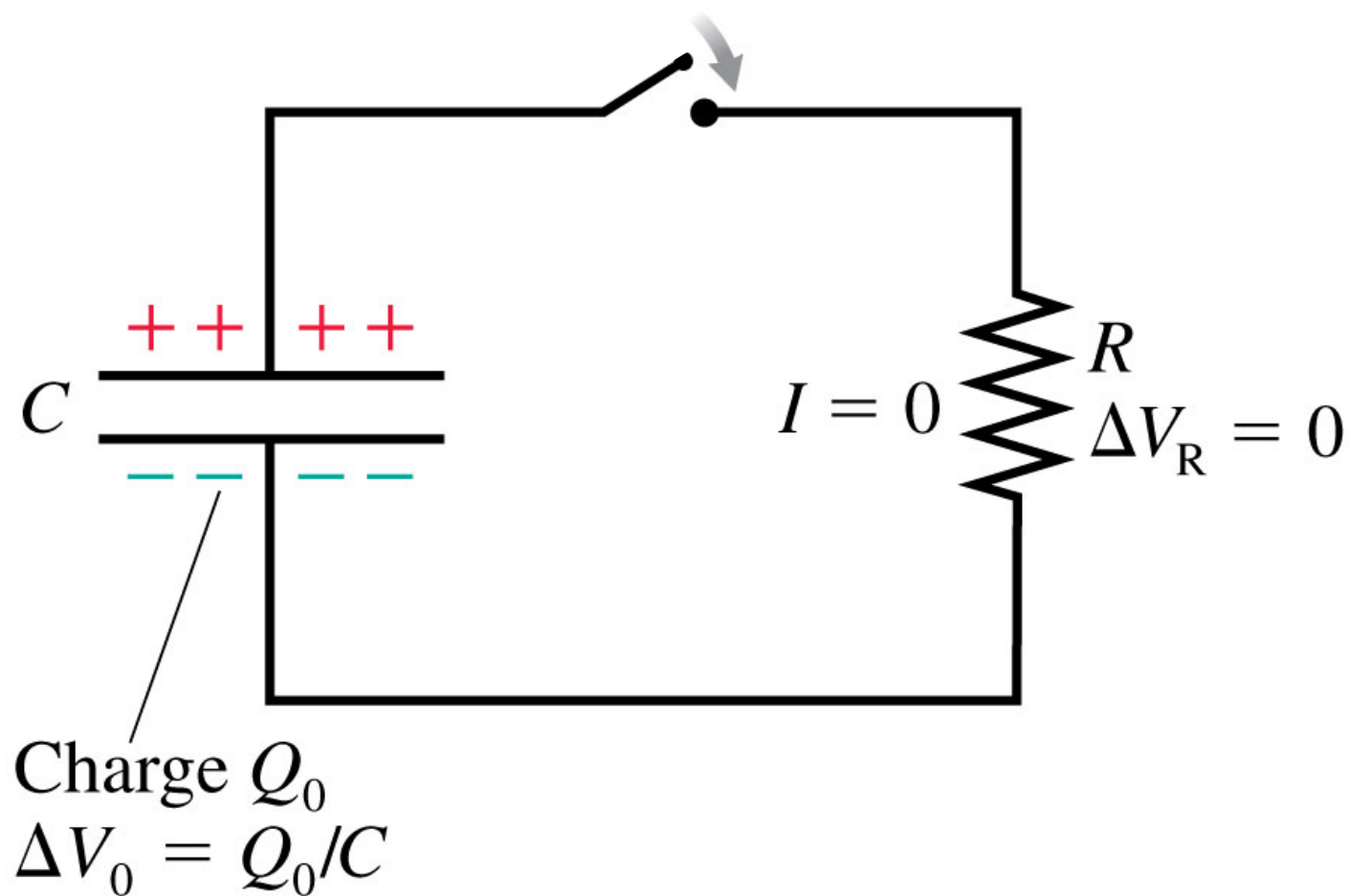Write down Kirchoff's loop rule for this circuit



$$\Delta V_{\text{cap}} + \Delta V_{\text{res}} = \frac{Q}{C} - IR = 0$$

$$I = -\frac{dQ}{dt}$$

$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$

- a) Gather all the variables with Q in them to one side.
- b) Integrate both sides.

$$Q = Q_0 e^{-t/\tau}$$


$$\tau = RC$$

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$

The Math

Write down Kirchoff's
loop rule for t
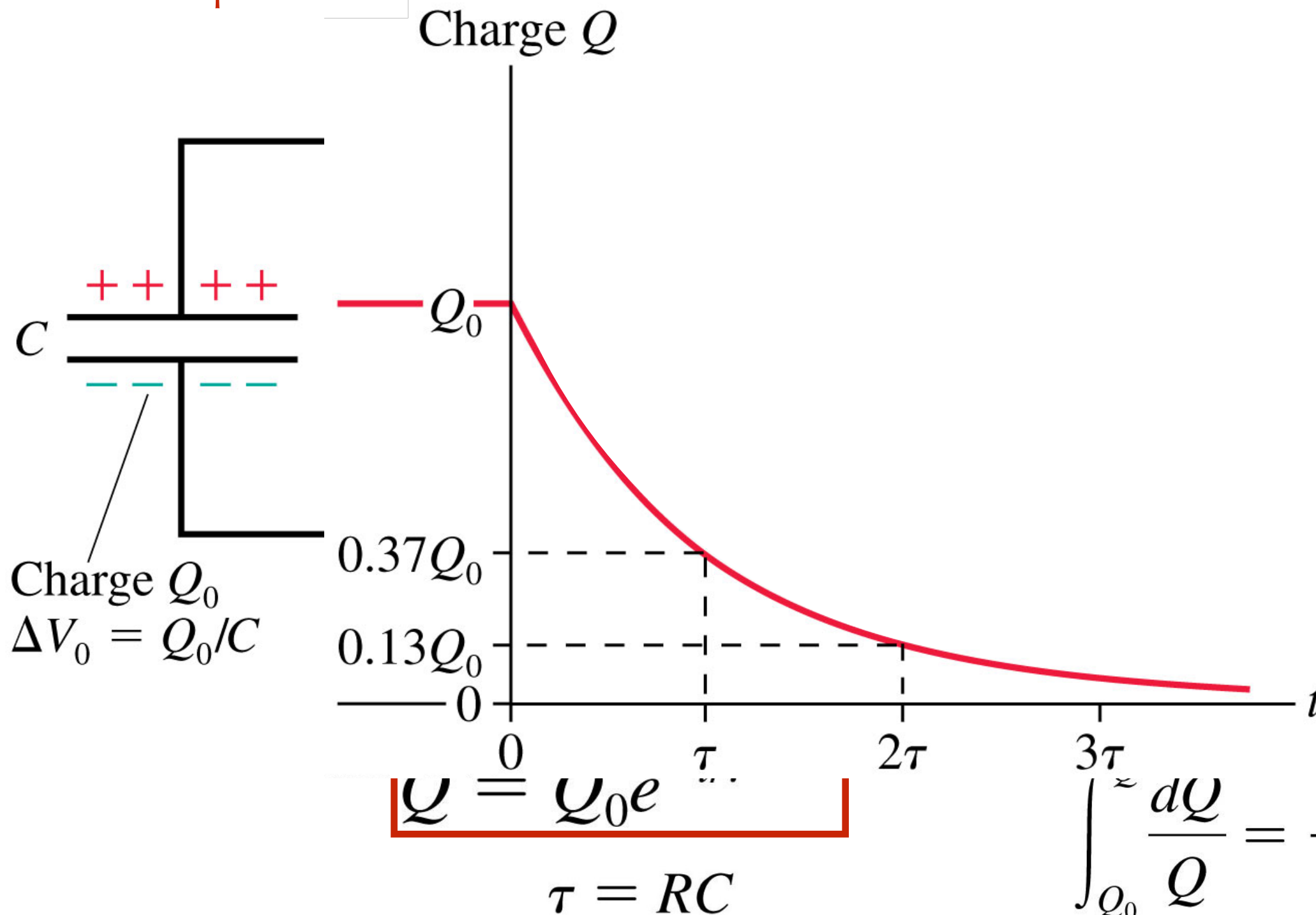
$$\Delta V + \Delta V = \frac{Q}{C} - IR = 0$$



$$\frac{dQ}{dt}$$


$$\frac{Q}{C} = 0$$

the
with Q in
re side.
both sides.

$$\int_{Q_0}^{\infty} \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$


Which capacitor discharges more quickly after the switch is closed?

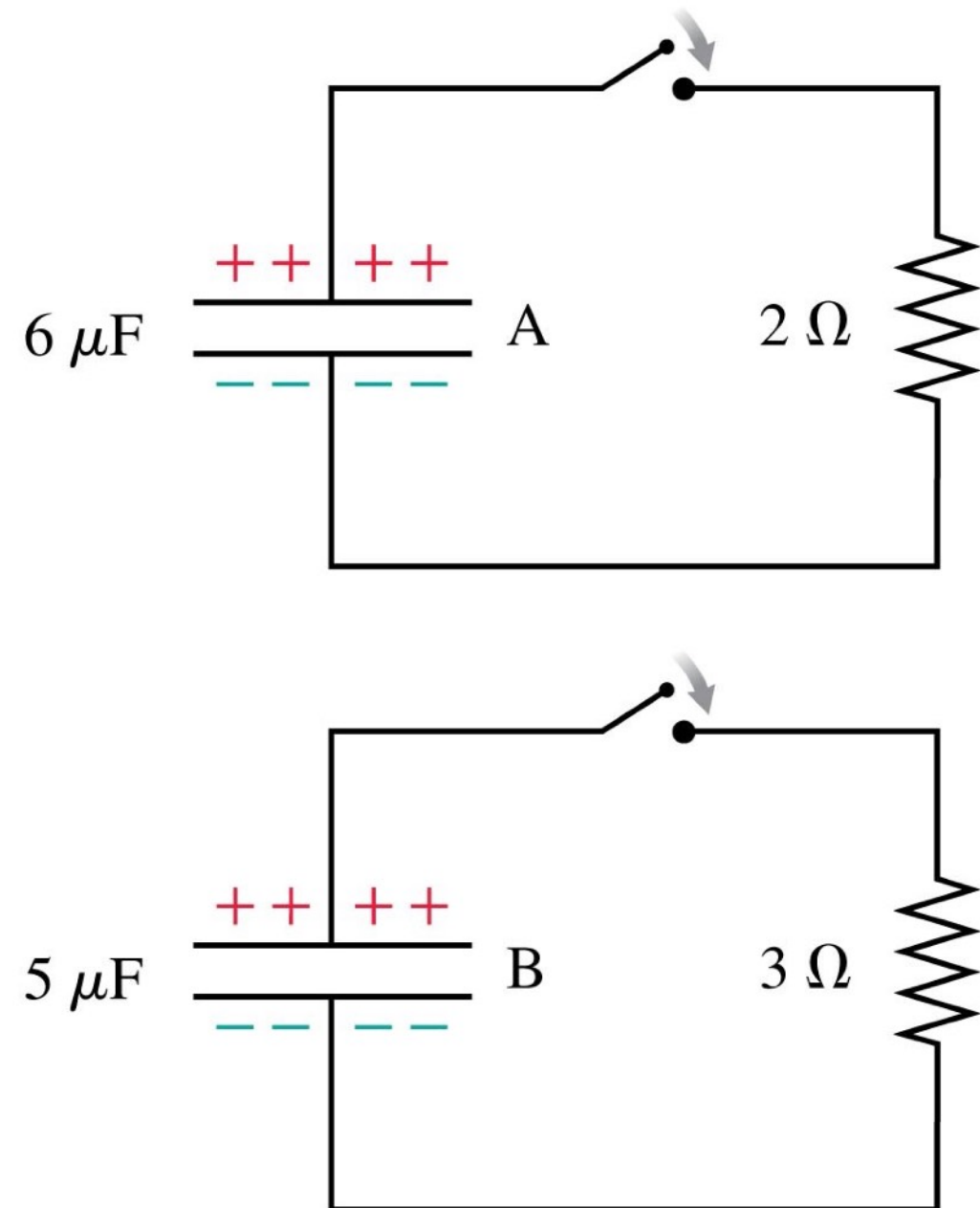- A. Capacitor A.
- B. Capacitor B.
- C. They discharge at the same rate.
- D. Can't say without knowing the initial amount of charge.




What is the time constant for this RC circuit

- a) 5 s b) 4 s c) 3s d) 2s e) 1s

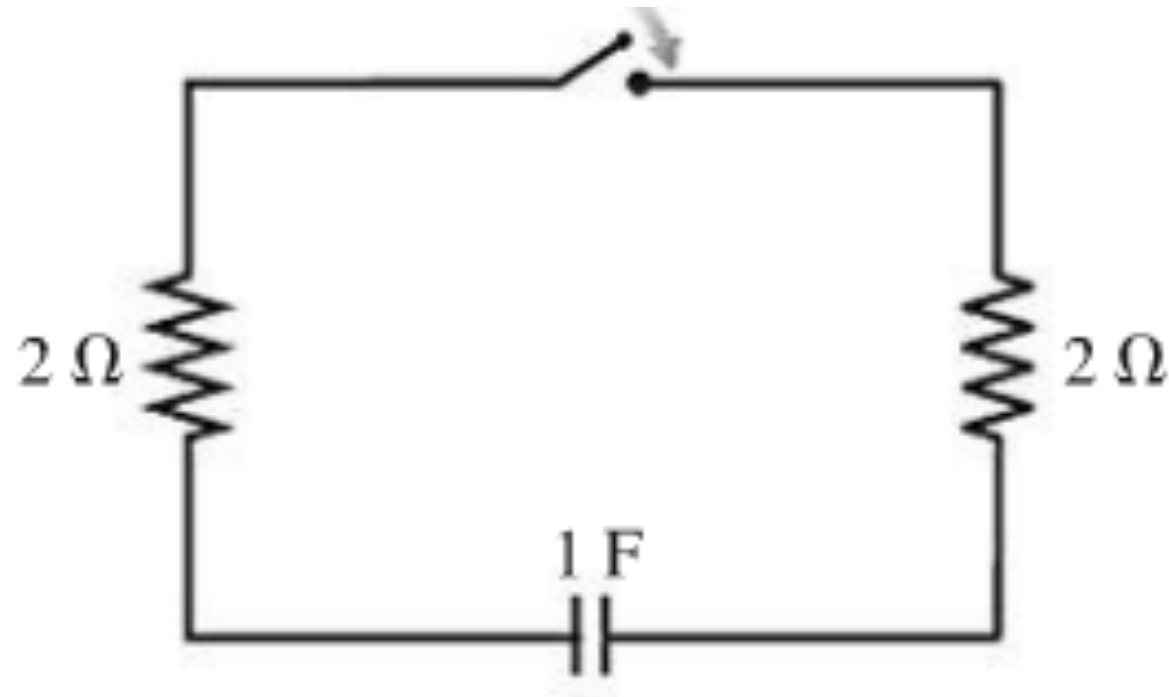

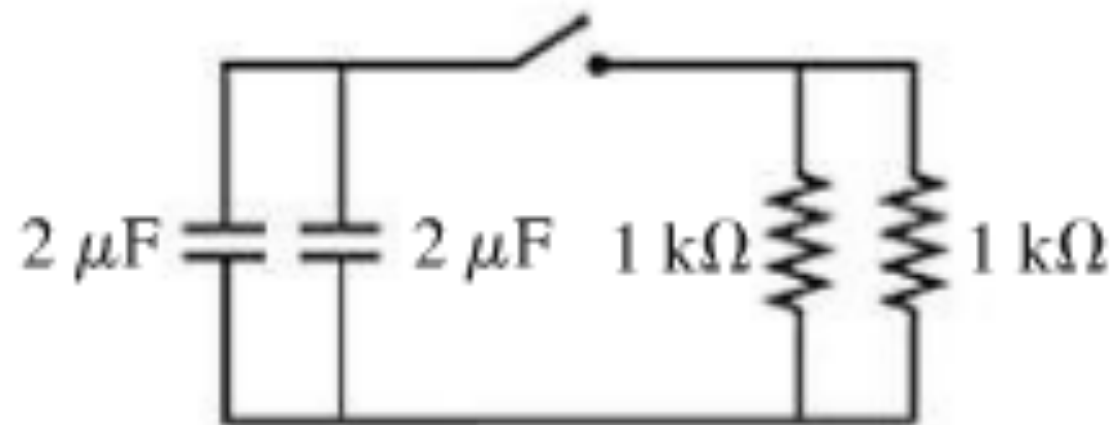What is the time constant for this RC circuit



$$Q = Q_0 e^{-t/\tau}$$

If the charge on the capacitor decays exponentially, how does the voltage on the capacitor vary with time?

$$Q = Q_0 e^{-t/\tau}$$

If the charge on the capacitor decays exponentially, how does the voltage on the capacitor vary with time?

$$\Delta V_C = \Delta V_0 e^{-t/\tau}$$

$$Q = Q_0 e^{-t/\tau}$$

If the charge on the capacitor decays exponentially, how does the voltage on the capacitor vary with time?

$$\Delta V_C = \Delta V_0 e^{-t/\tau}$$

What about the current through the resistor?

You'll need to do some math!

$$Q = Q_0 e^{-t/\tau}$$

If the charge on the capacitor decays exponentially, how does the voltage on the capacitor vary with time?


$$\Delta V_C = \Delta V_0 e^{-t/\tau}$$

What about the current through the resistor? You'll need to do some math!


$$I = -\frac{dQ}{dt} = \frac{Q_0}{\tau} e^{-t/\tau} = \frac{Q_0}{RC} e^{-t/\tau} = \frac{\Delta V_0}{R} e^{-t/\tau} = I_0 e^{-t/\tau}$$

The capacitor is initially uncharged.
Immediately after the switch closes,
the capacitor voltage is


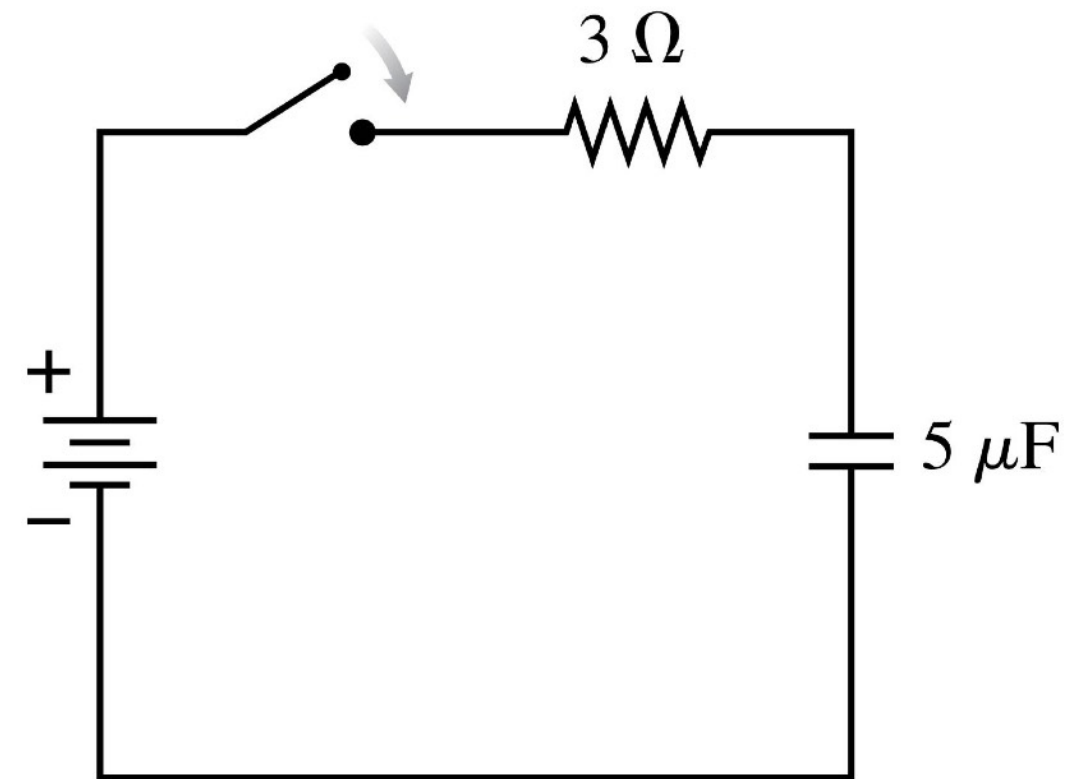
- A. 0 V.
- B. Somewhere between 0 V and 6 V.
- C. 6 V.
- D. Undefined.



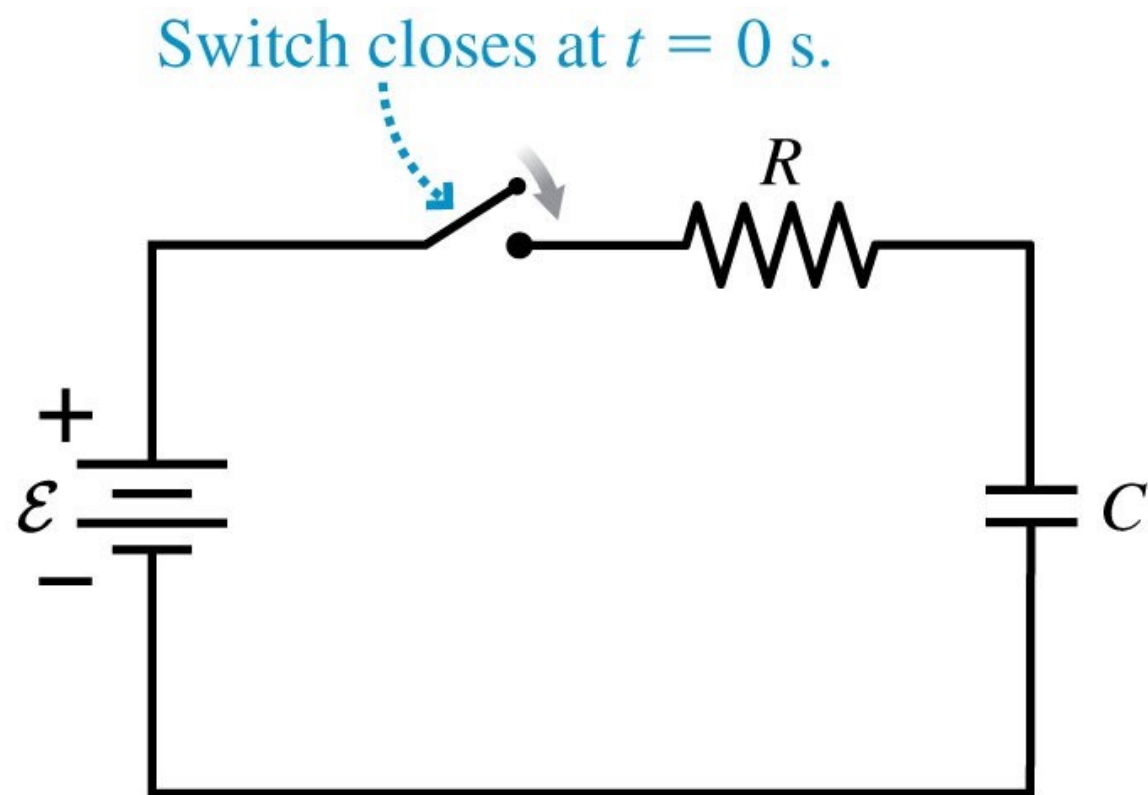Without looking in your book, draw the Q vs. t curve for the capacitor.



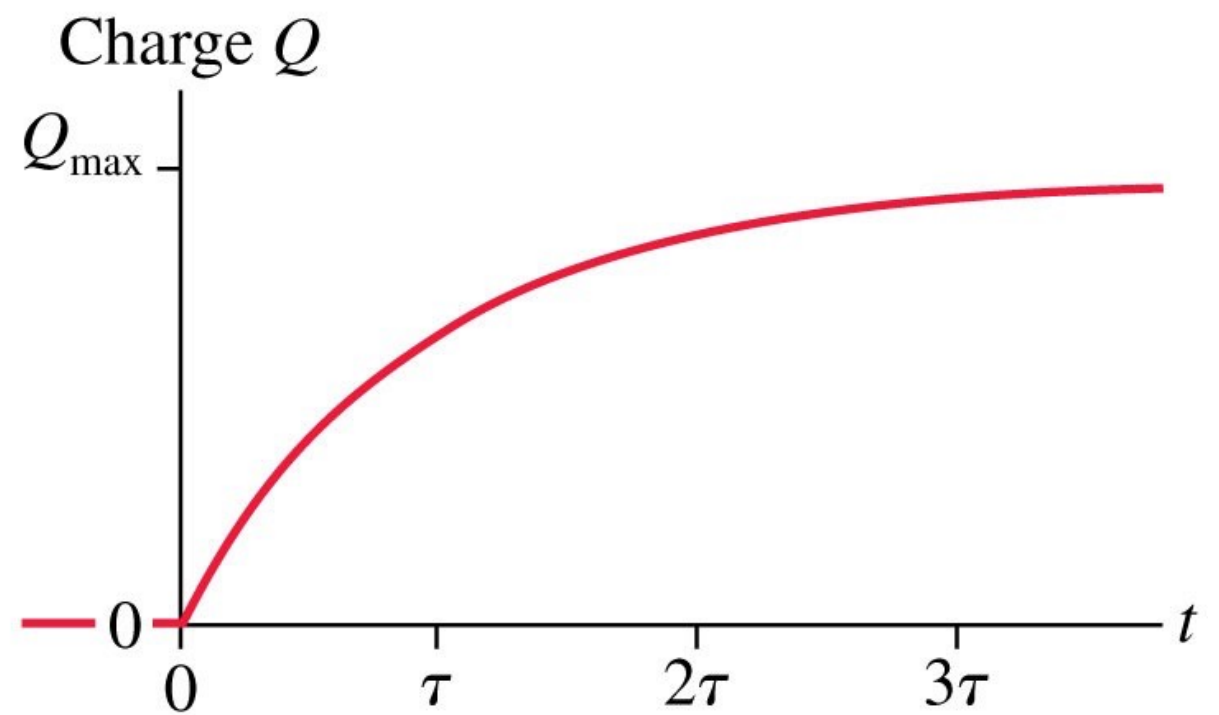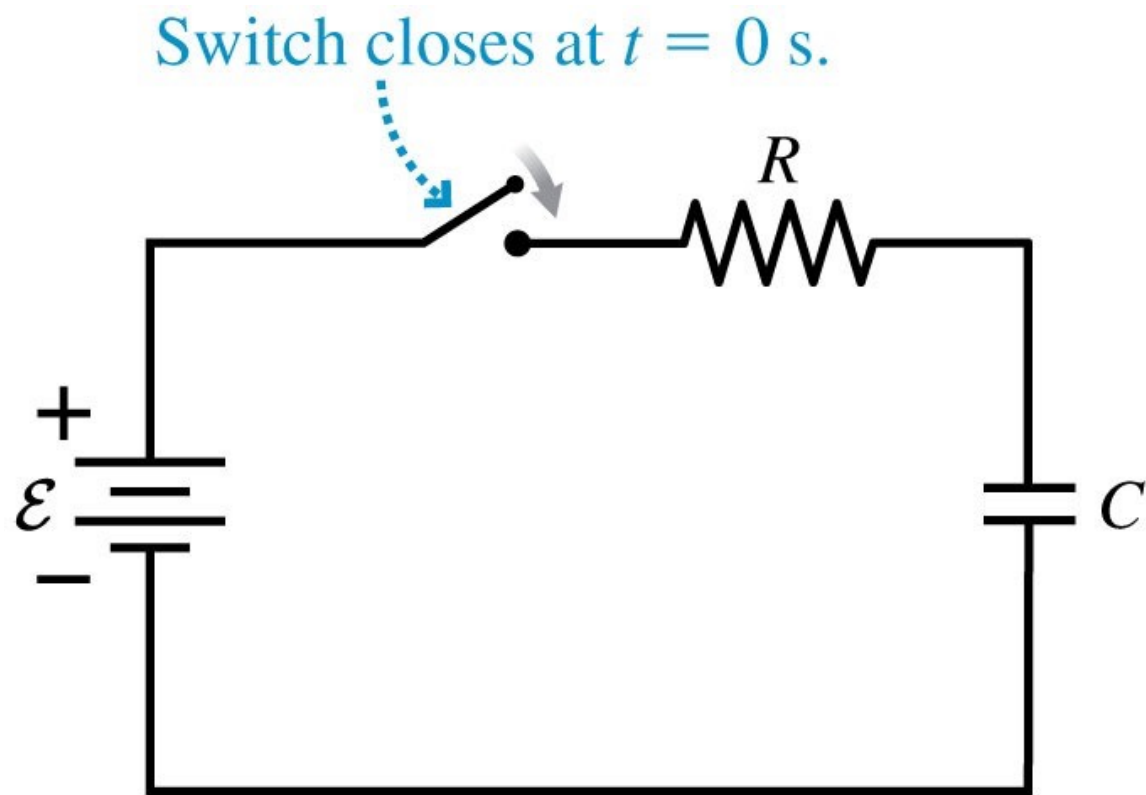
Without looking in your book, draw the Q vs. t curve for the capacitor.



The Math

Write down Kirchhoff's
loop rule for this circuit

Switch closes at $t = 0$ s.

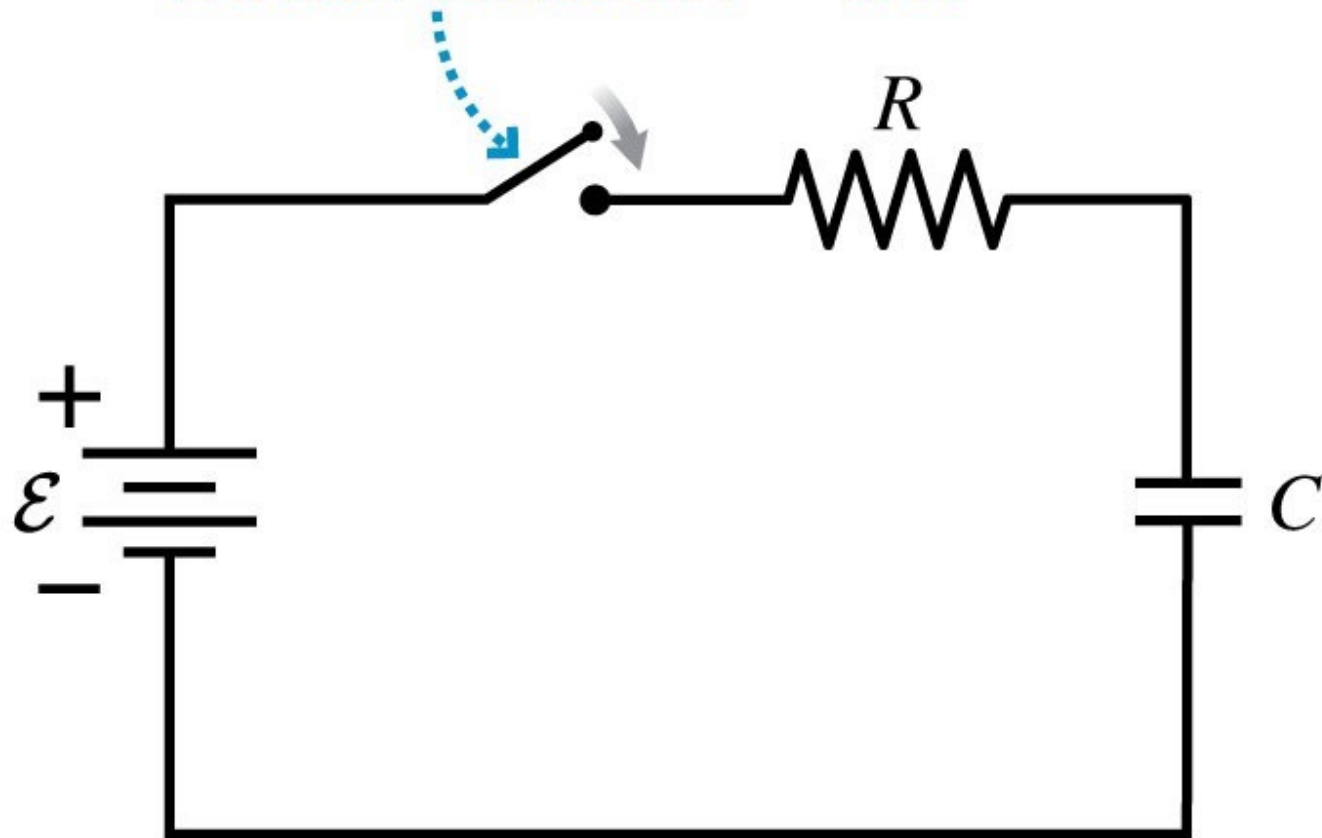


The Math

Write down Kirchhoff's
loop rule for this circuit

$$\epsilon - IR - \frac{q}{C} = 0$$


Switch closes at $t = 0$ s.

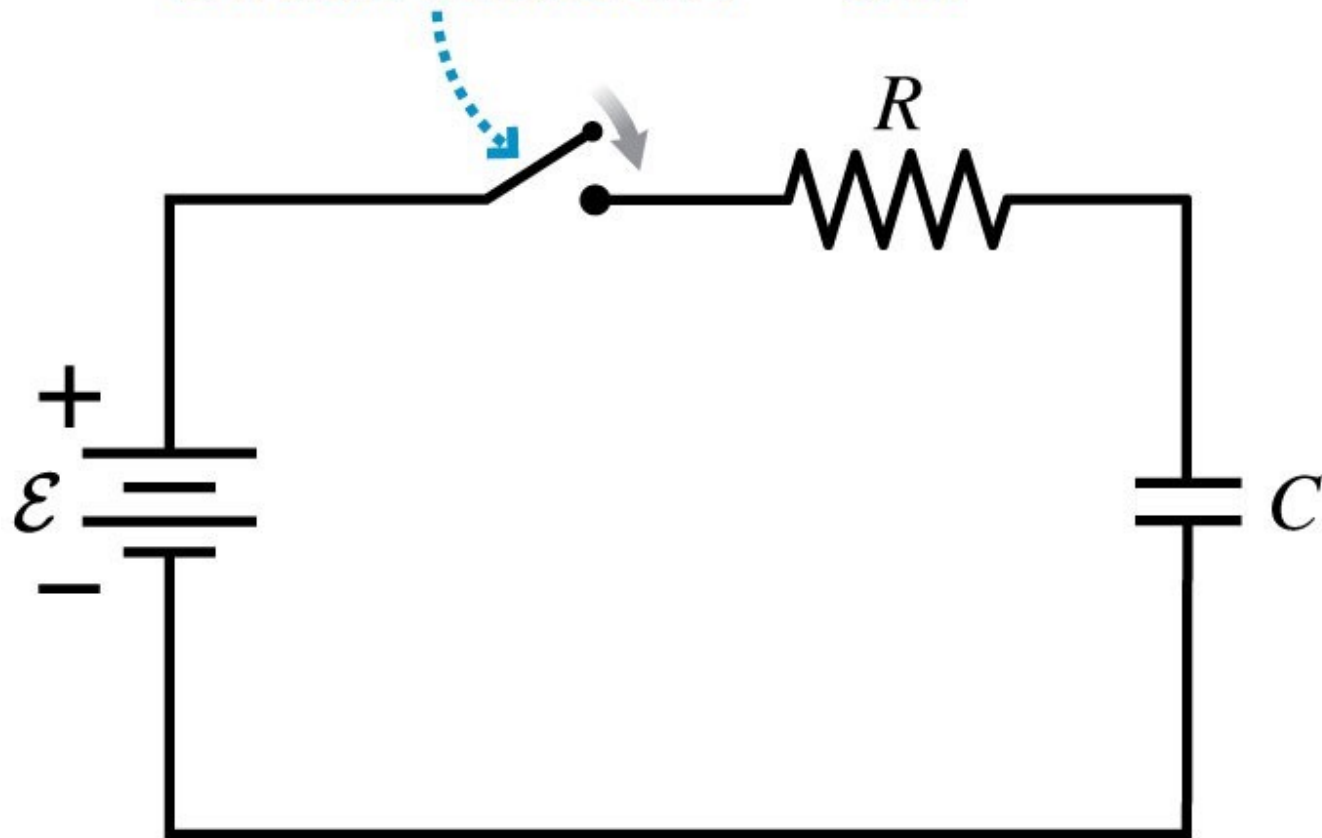

The Math

Write down Kirchhoff's
loop rule for this circuit

Switch closes at $t = 0$ s.

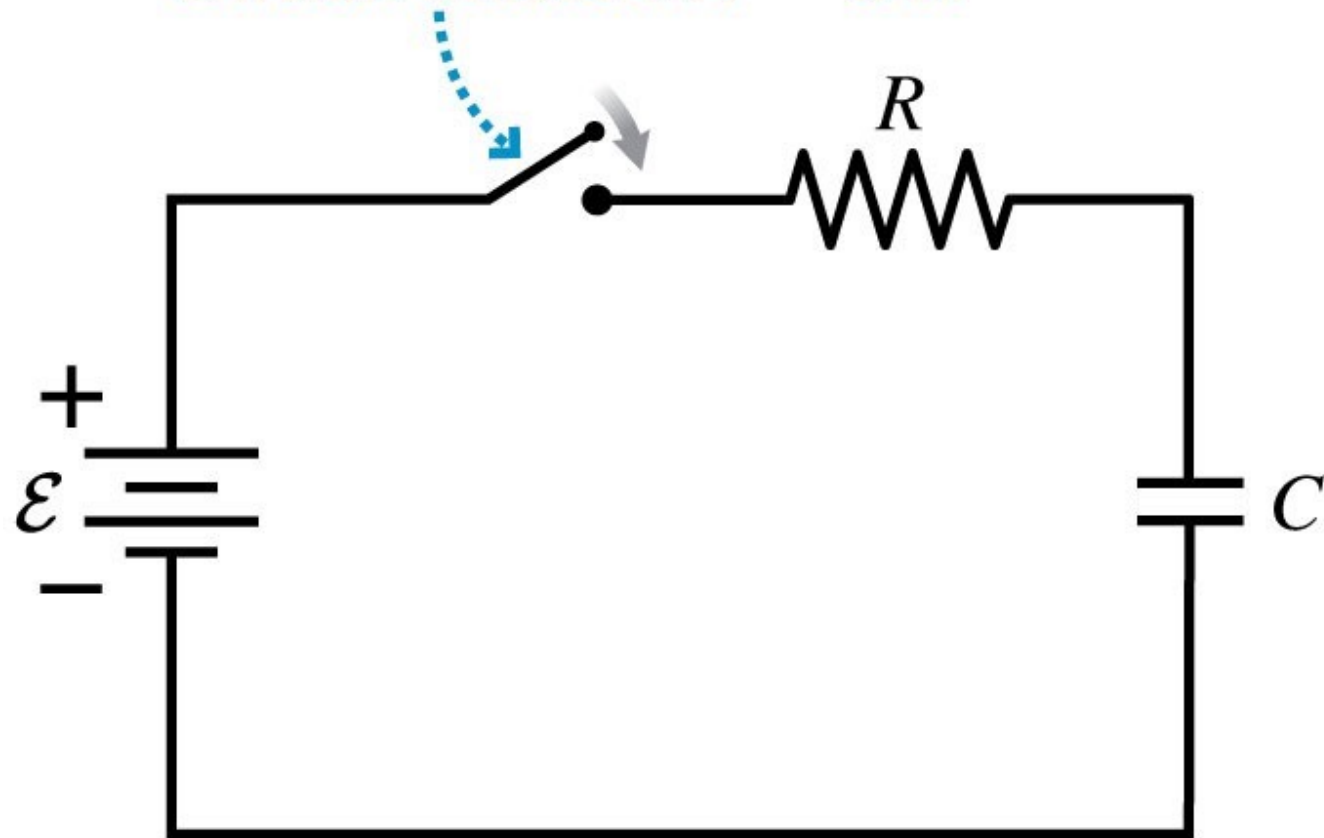


$$\mathcal{E} - IR - \frac{q}{C} = 0$$

$$I = \frac{dq}{dt}$$

The Math

Write down Kirchhoff's loop rule for this circuit

Switch closes at $t = 0$ s.

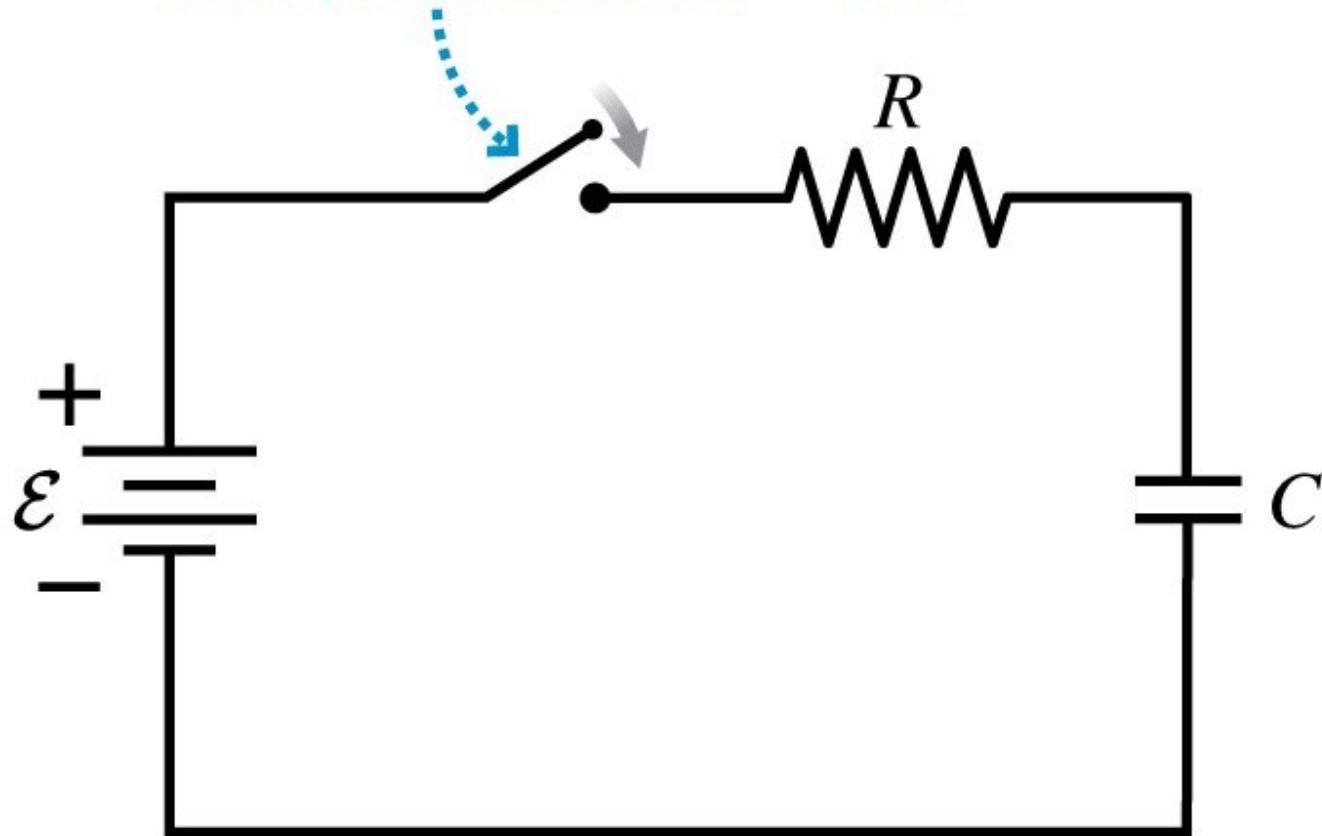

$$\mathcal{E} - IR - \frac{q}{C} = 0$$


$$I = \frac{dq}{dt}$$

$$\mathcal{E} - \frac{dq}{dt}R - \frac{q}{C} = 0$$

The Math

Write down Kirchhoff's loop rule for this circuit

Switch closes at $t = 0$ s.

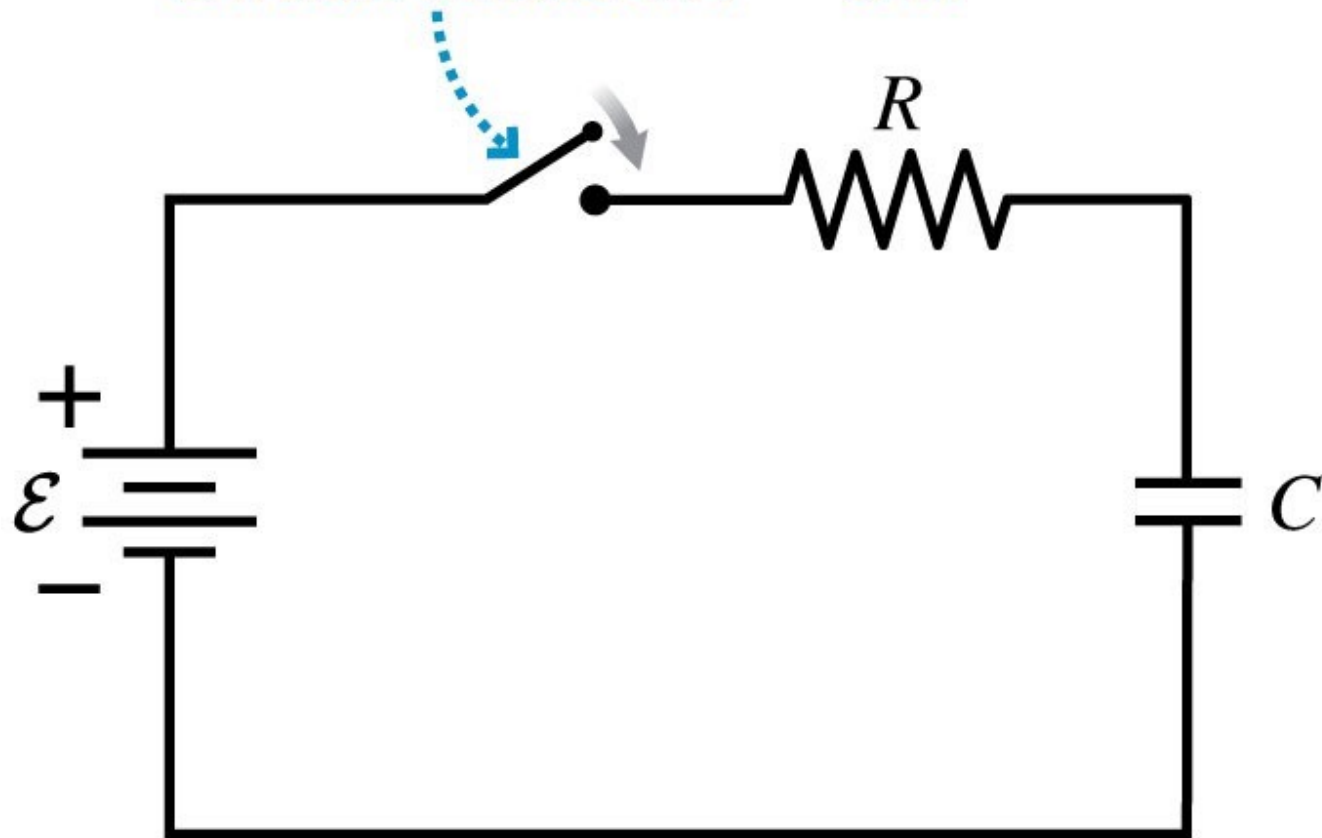

$$\mathcal{E} - IR - \frac{q}{C} = 0$$

$$I = \frac{dq}{dt}$$


$$\mathcal{E} - \frac{dq}{dt}R - \frac{q}{C} = 0$$

- a) Gather all the variables with Q in them to one side.
- b) Integrate both sides.

The Math

Write down Kirchhoff's loop rule for this circuit

Switch closes at $t = 0$ s.

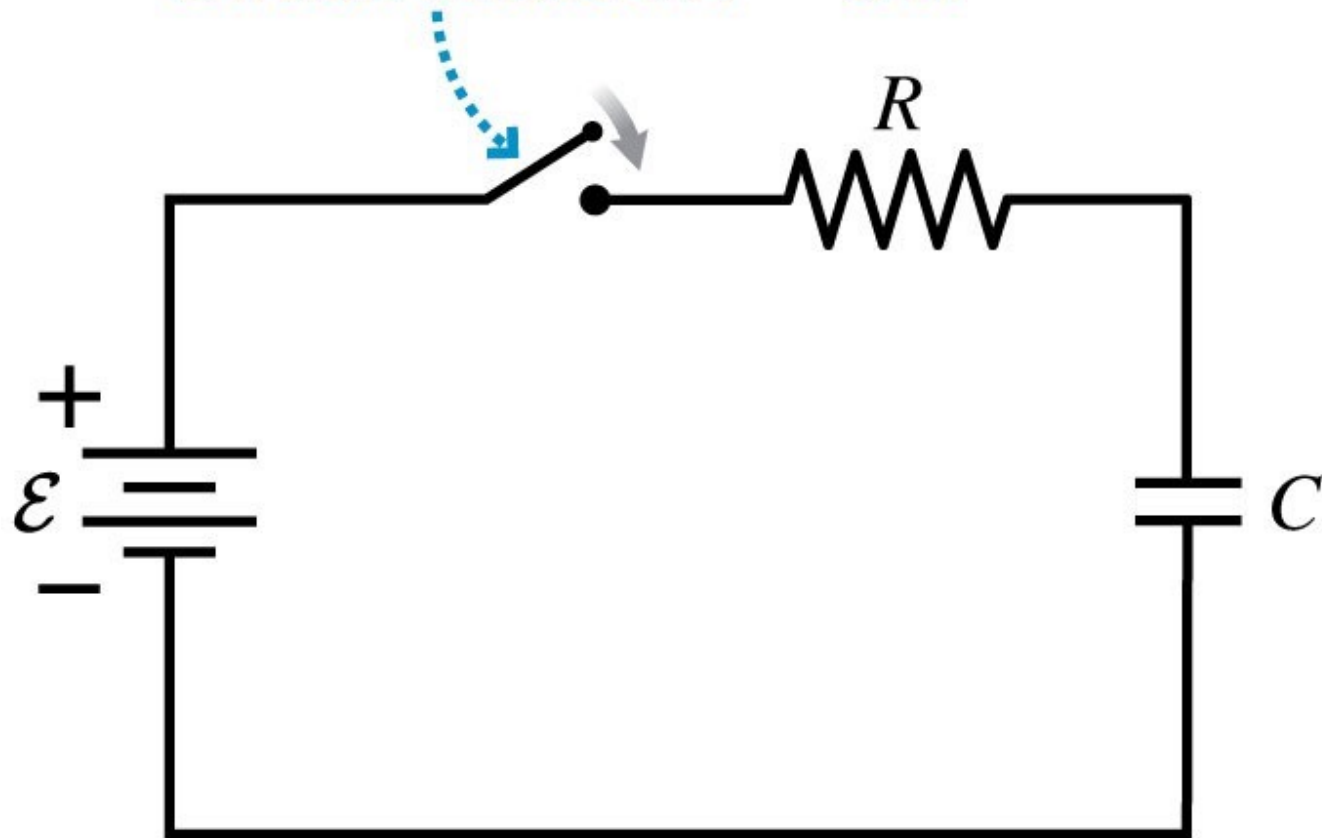

$$\epsilon - IR - \frac{q}{C} = 0$$

$$I = \frac{dq}{dt}$$

$$\epsilon - \frac{dq}{dt}R - \frac{q}{C} = 0$$


- a) Gather all the variables with Q in them to one side.
- b) Integrate both sides.

$$\int_0^Q \frac{dq}{\epsilon C - q} = \int_0^t \frac{dt}{RC}$$

The Math

Write down Kirchhoff's loop rule for this circuit

Switch closes at $t = 0$ s.

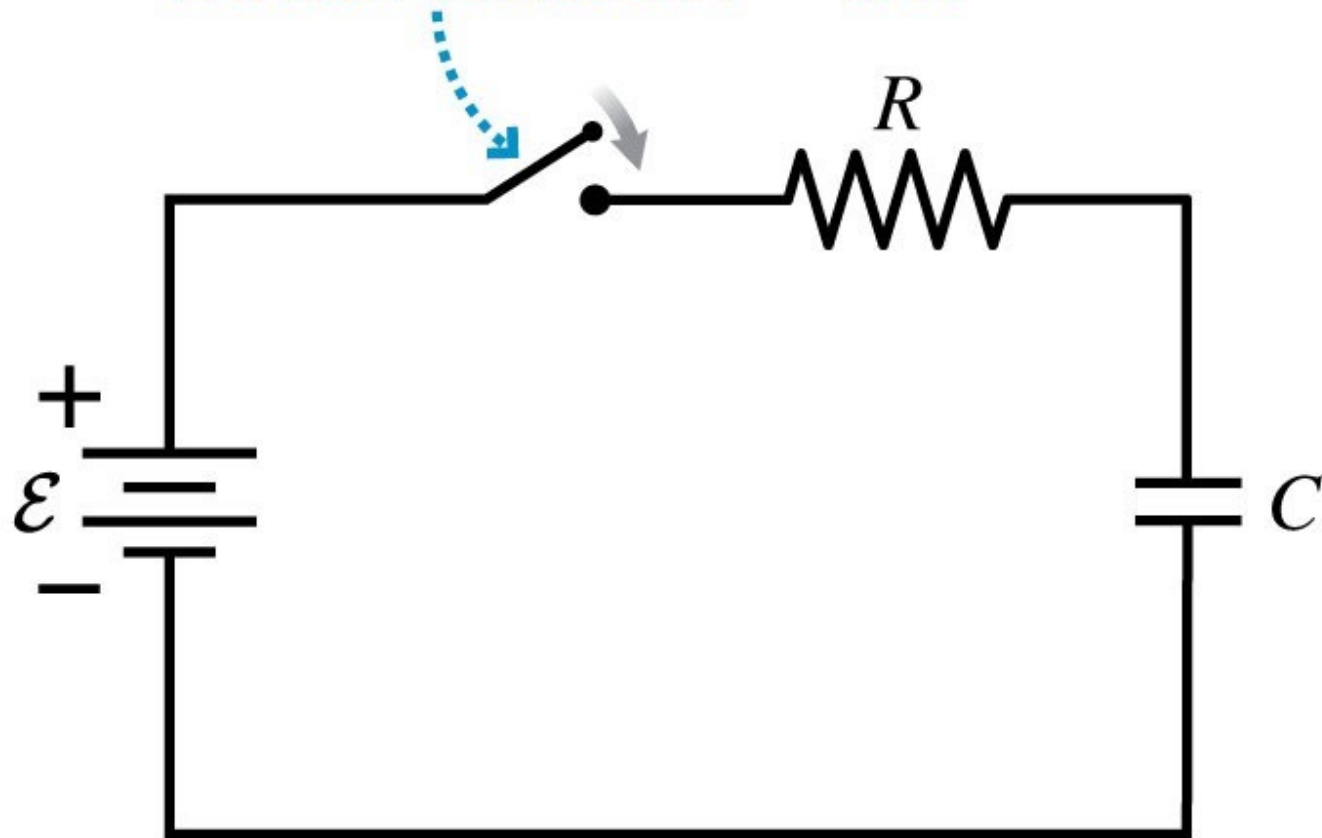

$$\epsilon - IR - \frac{q}{C} = 0$$

$$I = \frac{dq}{dt}$$

$$\epsilon - \frac{dq}{dt}R - \frac{q}{C} = 0$$

- a) Gather all the variables with Q in them to one side.
- b) Integrate both sides.

$$Q = Q_{\max}(1 - e^{-t/\tau})$$


$$\tau = RC$$

$$\int_0^Q \frac{dq}{\epsilon C - q} = \int_0^t \frac{dt}{RC}$$

The Math

Write down Kirchoff's

$$\epsilon - IR - \frac{q}{C} = 0$$

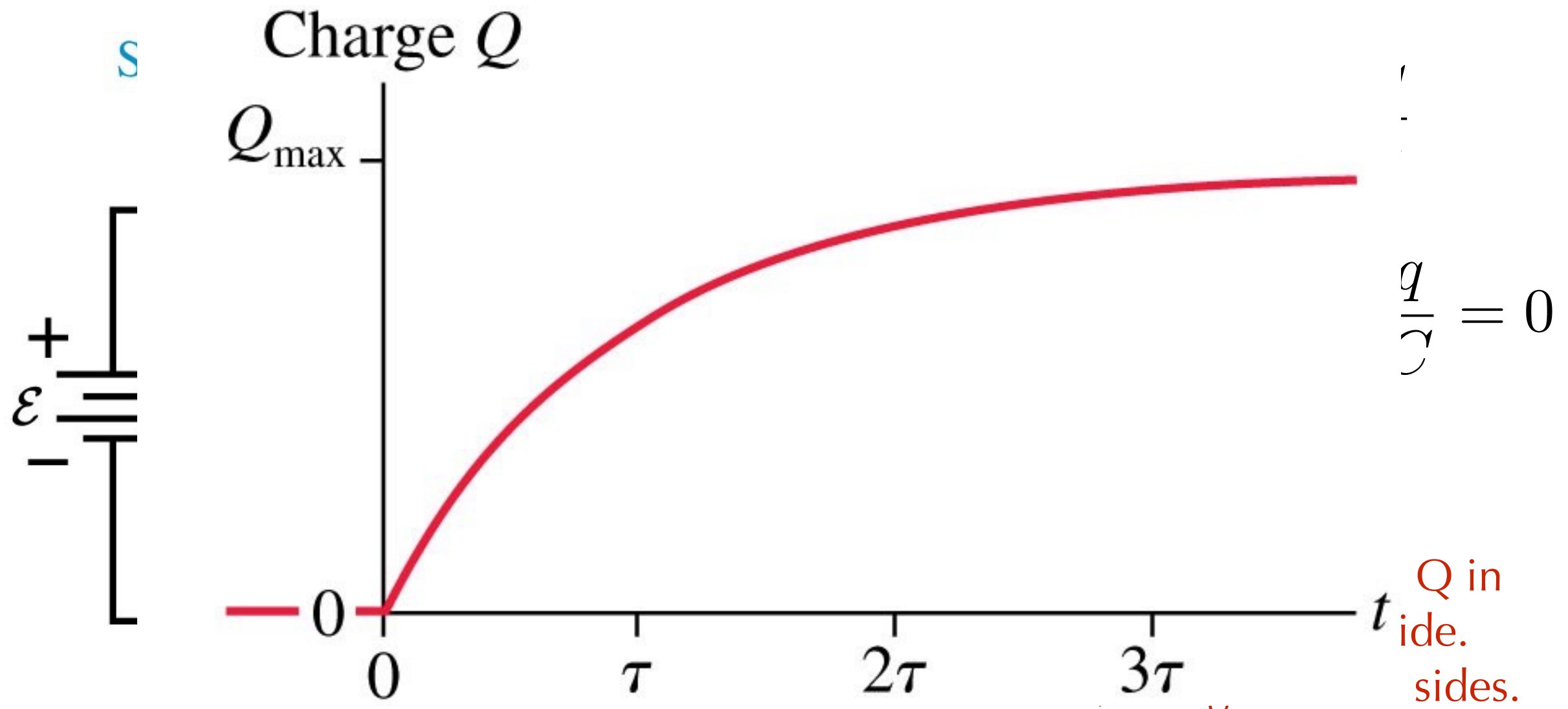

$$Q = Q_{\max}(1 - e^{-t/\tau})$$

$$\tau = RC$$

$$\int_0^Q \frac{dq}{\epsilon C - q} = \int_0^t \frac{dt}{RC}$$

The capacitor is initially unchanged.
Immediately after the switch closes,
the capacitor voltage is

- A. 0 V.
- B. Somewhere between 0 V and 6 V.
- C. 6 V.
- D. Undefined.

