



PH 220

Lance Nelson

Important for today

Remember:

- Try to minimize time when I am imparting information and maximize the time when the student is explaining, thinking and doing.
- Ensure that every slide has a clearly-defined purpose.
- Ask concise, well thought-out, and thought-provoking questions that cause the student to ponder and ask why.
- Give the student time to ponder silently, ask their neighbor questions and receive instruction from them.

Outcomes

What is a phasor? Difference between instantaneous value and peak value. Rotating phasor illustrates concept of oscillating currents and voltages.

-AC resistor circuit

Summary

State in words and in math, the meaning of these laws.

Gauss's Law

Gauss's Law for magnetism

Faraday's Law

Ampere-Maxwell

Lorentz force law

Summary

State in words and in math, the meaning of these laws.

$$(\Phi_e)_{\text{closed surface}} = \oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{in}}}{\epsilon_0}$$

Gauss's Law

Gauss's Law for magnetism

Faraday's Law

Ampere-Maxwell

Lorentz force law

Summary

State in words and in math, the meaning of these laws.

$$(\Phi_e)_{\text{closed surface}} = \oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{in}}}{\epsilon_0}$$

Gauss's Law

$$(\Phi_m)_{\text{closed surface}} = \oint \vec{B} \cdot d\vec{A} = 0$$

Gauss's Law for magnetism

$$\mathcal{E} = \oint \vec{E} \cdot d\vec{s} = -\frac{d\Phi_m}{dt}$$

Faraday's Law

Ampere-Maxwell

Lorentz force law

Summary

State in words and in math, the meaning of these laws.

$$(\Phi_e)_{\text{closed surface}} = \oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{in}}}{\epsilon_0}$$

Gauss's Law

$$(\Phi_m)_{\text{closed surface}} = \oint \vec{B} \cdot d\vec{A} = 0$$

Gauss's Law for magnetism

$$\mathcal{E} = \oint \vec{E} \cdot d\vec{s} = -\frac{d\Phi_m}{dt}$$

Faraday's Law

$$\oint \vec{B} \cdot d\vec{s} = \mu_0 \left(I_{\text{through}} + \epsilon_0 \frac{d\Phi_E}{dt} \right)$$

Ampere-Maxwell

Lorentz force law

Summary

State in words and in math, the meaning of these laws.

$$(\Phi_e)_{\text{closed surface}} = \oint \vec{E} \cdot d\vec{A} = \frac{Q_{\text{in}}}{\epsilon_0}$$

Gauss's Law

$$(\Phi_m)_{\text{closed surface}} = \oint \vec{B} \cdot d\vec{A} = 0$$

Gauss's Law for magnetism

$$\mathcal{E} = \oint \vec{E} \cdot d\vec{s} = -\frac{d\Phi_m}{dt}$$

Faraday's Law



$$\oint \vec{B} \cdot d\vec{s} = \mu_0 \left(I_{\text{through}} + \epsilon_0 \frac{d\Phi_E}{dt} \right)$$

Ampere-Maxwell

$$\vec{F} = q(\vec{E} + \vec{v} \times \vec{B})$$


Lorentz force law


AC sources

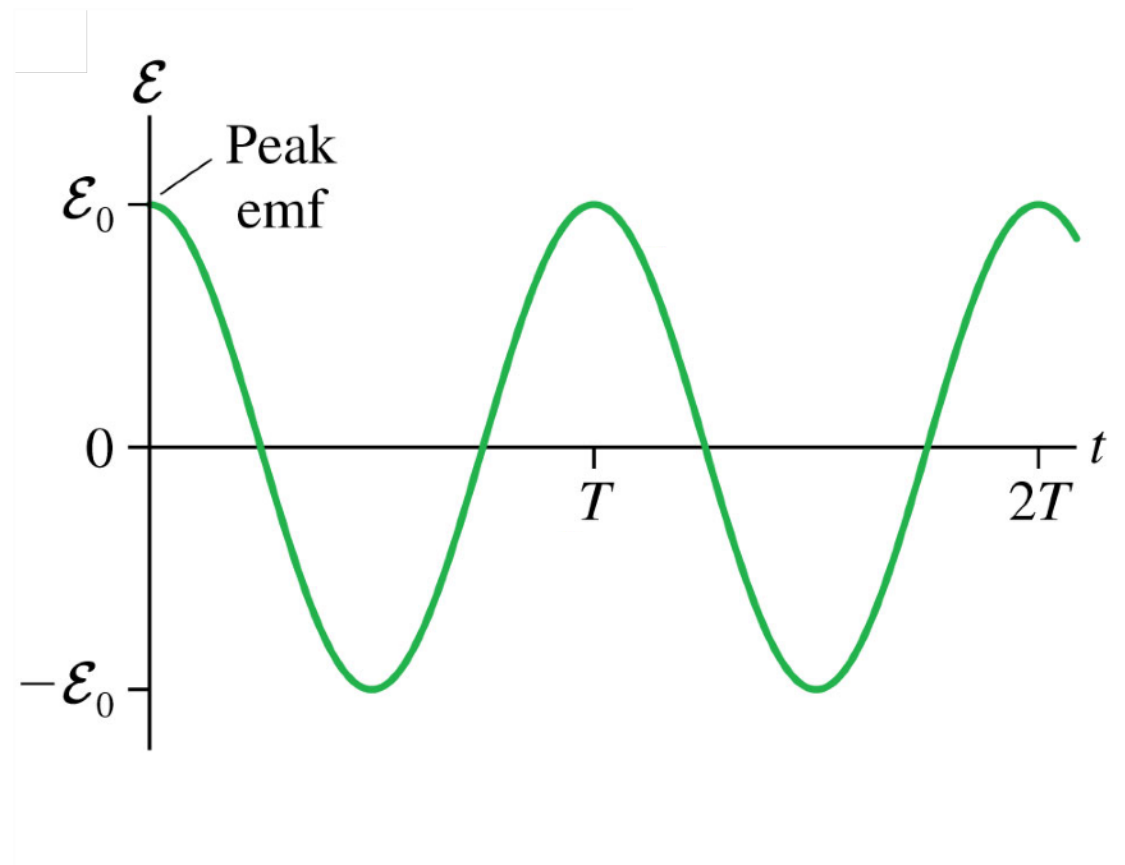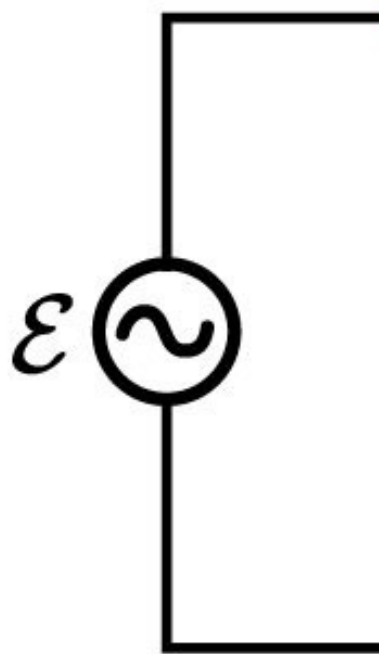



$$\mathcal{E} = \mathcal{E}_0 \cos \omega t$$


Phasors: Not something from Star Trek

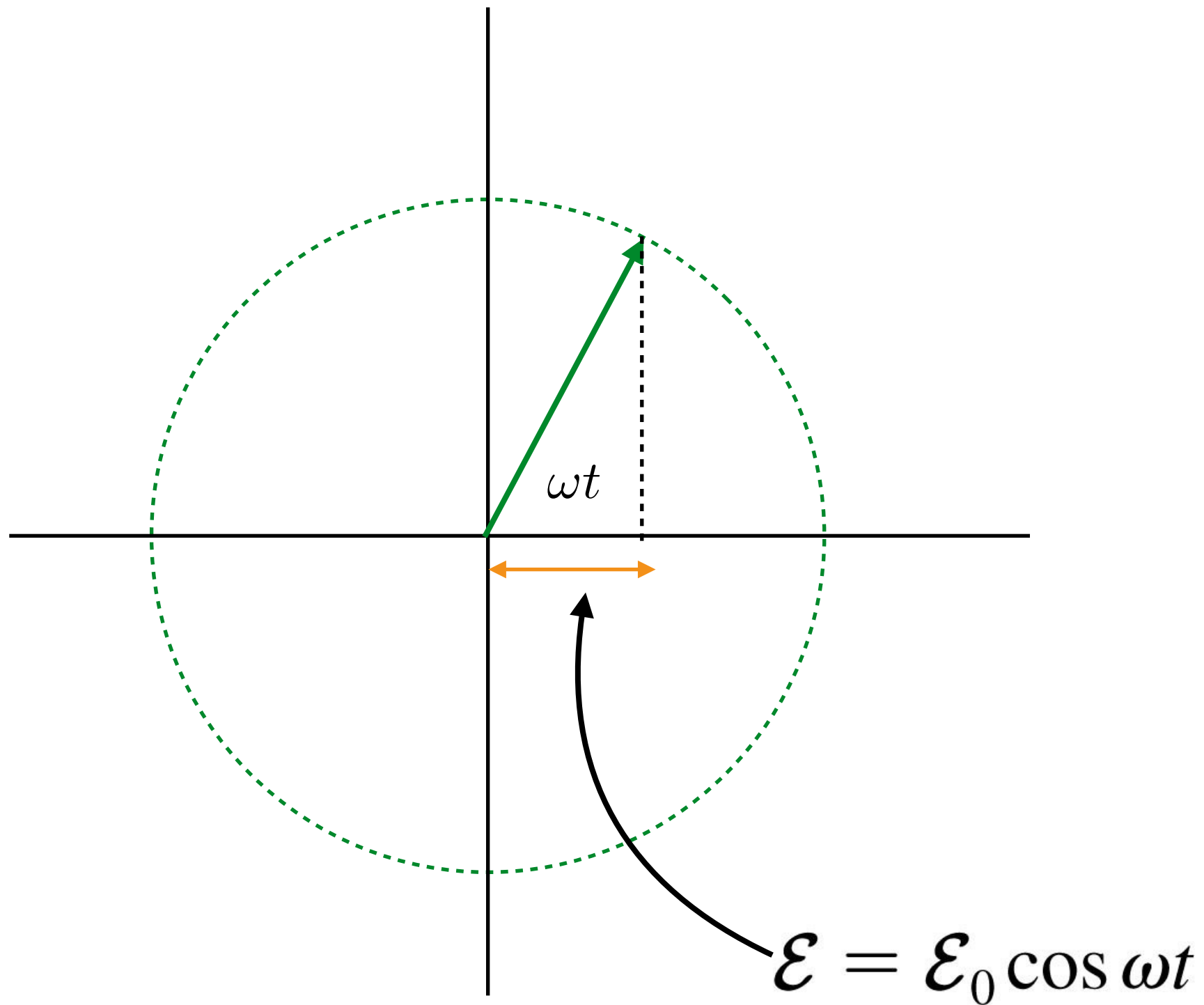


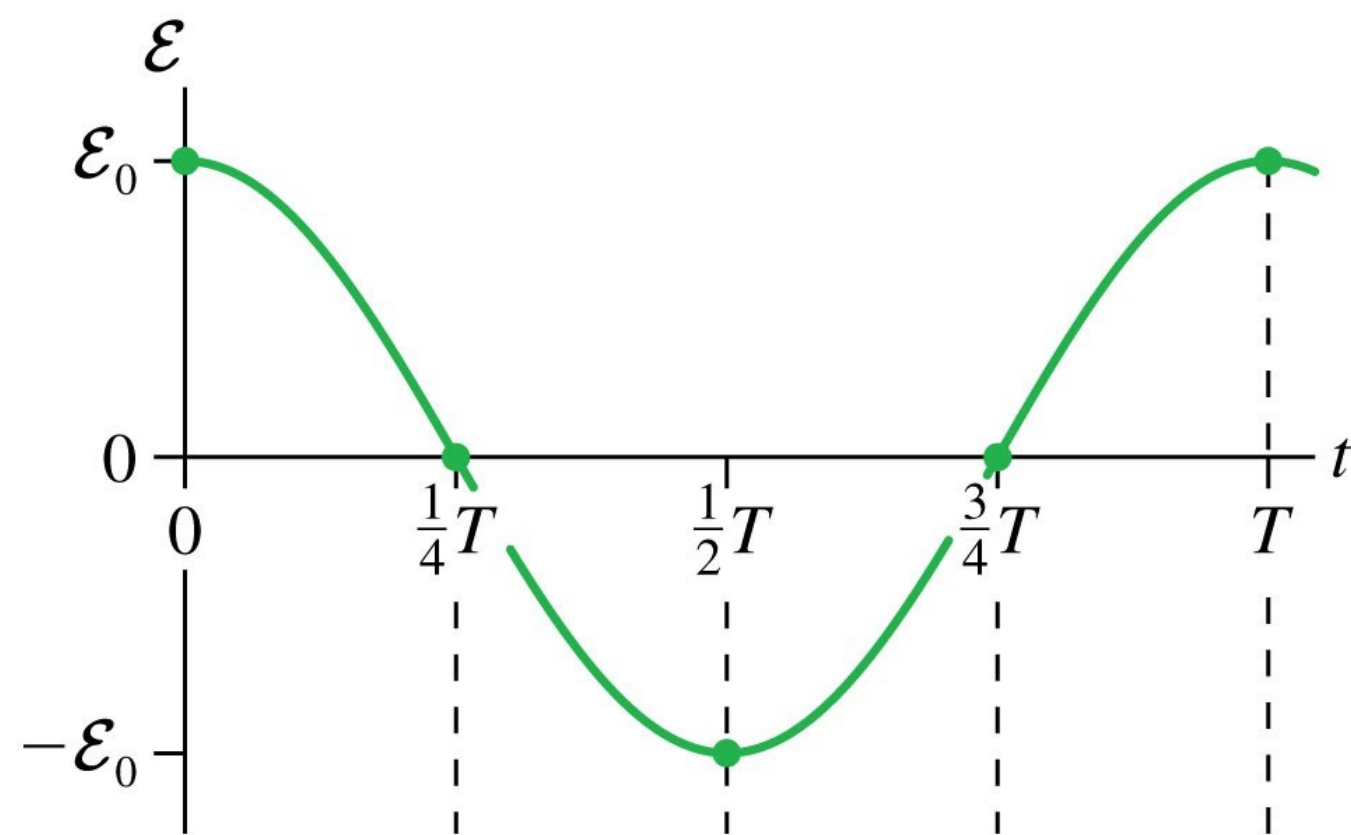


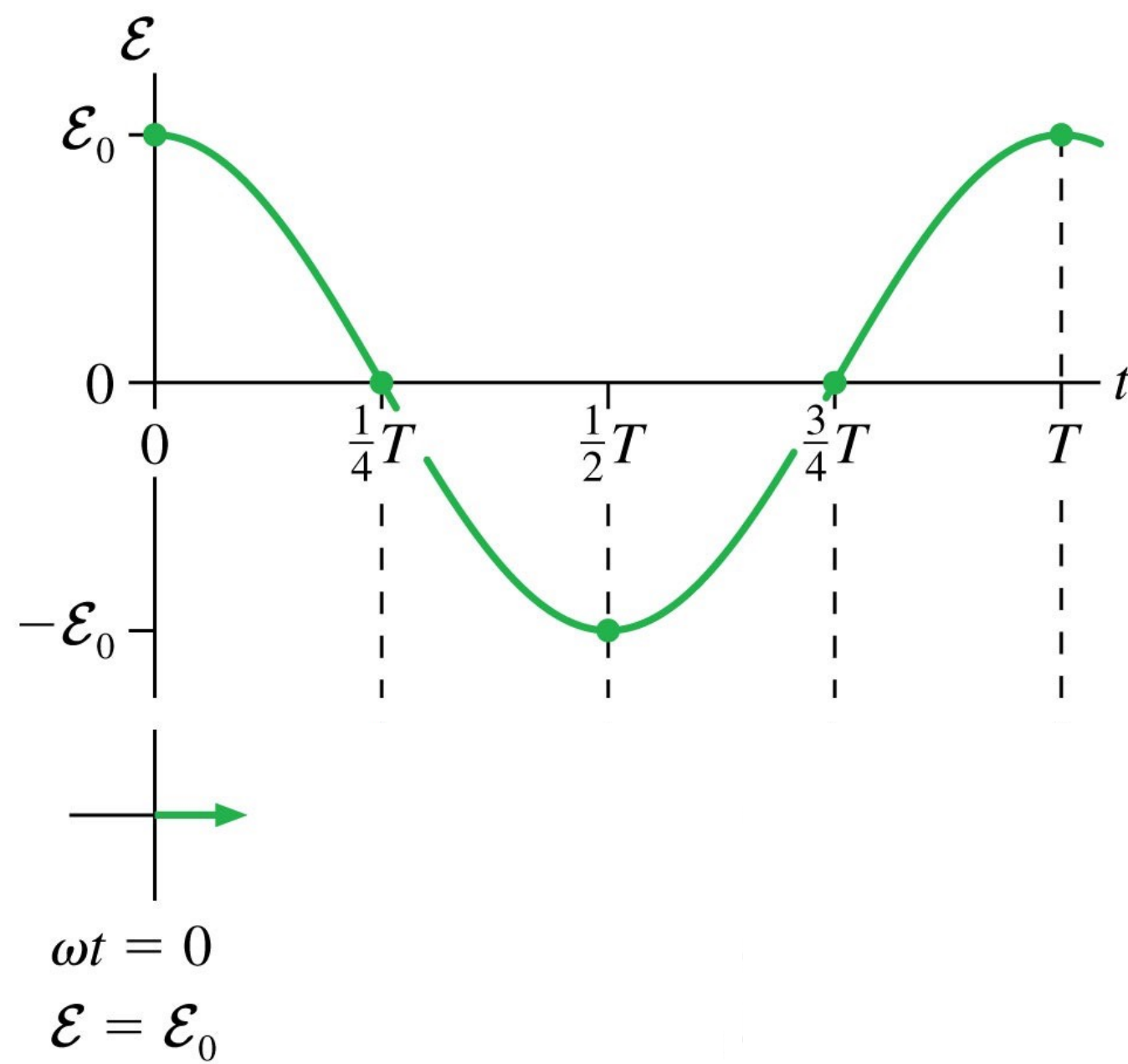

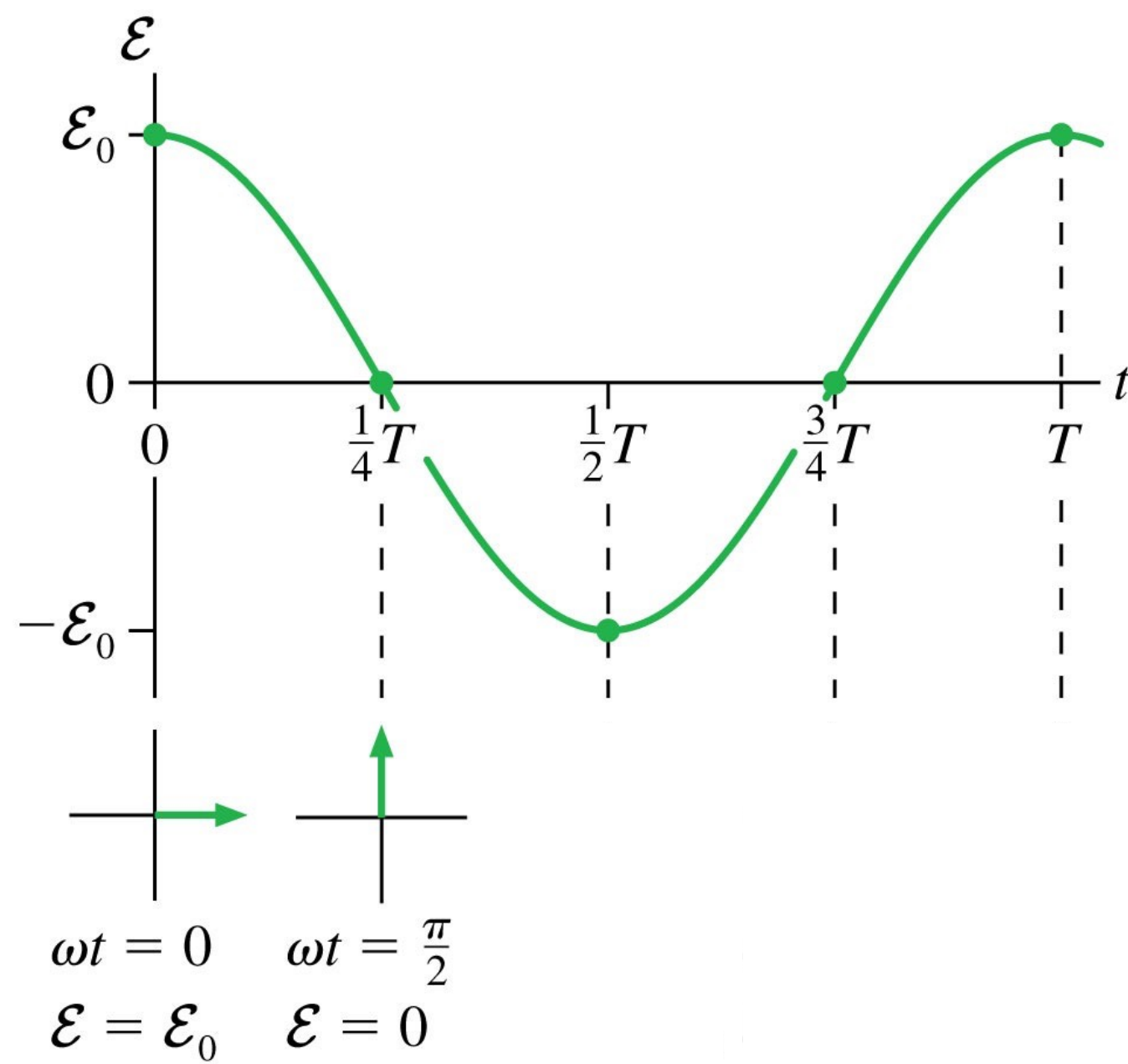

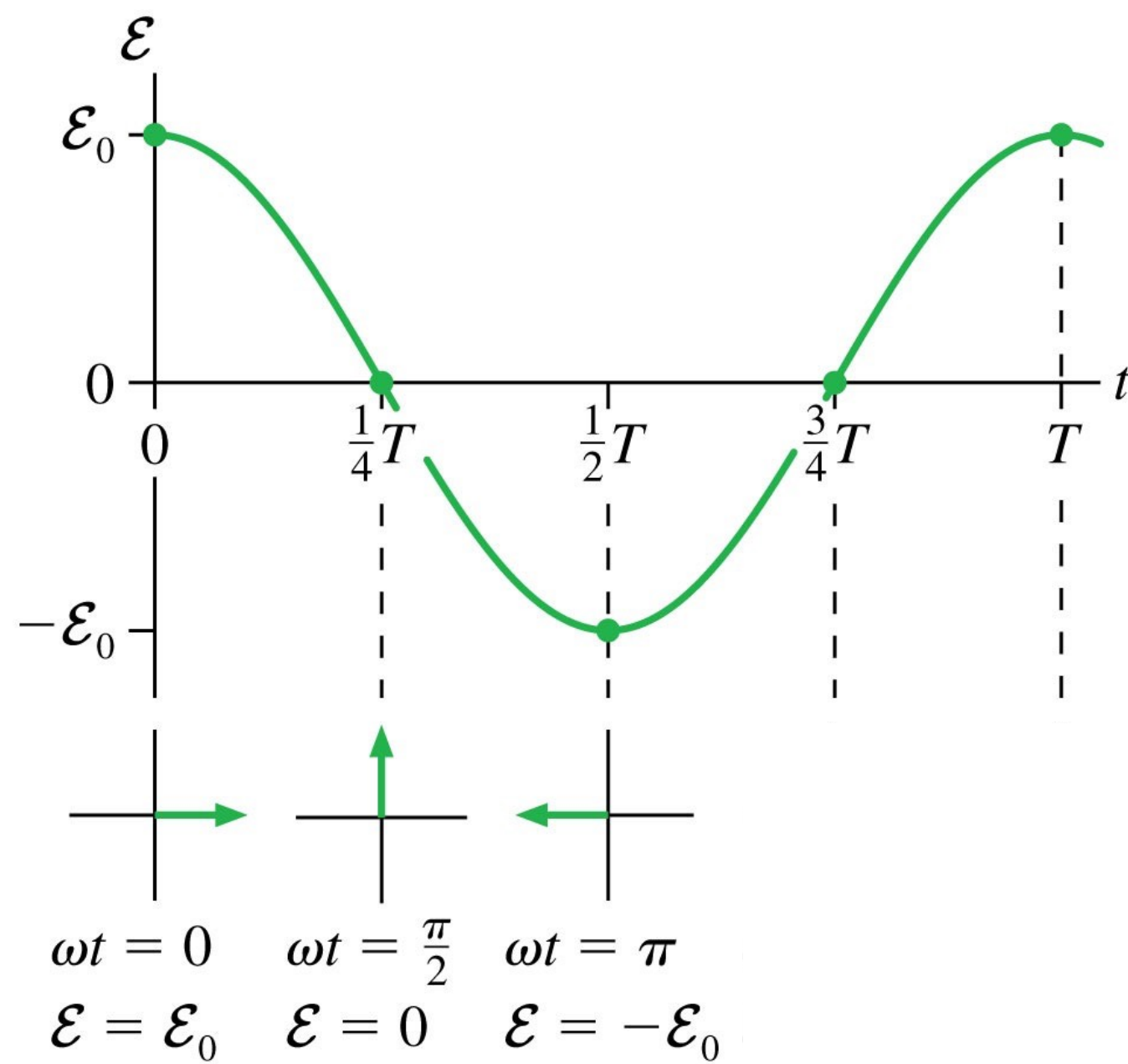

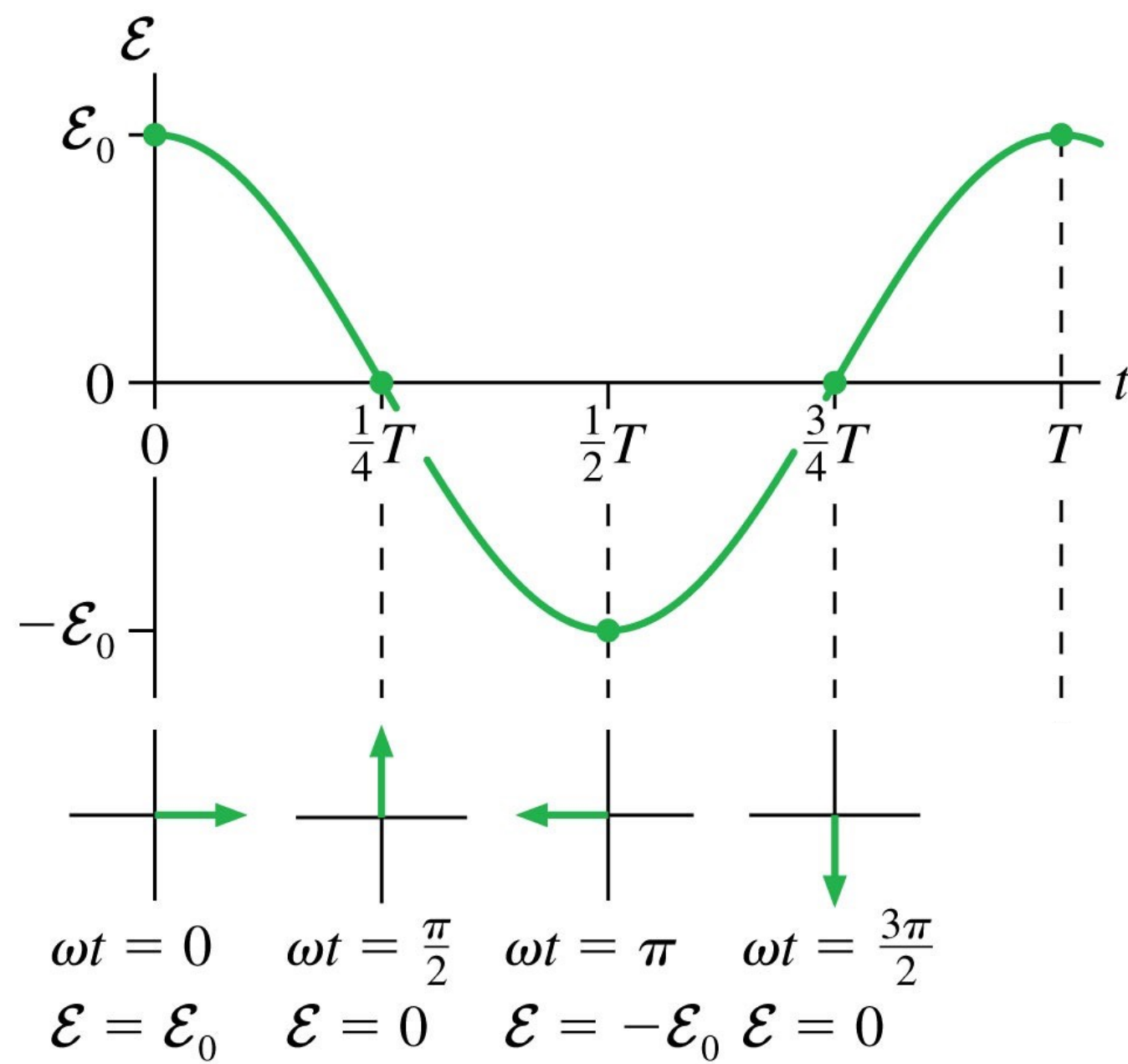


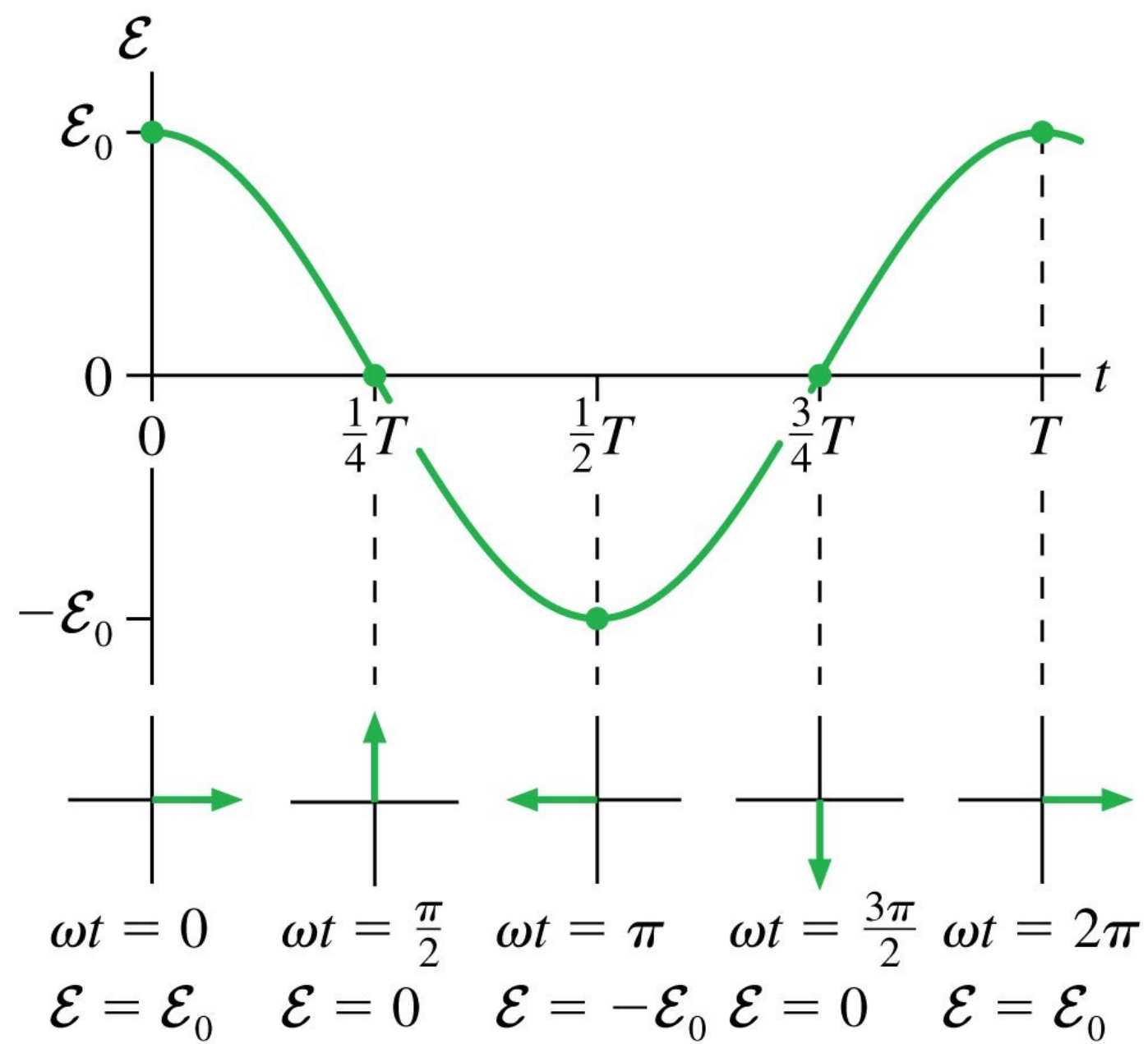


Question #25

This is a current phasor. The magnitude of the instantaneous value of the current is

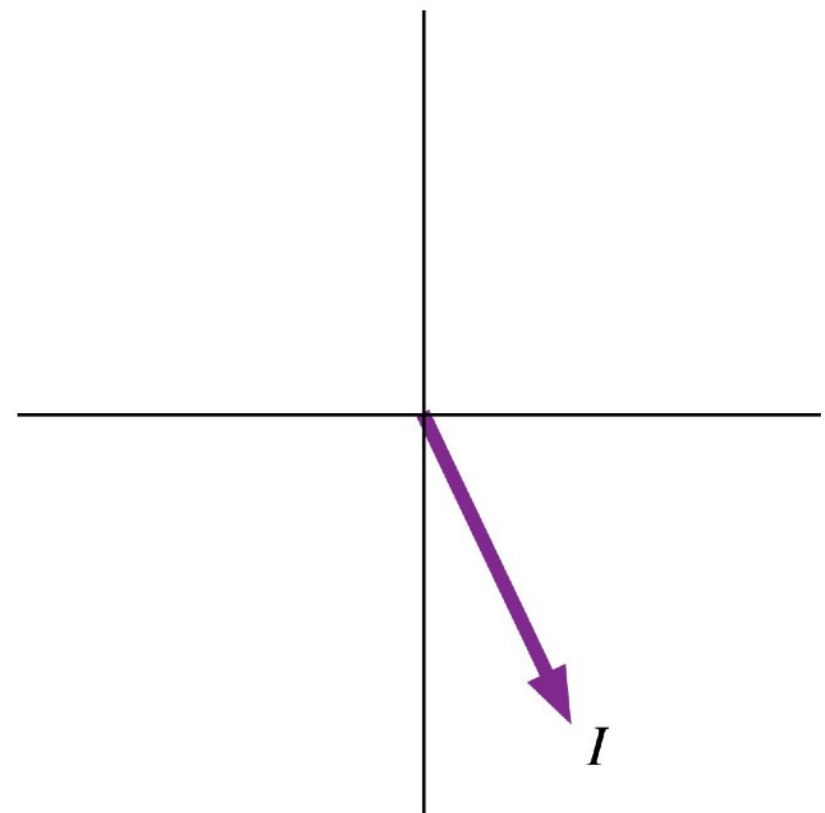- A. Increasing.
- B. Decreasing.
- C. Constant.




Resistor Circuit

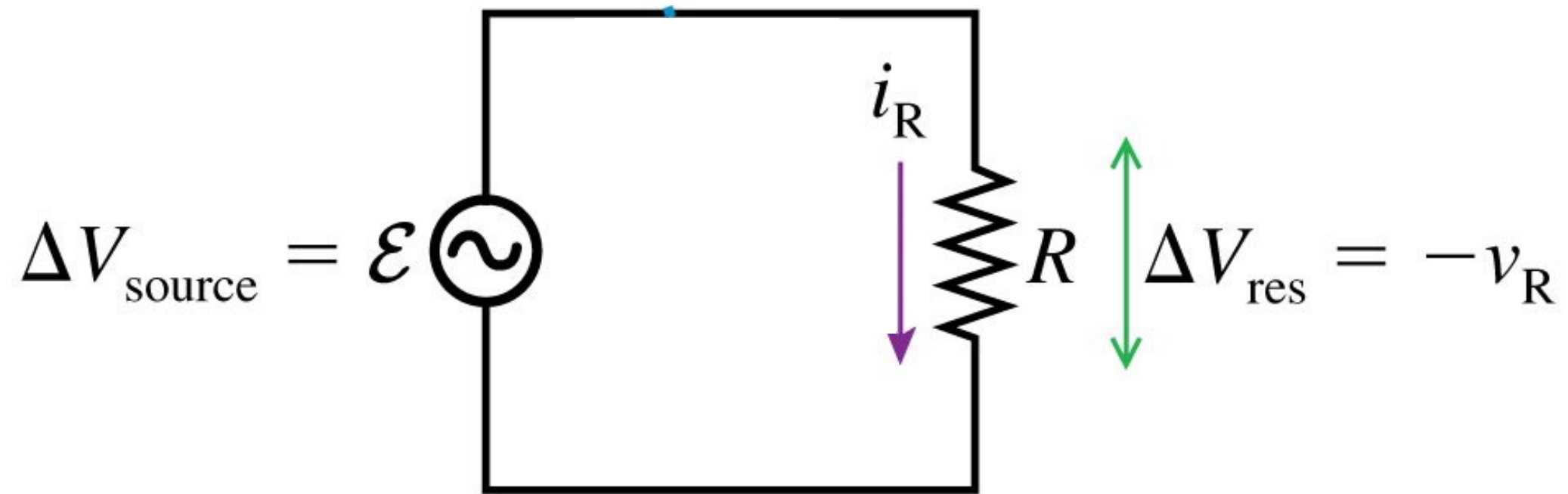

Why little i and little v?


Resistor Circuit

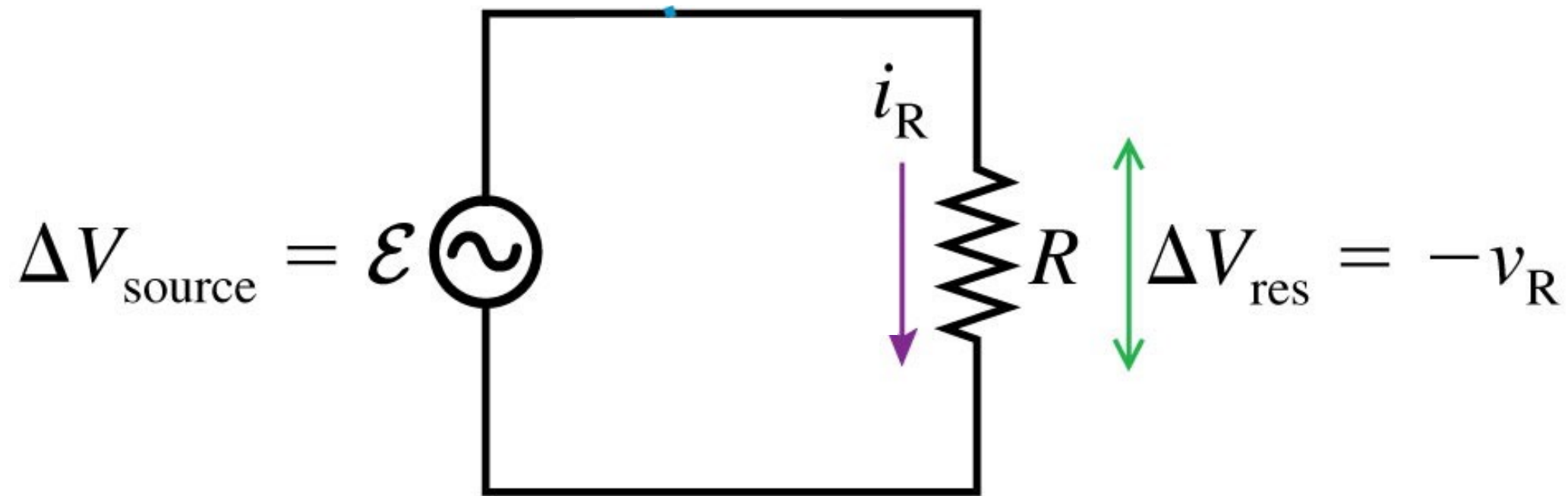

Why little i and little v?

When the current through the resistor is a max/min is the voltage across the resistor a max or a min?

Resistor Circuit

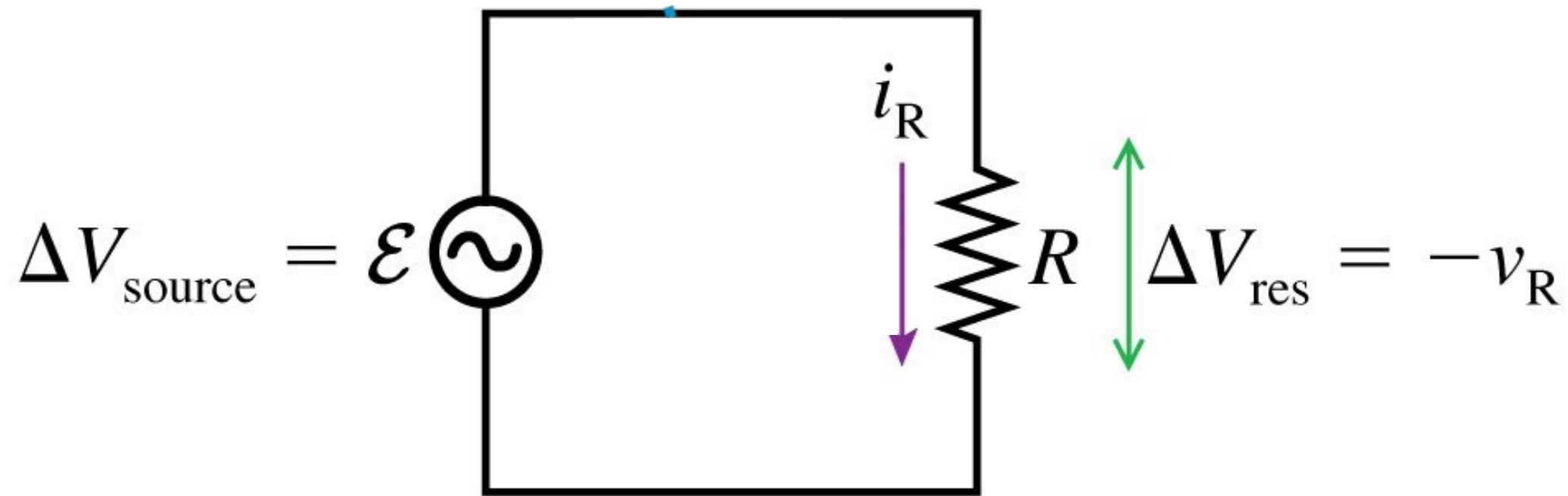


Why little i and little v?

When the current through the resistor is a max/min is the voltage across the resistor a max or a min?

$$i_R = \frac{v_R}{R} = \frac{V_R \cos \omega t}{R} = I_R \cos \omega t$$


Resistor Circuit

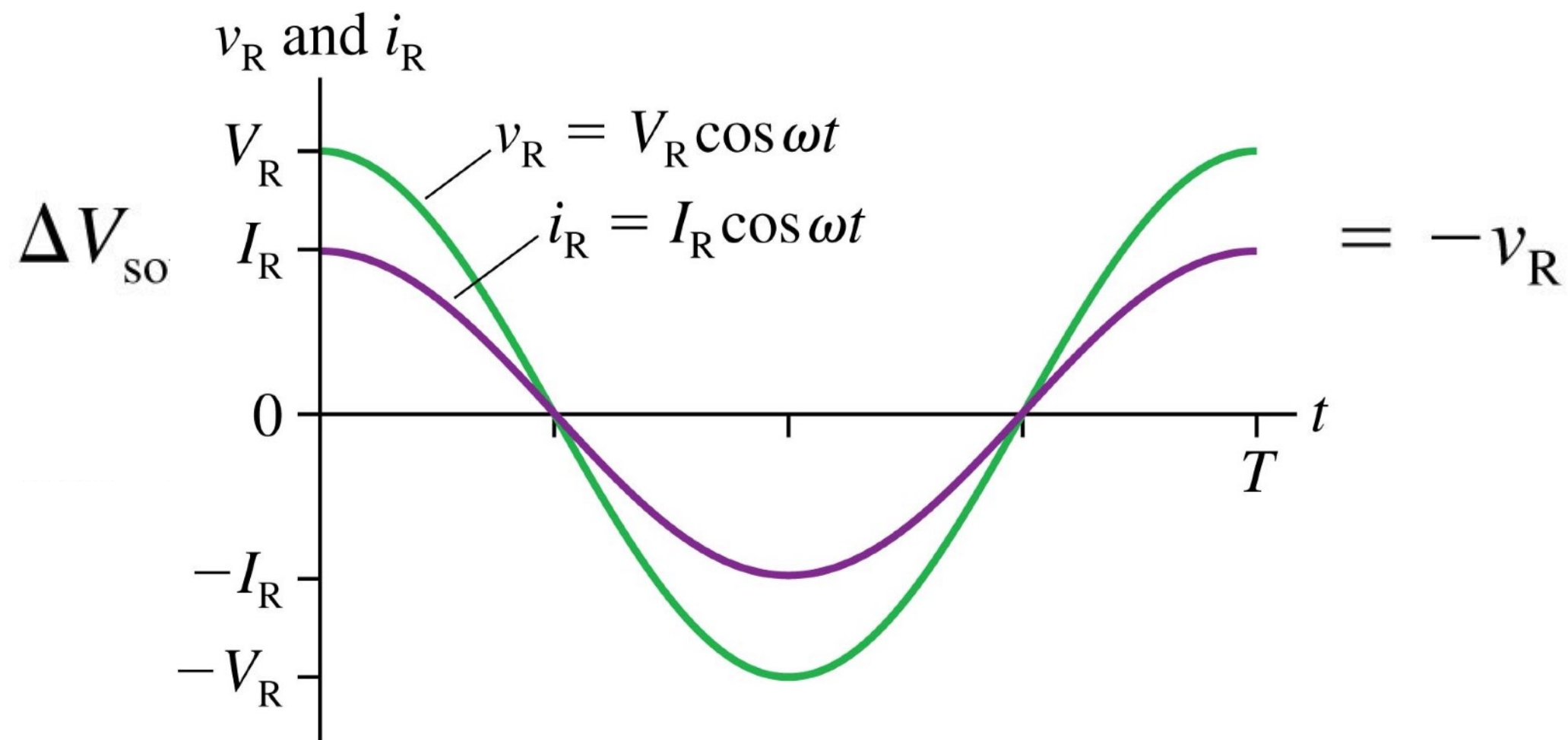

When the current through the resistor is a max/min is the voltage across the resistor a max or a min?

$$i_R = \frac{v_R}{R} = \frac{V_R \cos \omega t}{R} = I_R \cos \omega t$$


Resistor Circuit

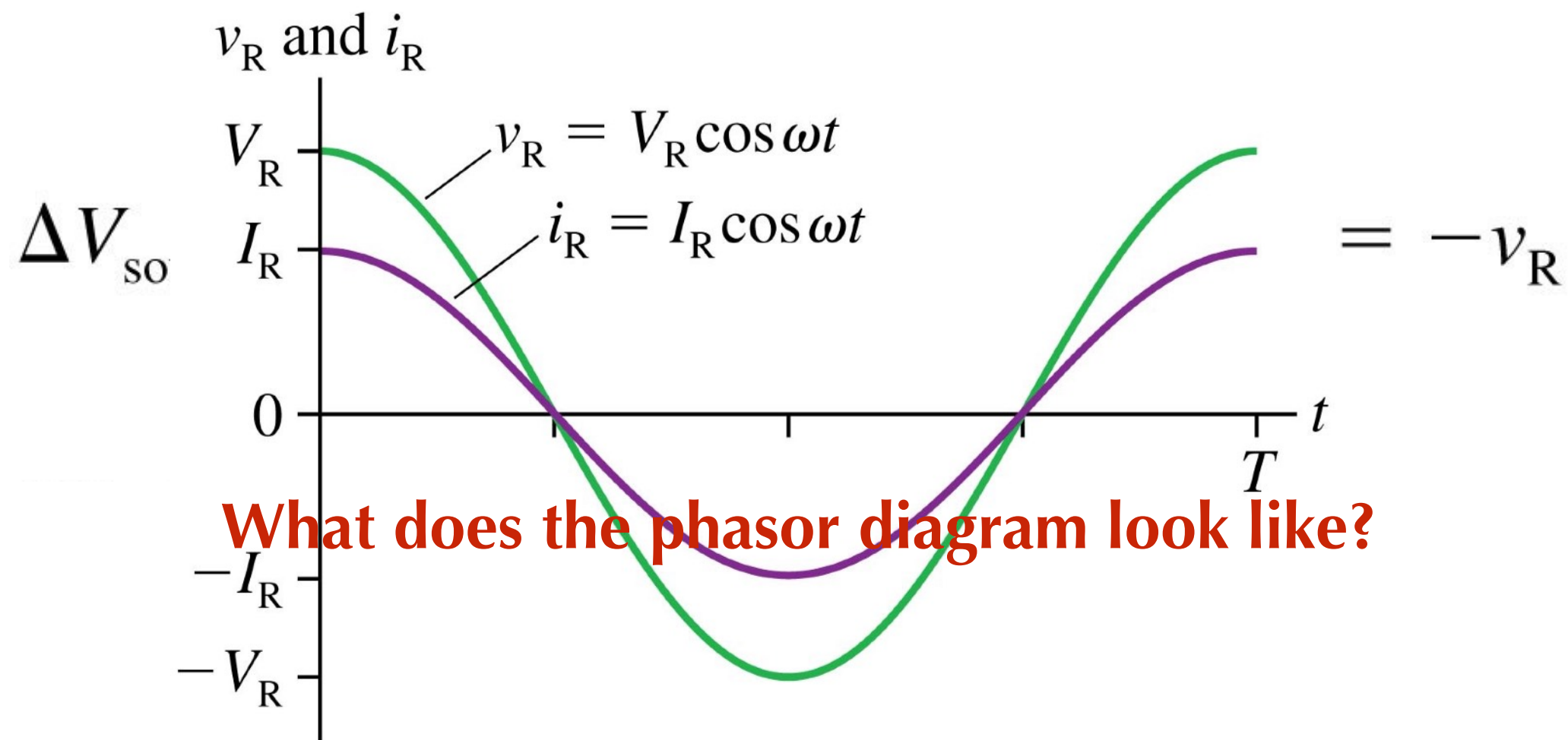

When the current through the resistor is a max/min is the voltage across the resistor a max or a min?

$$i_R = \frac{v_R}{R} = \frac{V_R \cos \omega t}{R} = I_R \cos \omega t$$


Resistor Circuit

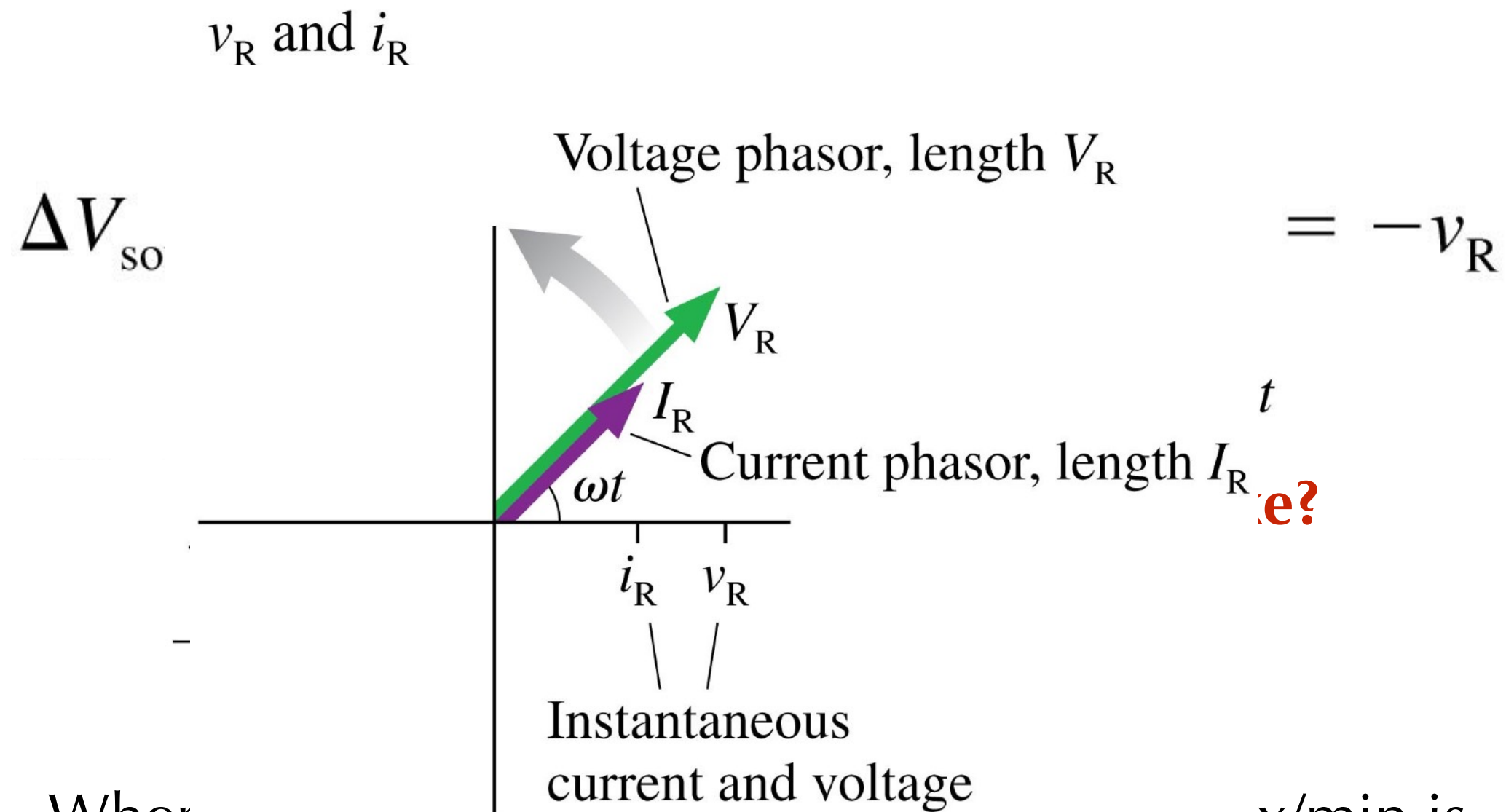

When the current through the resistor is a max/min is the voltage across the resistor a max or a min?

$$i_R = \frac{v_R}{R} = \frac{V_R \cos \omega t}{R} = I_R \cos \omega t$$

Capacitor Circuit

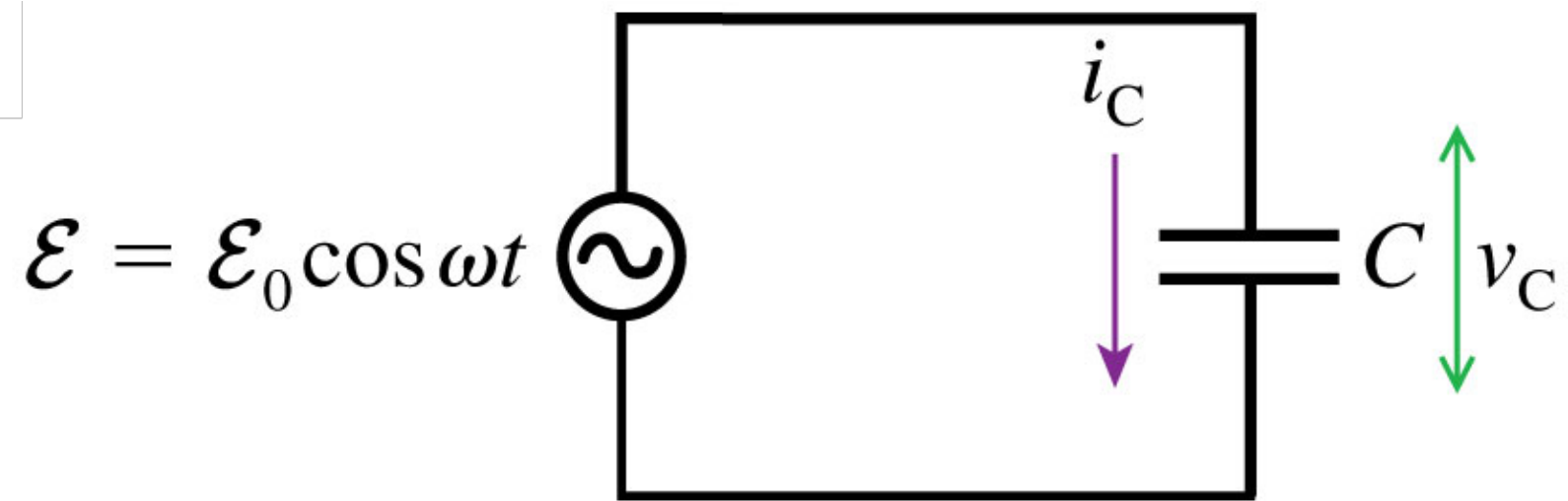


When the current in the circuit is high, the voltage across the capacitor is _____?

Question #26


C- Low

D- High

Capacitor Circuit

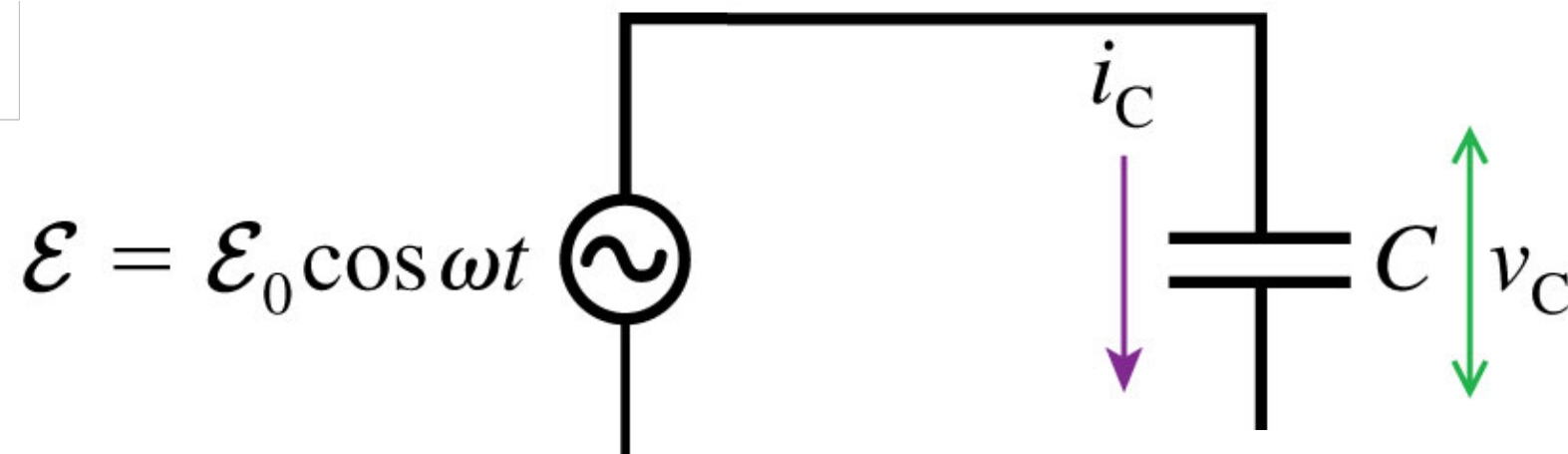

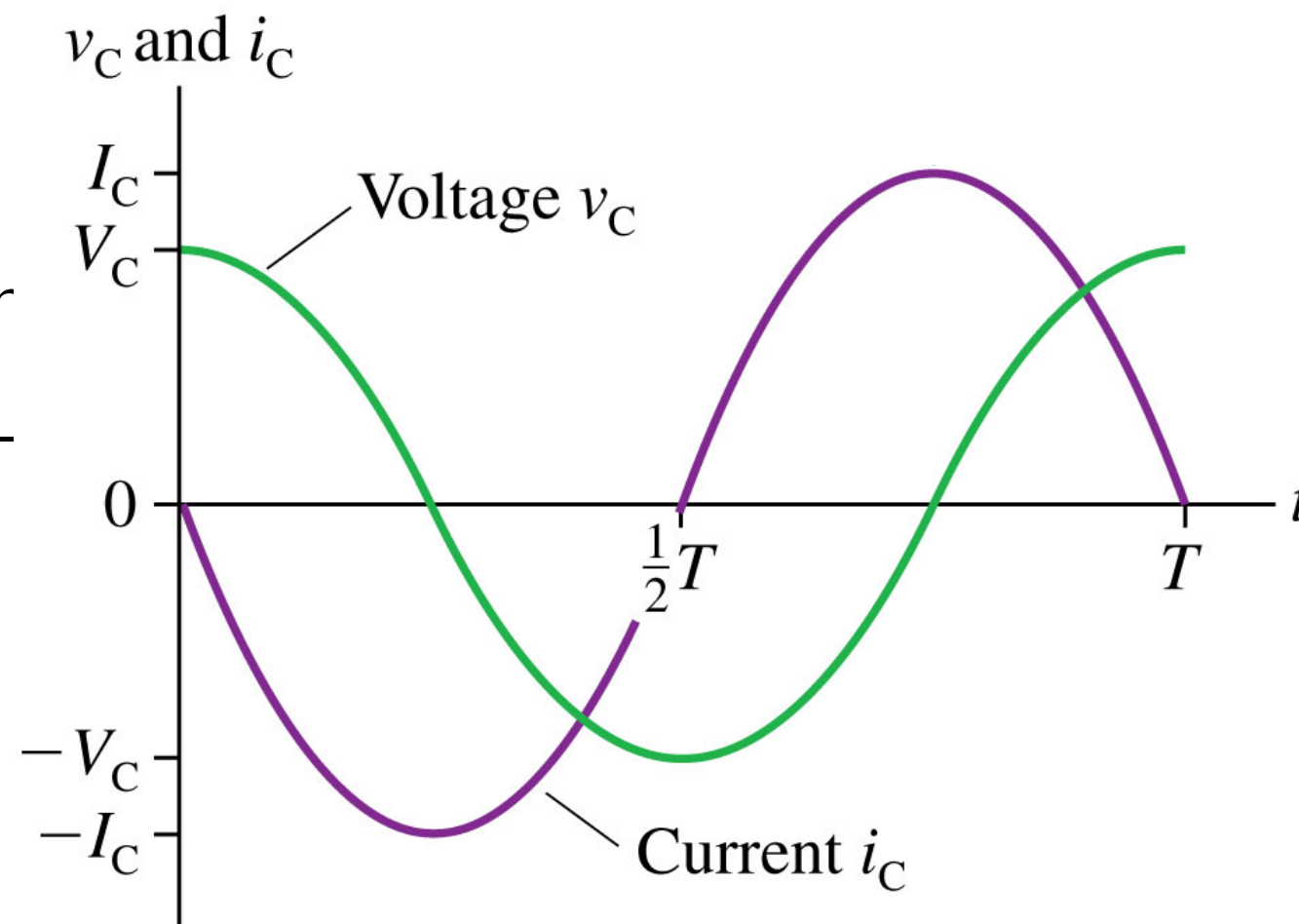
When the current through the capacitor is _____



cross the


on #26

The Math

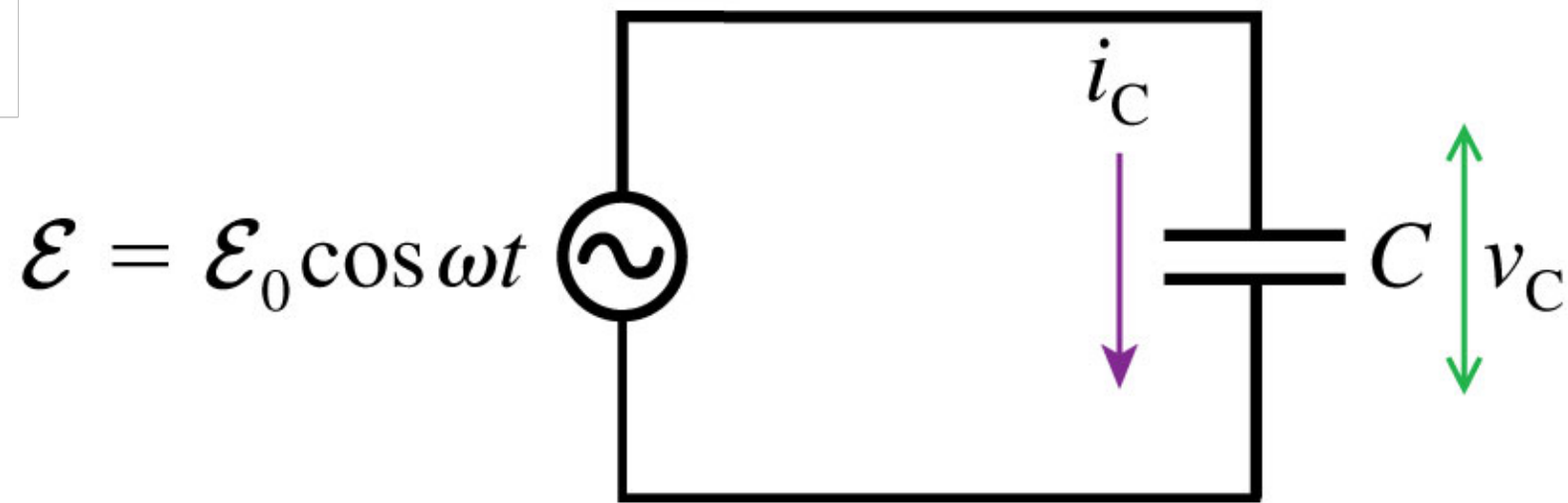

$$q = Cv_C = CV_C \cos \omega t$$


The Math

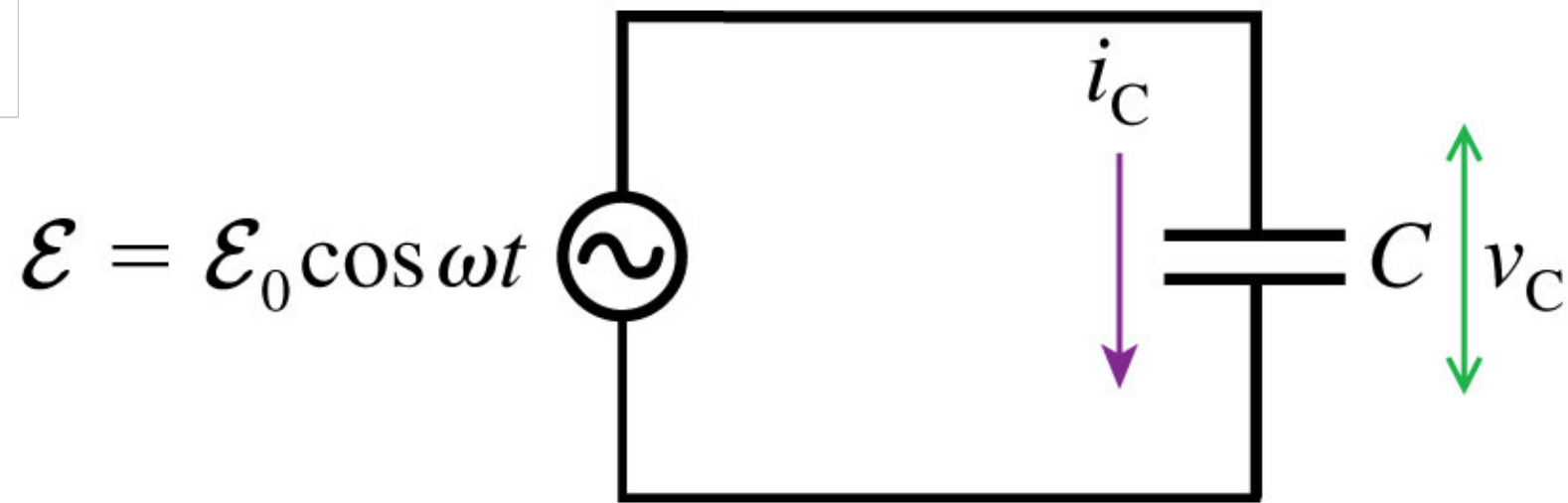

$$q = Cv_C = CV_C \cos \omega t$$

$$i_C = \frac{dq}{dt}$$


The Math

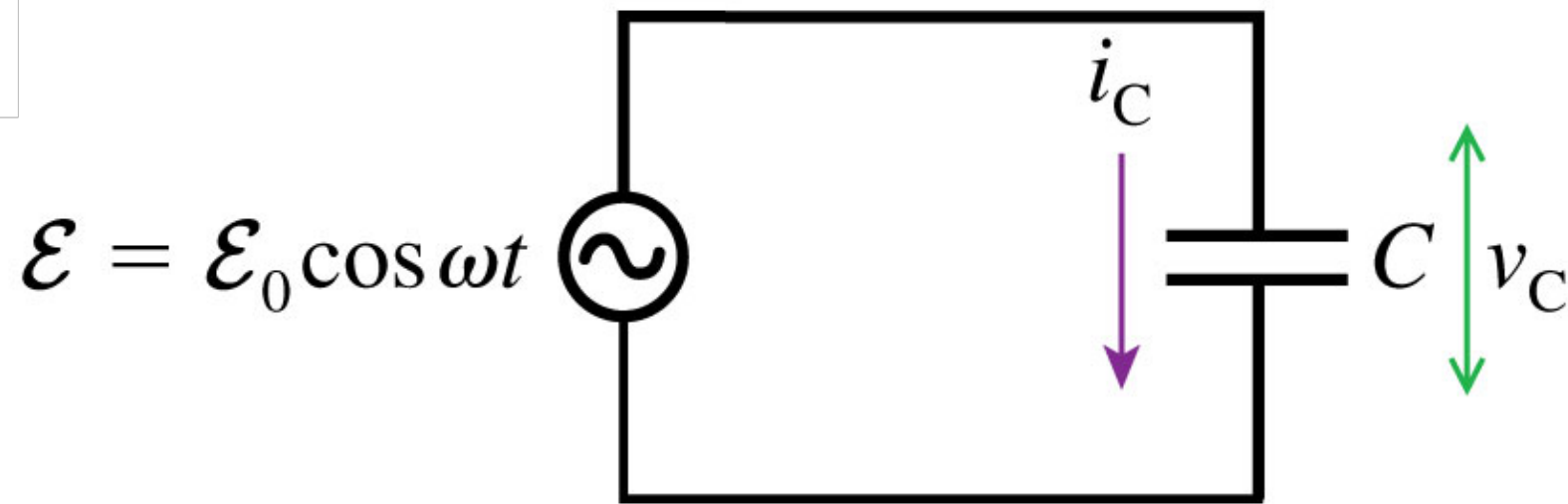

$$q = Cv_C = CV_C \cos \omega t$$

$$i_C = \frac{dq}{dt} = \frac{d}{dt}(CV_C \cos \omega t) = -\omega CV_C \sin \omega t$$

The Math

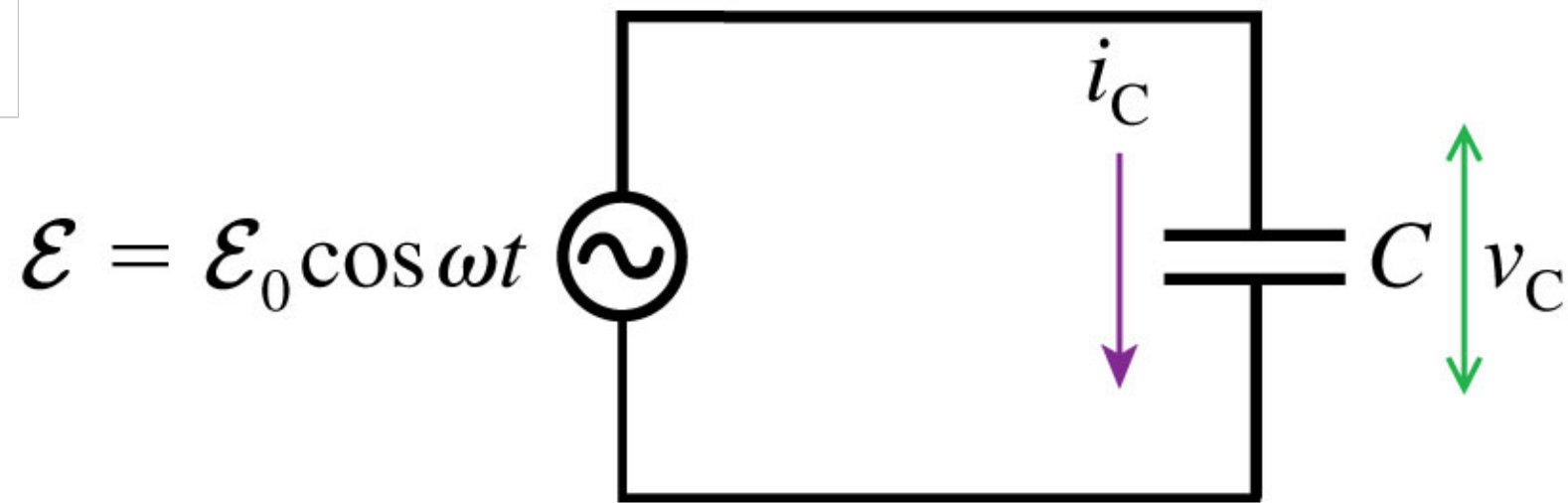


$$q = Cv_C = CV_C \cos \omega t$$

$$i_C = \frac{dq}{dt} = \frac{d}{dt}(CV_C \cos \omega t) = -\omega CV_C \sin \omega t$$

$$-\sin(x) = \cos(x + \pi/2)$$

The Math


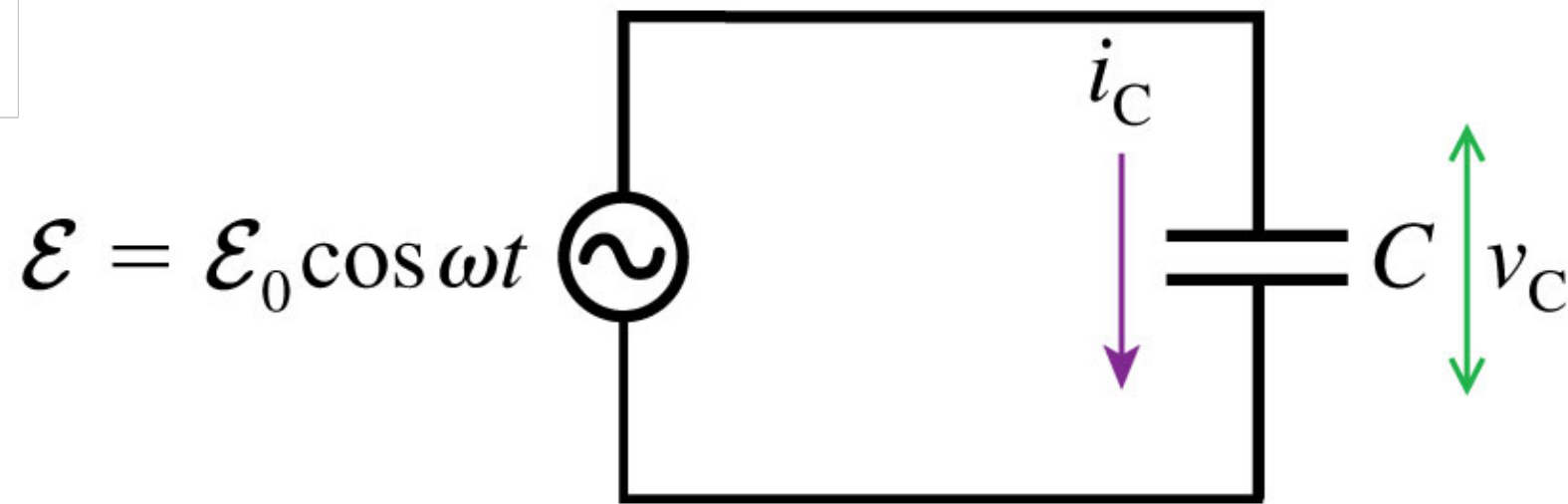


$$q = Cv_C = CV_C \cos \omega t$$


$$i_C = \frac{dq}{dt} = \frac{d}{dt}(CV_C \cos \omega t) = -\omega CV_C \sin \omega t \quad -\sin(x) = \cos(x + \pi/2)$$

$$i_C = \omega CV_C \cos \left(\omega t + \frac{\pi}{2} \right)$$

The Math

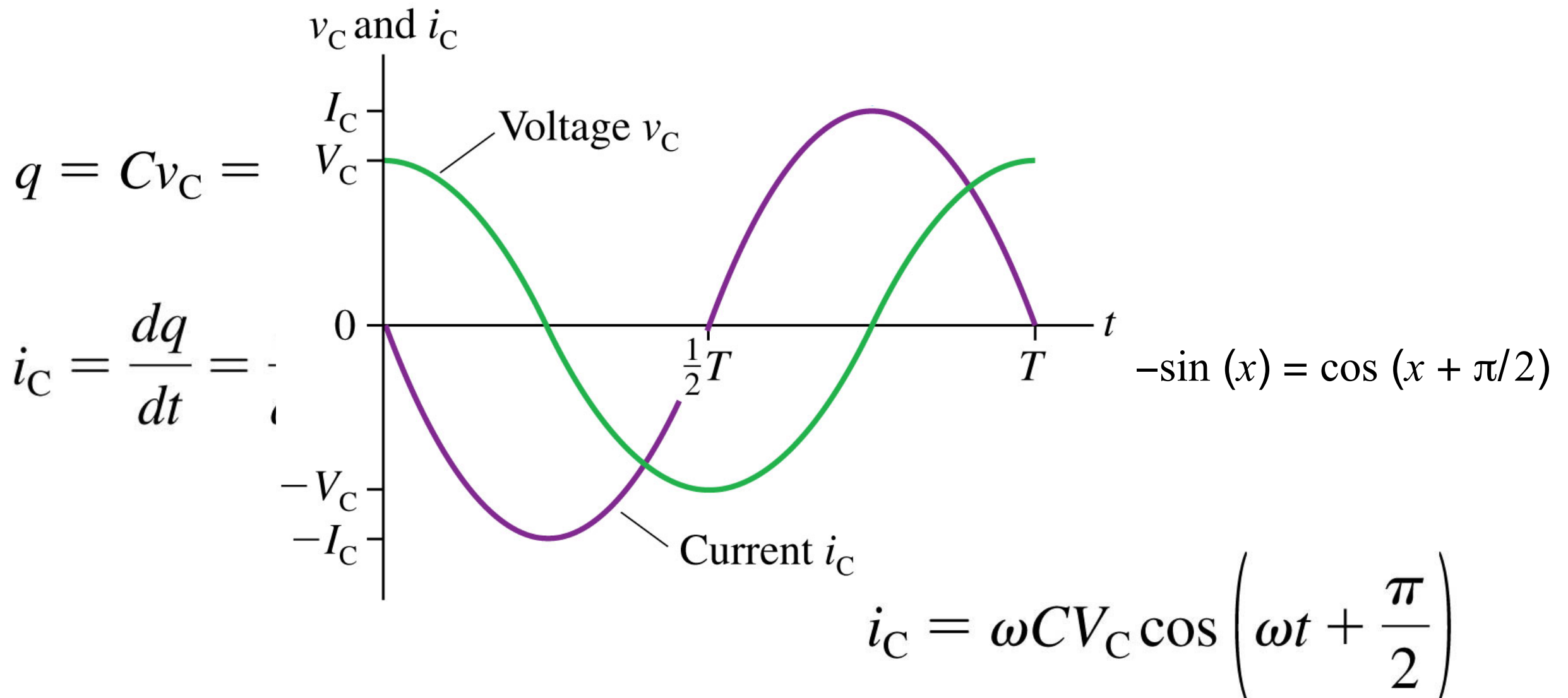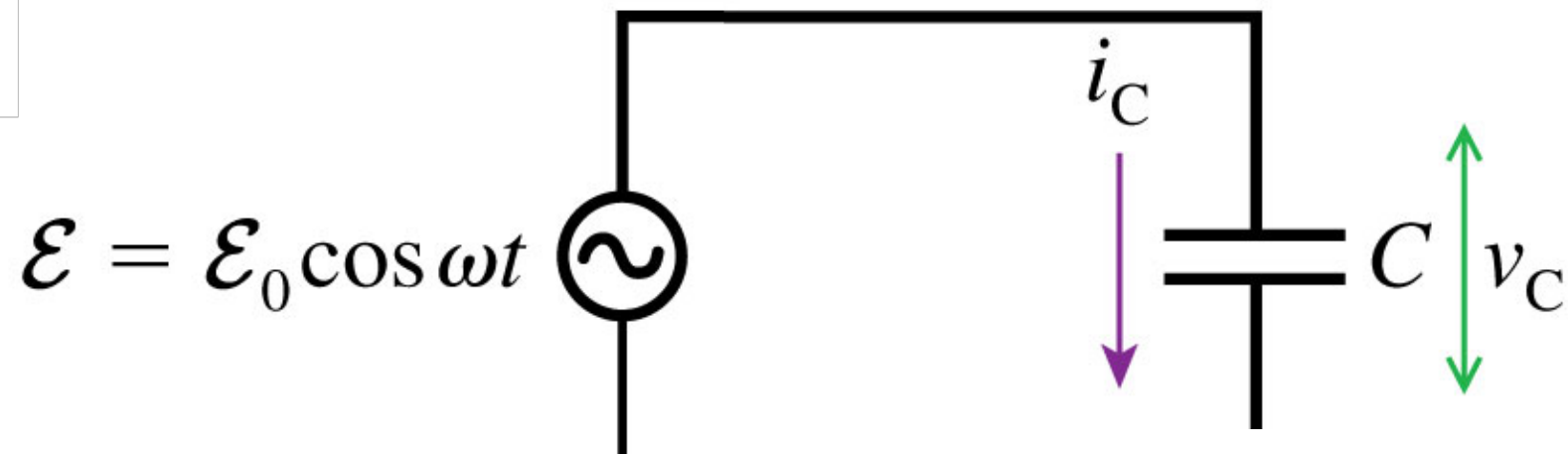


The Math

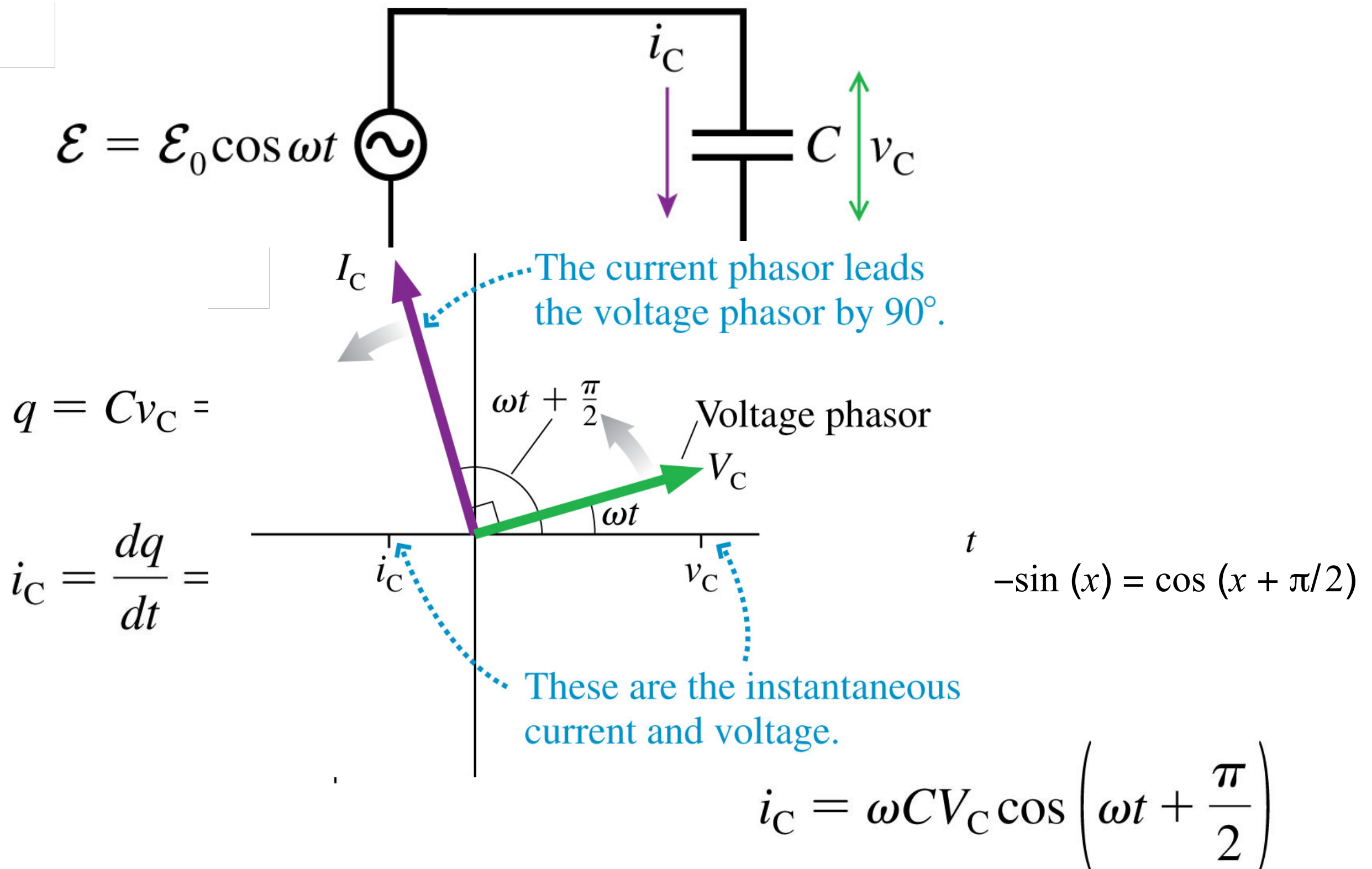

Question #27

In the circuit represented by these phasors, the current _____ the voltage

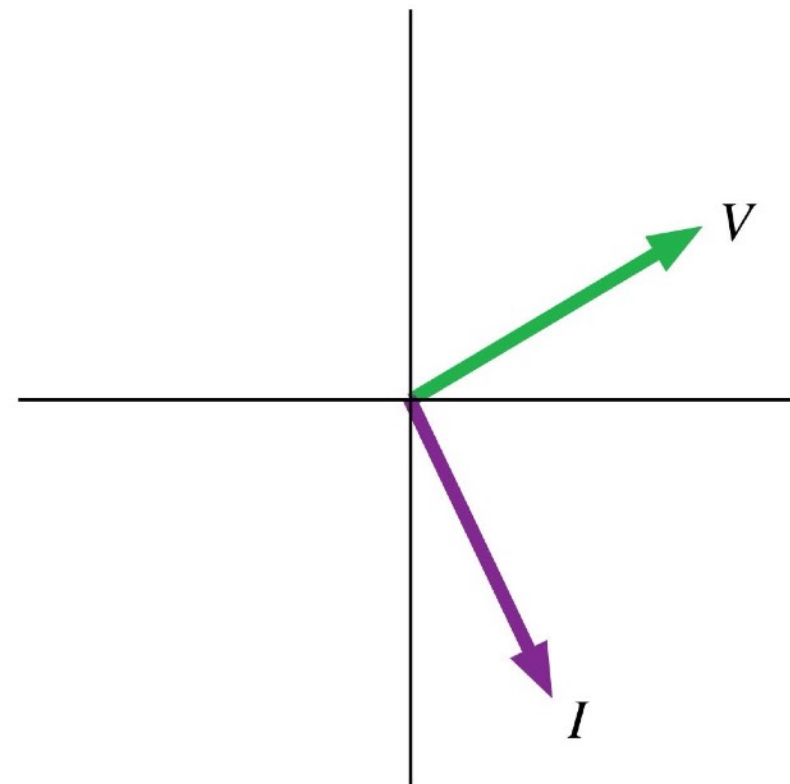- A. leads
- B. is perpendicular to
- C. lags
- D. is out of phase with




Question #28


In the circuit represented by these graphs, the current _____ the voltage

- A. leads
- B. is less than
- C. is out of phase with
- D. lags

Voltage and current

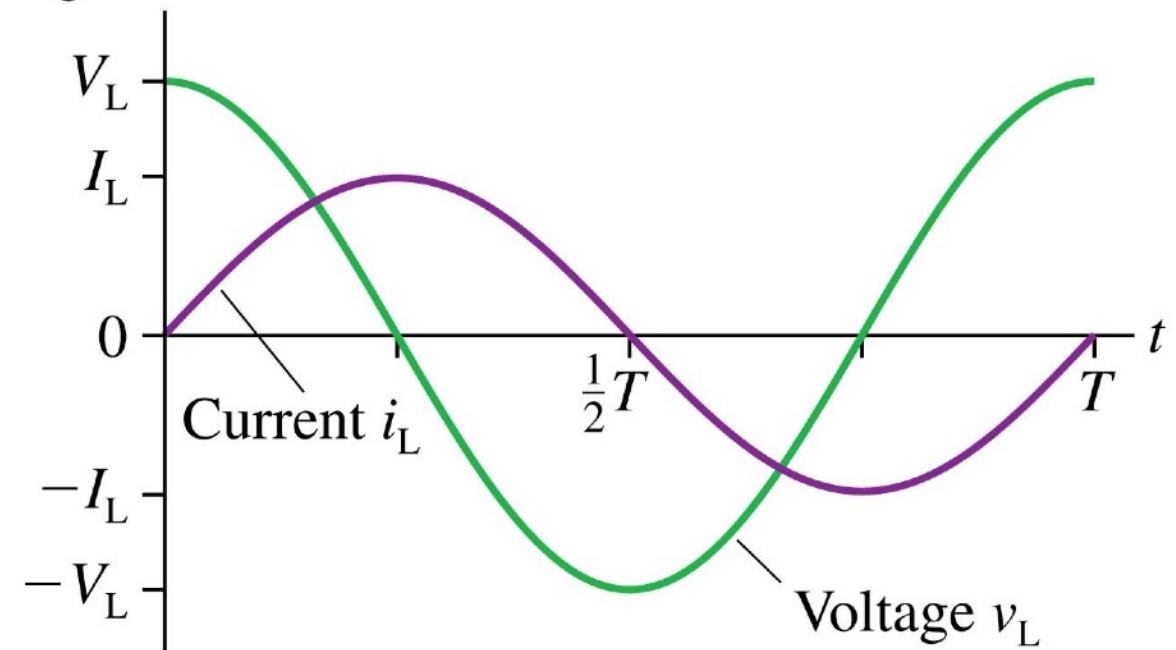

What about the frequency of the source

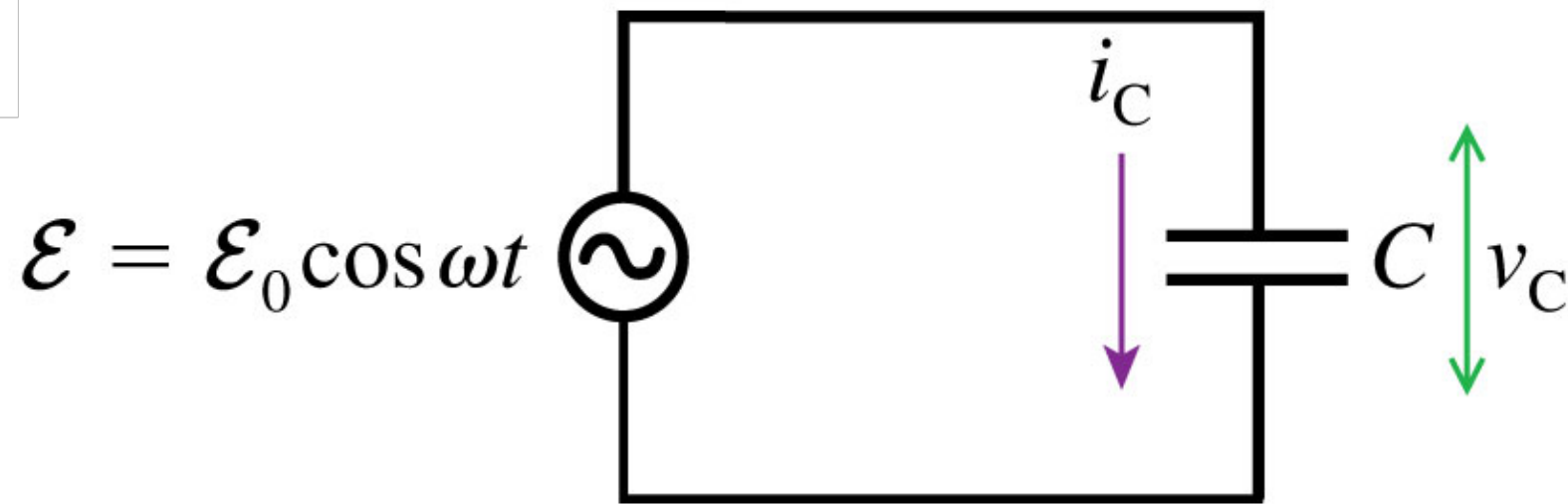


If the frequency of the source is high(low) will the max current in the circuit be high or low?

Question #29

D- Low
E- High

What about the frequency of the source

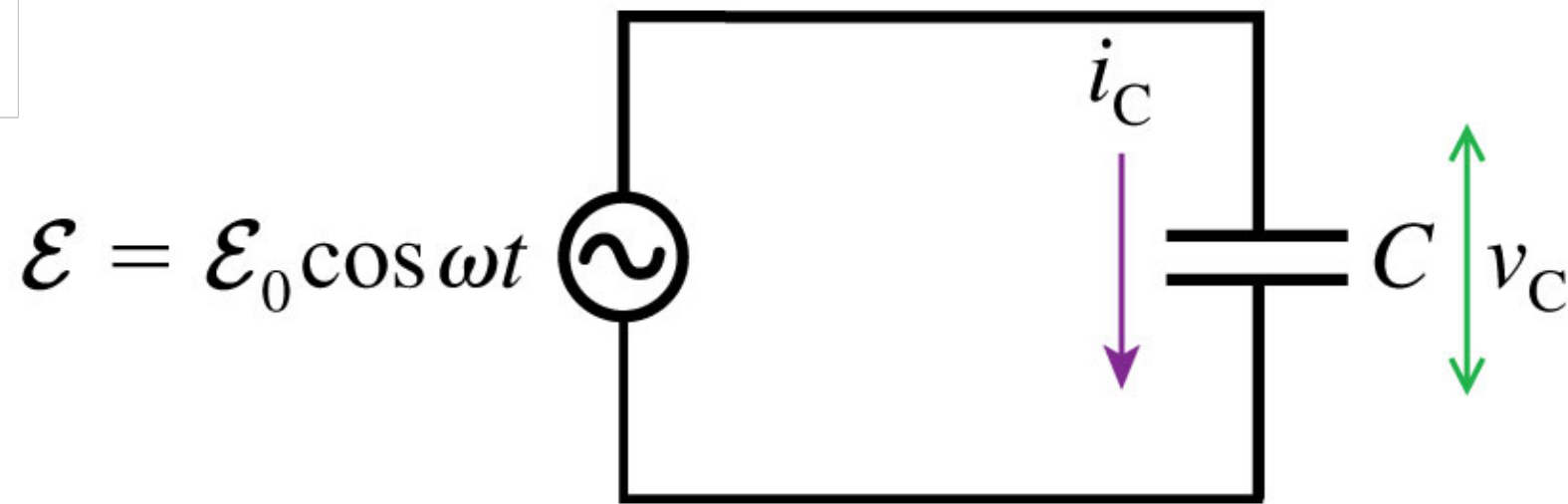


If the frequency of the source is high(low) will the max current in the circuit be high or low?

Question #29

$$i_C = \omega C V_C \cos \left(\omega t + \frac{\pi}{2} \right)$$

What about the frequency of the source

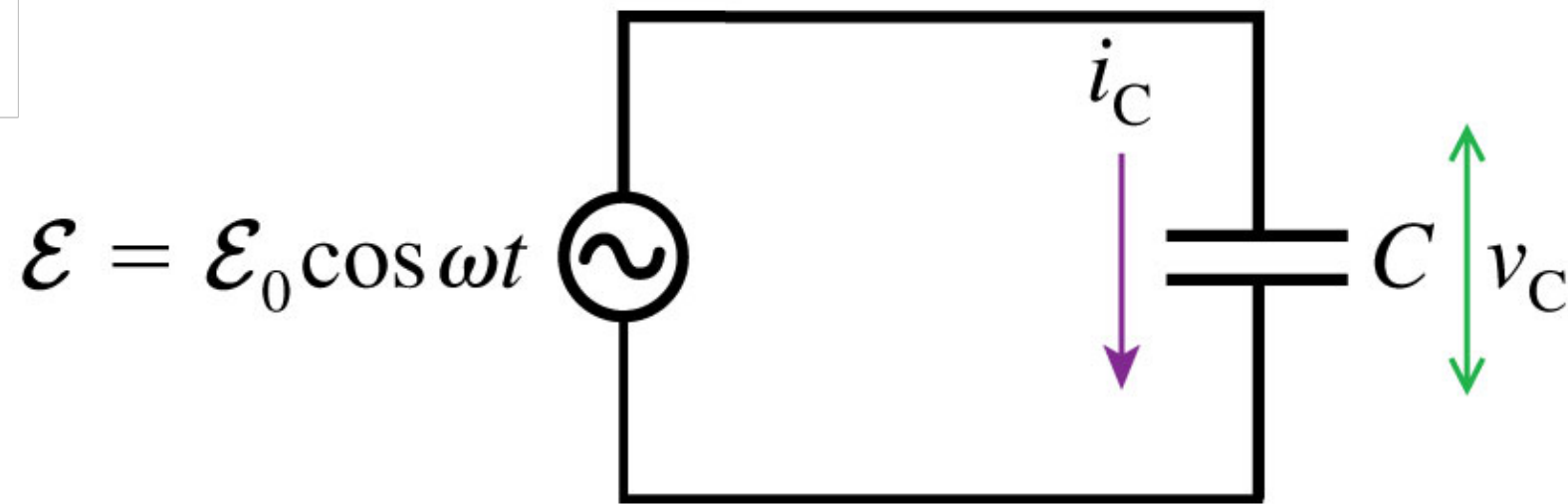


If the frequency of the source is high(low) will the max current in the circuit be high or low?

Question #29

$$i_C = \omega C V_C \cos \left(\omega t + \frac{\pi}{2} \right)$$

$$I_C = \omega C V_C \quad (\text{Max current in the circuit})$$

What about the frequency of the source

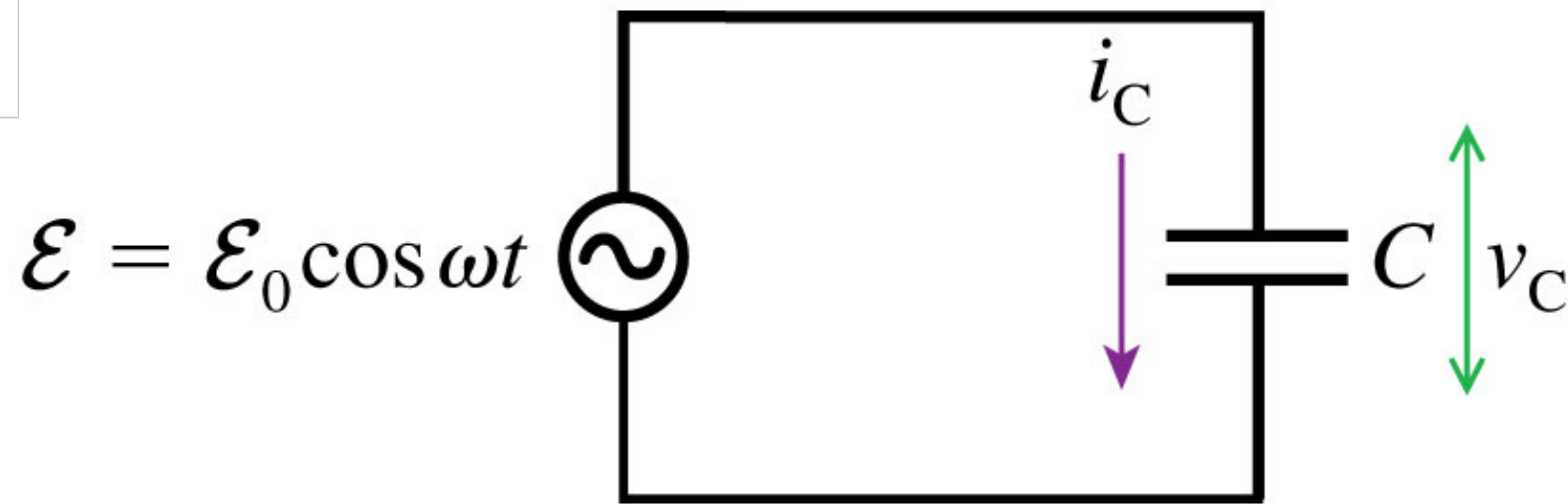

If the frequency of the source is high(low) will the max current in the circuit be high or low?


Question #29

$$i_C = \omega C V_C \cos \left(\omega t + \frac{\pi}{2} \right)$$

$$I_C = \omega C V_C \quad (\text{Max current in the circuit})$$

$$X_C = \frac{1}{\omega C} \quad (\text{Capacitive Reactance})$$

What about the frequency of the source

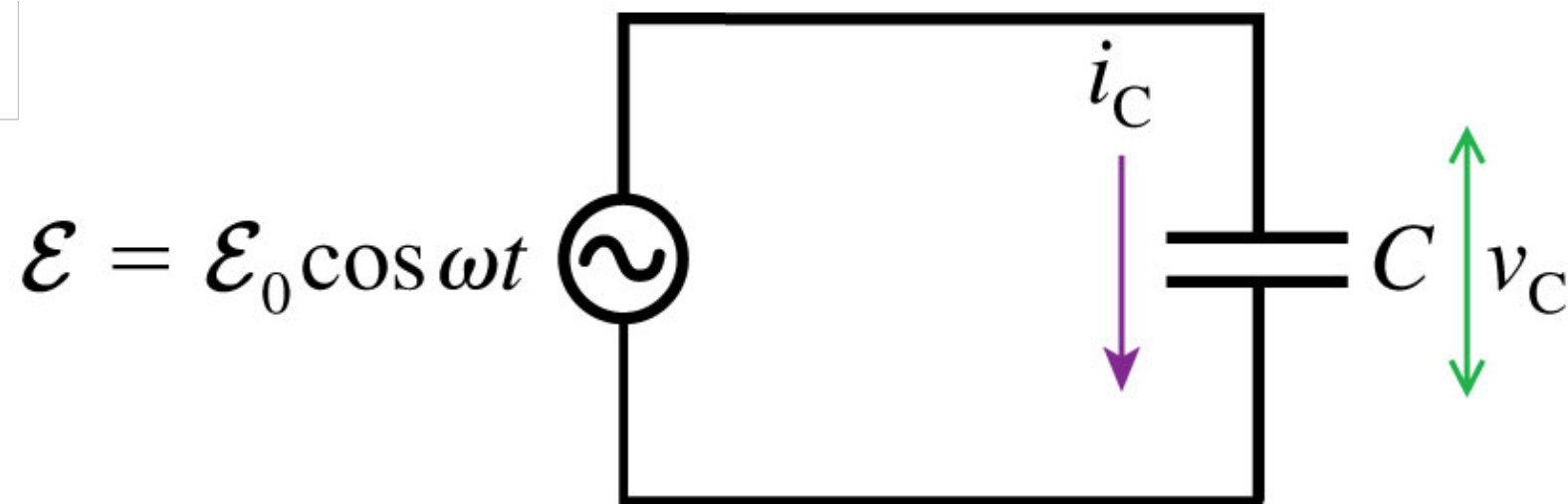

If the frequency of the source is high(low) will the max current in the circuit be high or low?

Question #29


$$i_C = \omega C V_C \cos \left(\omega t + \frac{\pi}{2} \right)$$

$$I_C = \omega C V_C \quad (\text{Max current in the circuit})$$

$$X_C = \frac{1}{\omega C} \quad (\text{Capacitive Reactance})$$

$$I_C = \frac{V_C}{X_C} \quad (\text{Ohm's Law...kind of})$$

What about the frequency of the source

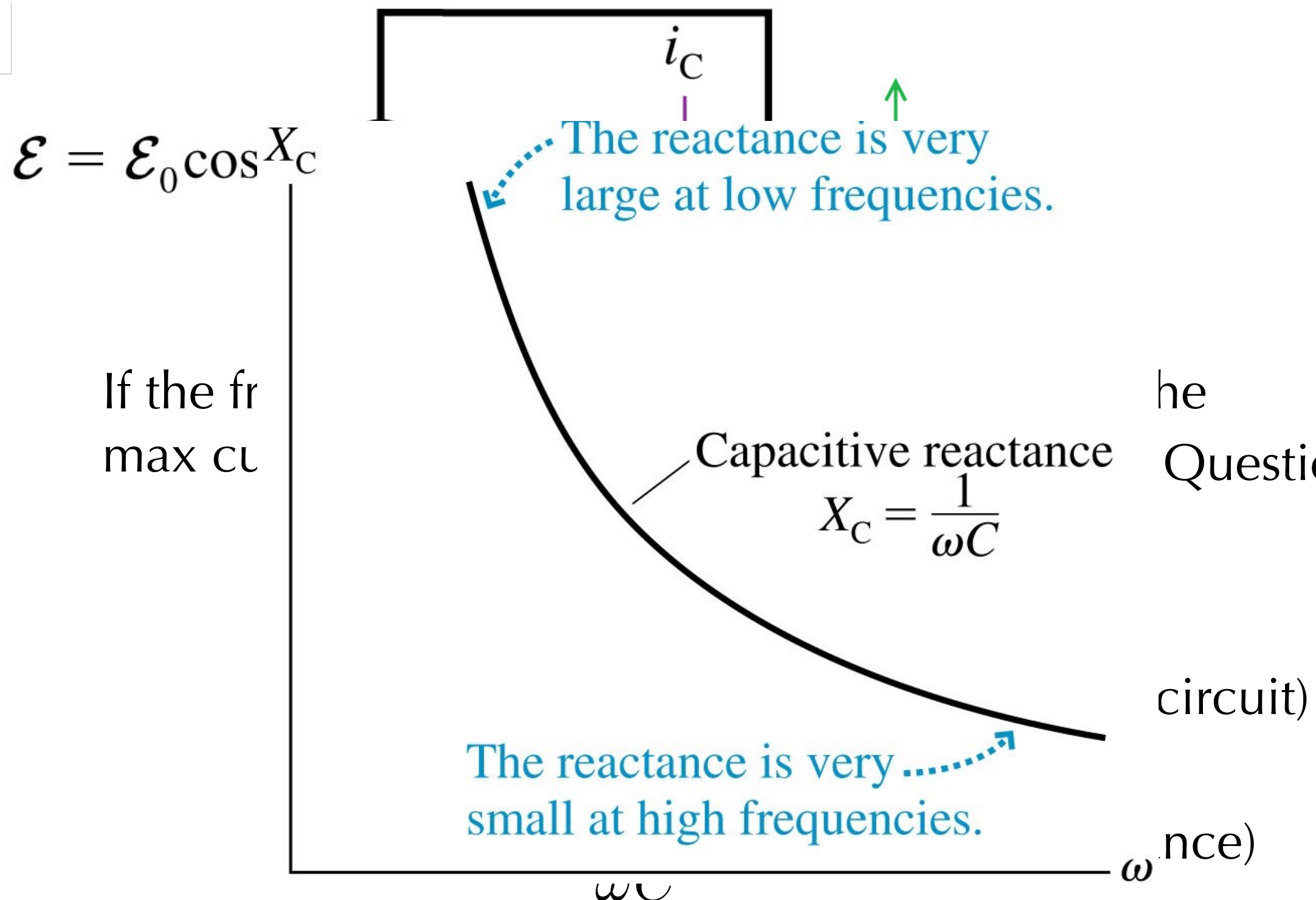

If the fr
max cu

he
Question #29

circuit)


ance)

$$I_C = \frac{V_C}{X_C} \quad (\text{Ohm's Law...kind of})$$

Question #30

If the value of the capacitance is doubled, the capacitive reactance

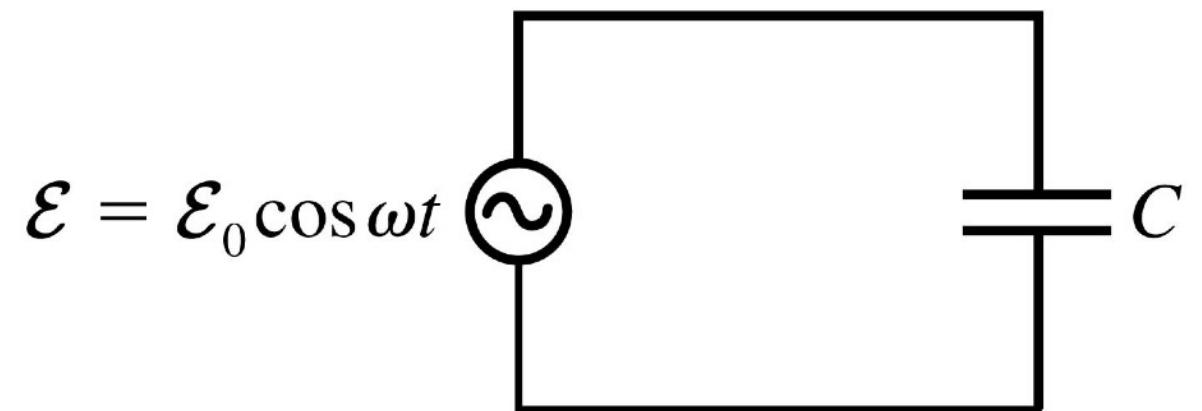
- A. Is quartered.
- B. Is halved.
- C. Is doubled.
- D. Is quadrupled.
- E. Can't tell without knowing ω .




Question #31

If the value of the capacitance is doubled, the peak current

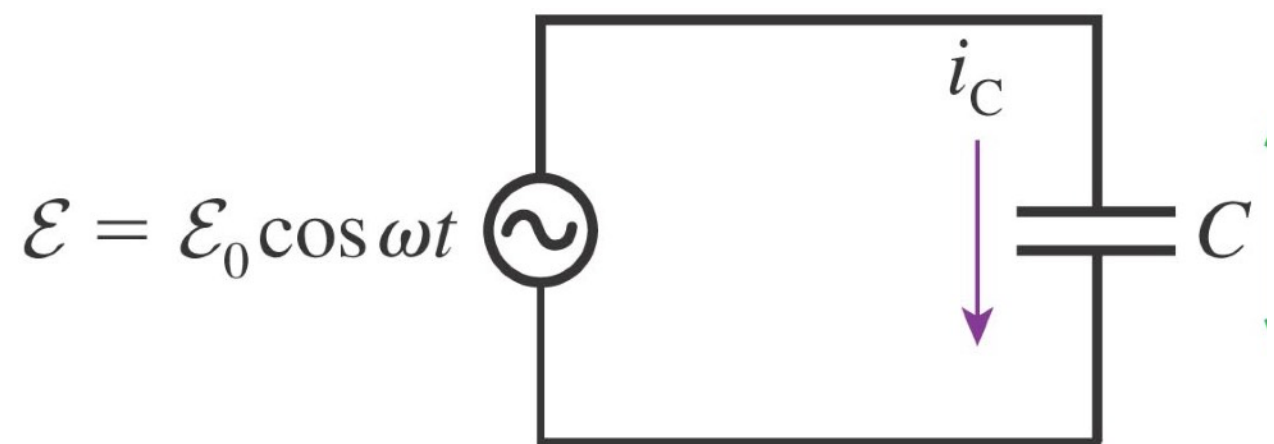- A. Is quartered.
- B. Is doubled.
- C. Is halved.
- D. Is quadrupled.
- E. Can't tell without knowing C .




AC RC circuit

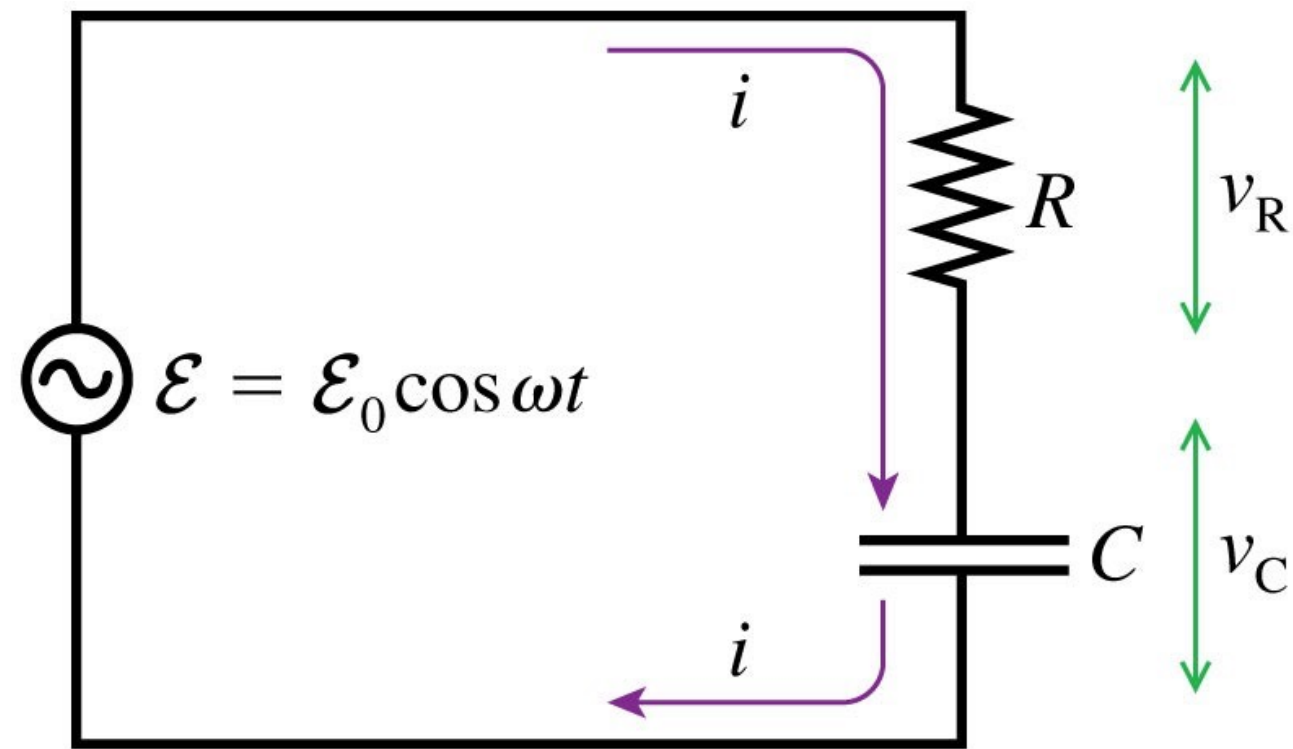


If the source frequency is high(low), will the peak voltage across the resistor (capacitor) be high or low?

Phasor Diagram

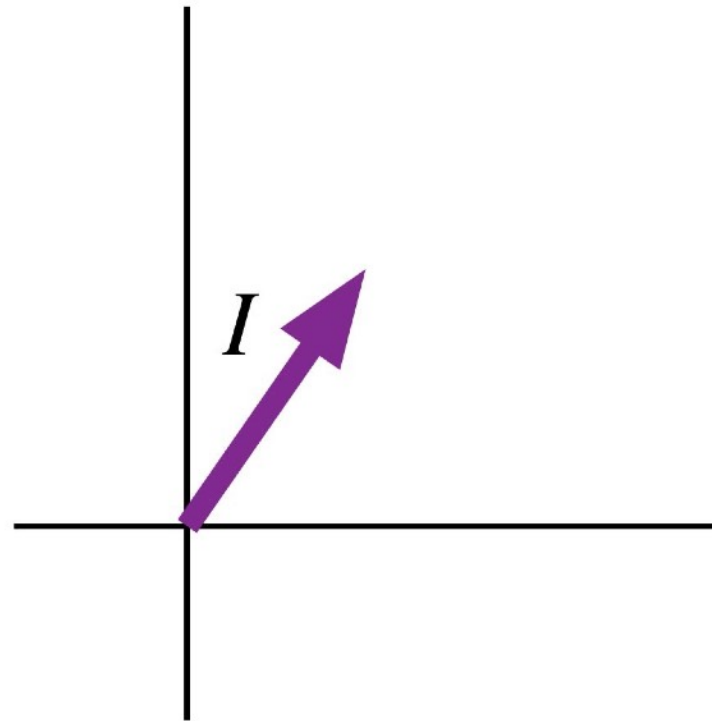


Draw the resistor voltage phasor and the capacitor voltage phasor

Phasor Diagram

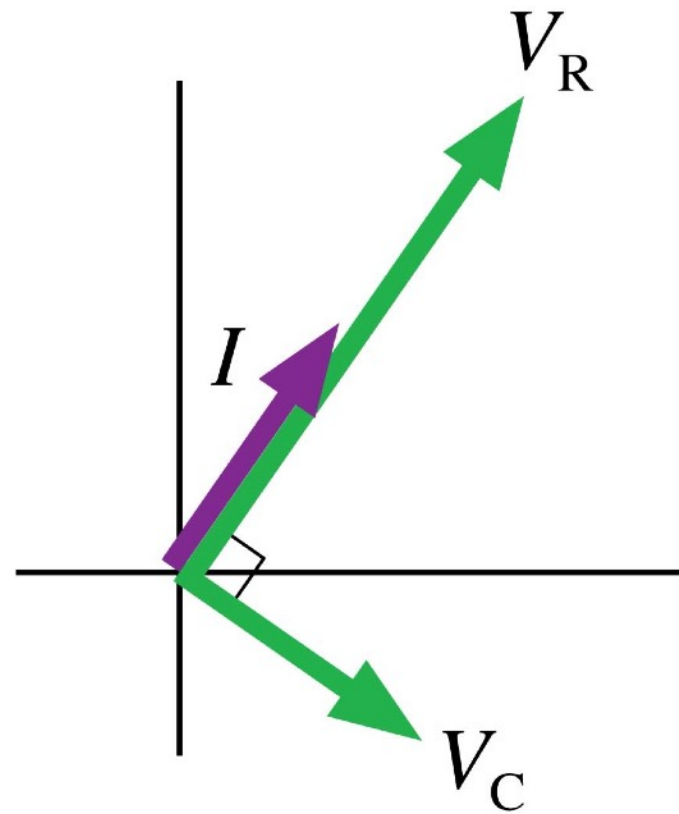


Draw the resistor voltage phasor and the capacitor voltage phasor

Phasor Diagram

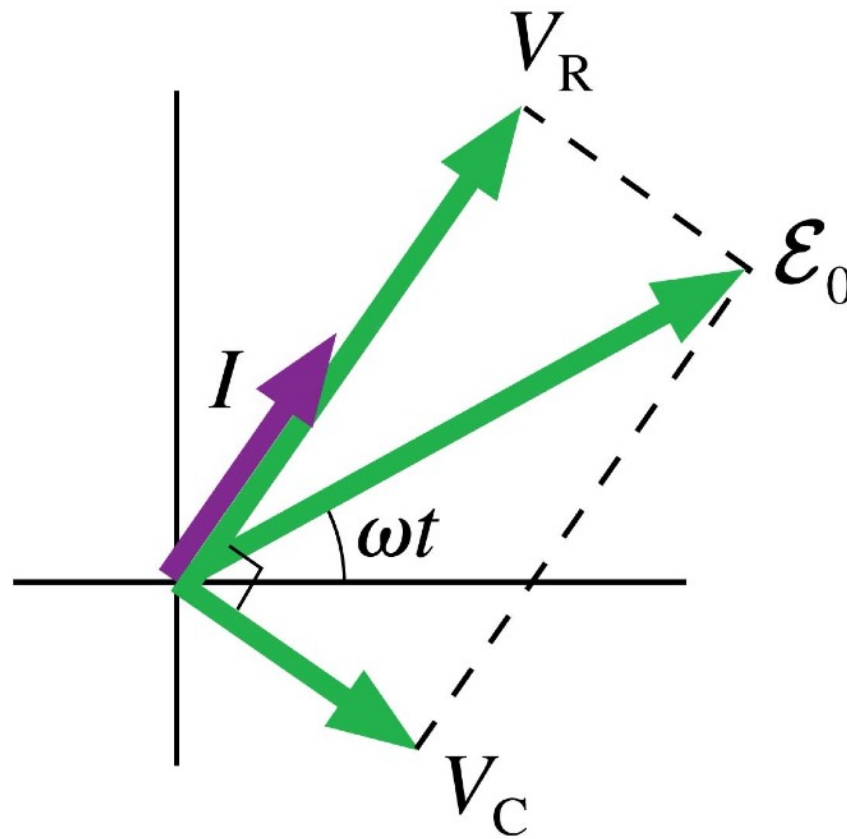


Draw the resistor voltage phasor and the capacitor voltage phasor

Phasor Diagram

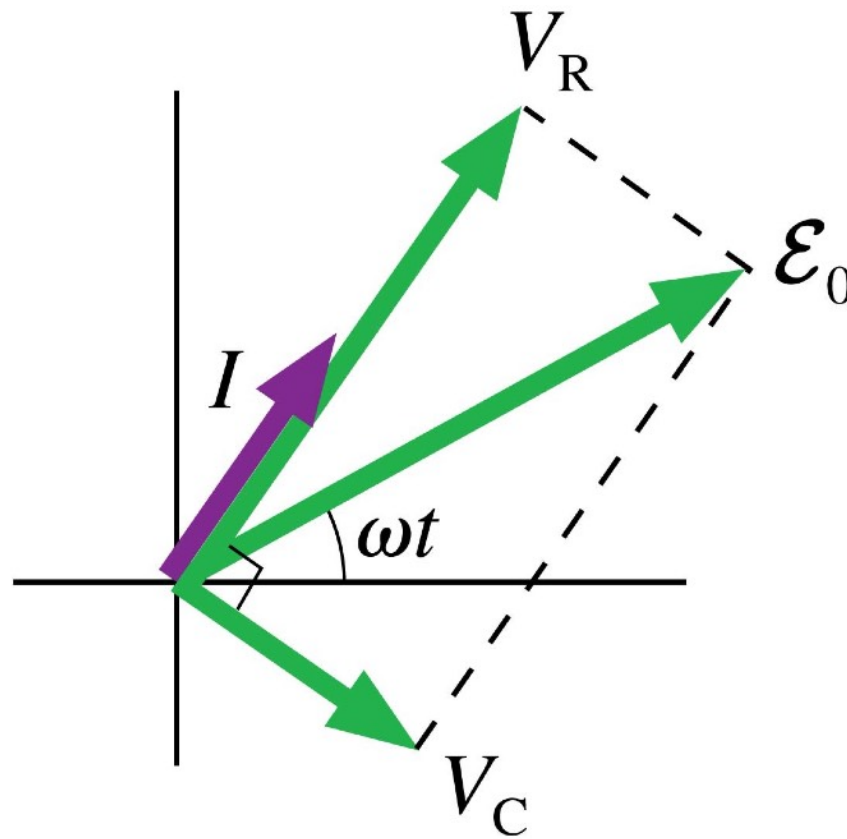


Draw the resistor voltage phasor and the capacitor voltage phasor


$$\mathcal{E}_0^2 = V_R^2 + V_C^2$$

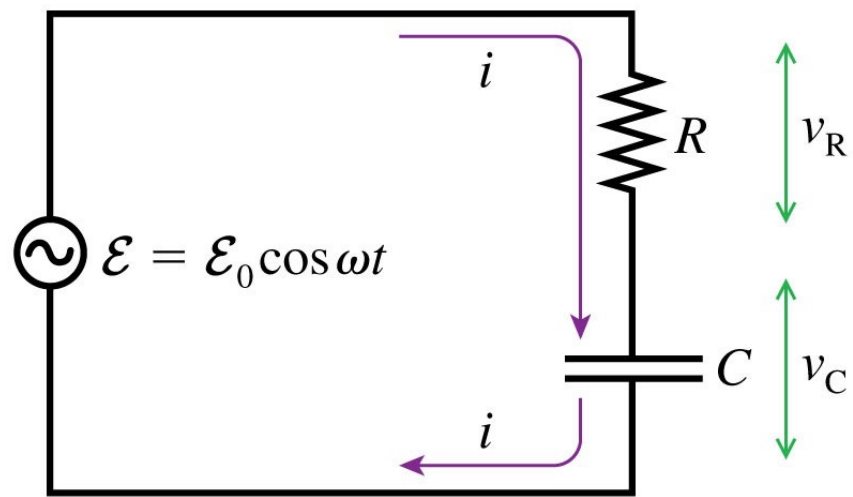

$$\mathcal{E}_0^2 = V_R^2 + V_C^2$$

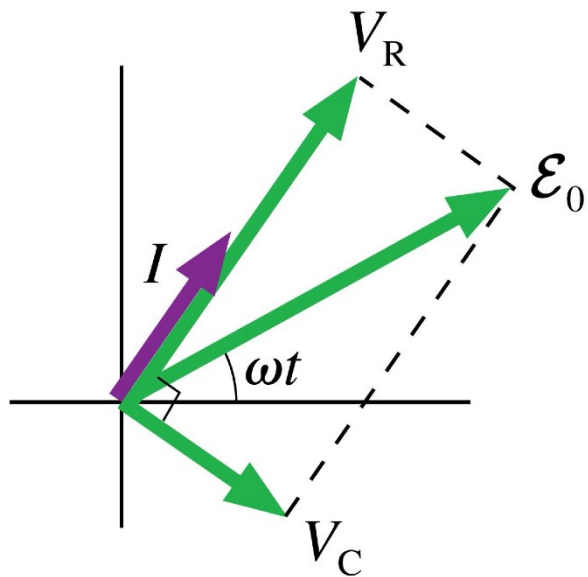-
- Fill in the details and solve for I
-




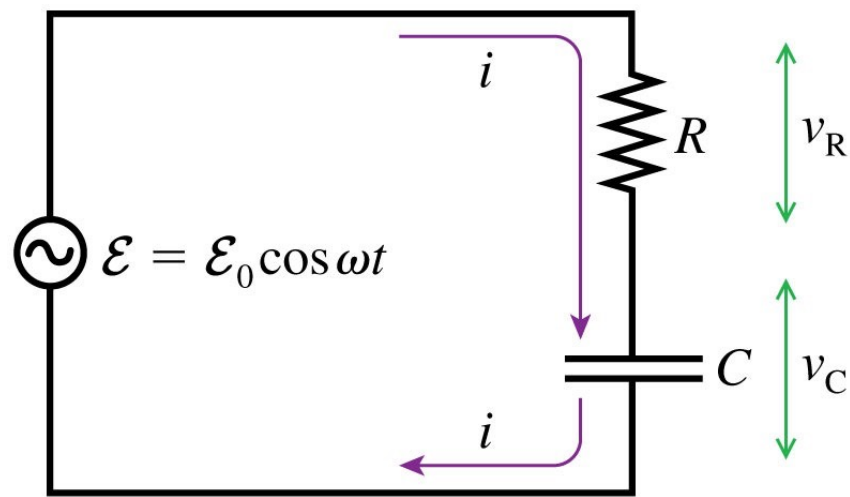


$$\mathcal{E}_0^2 = V_R^2 + V_C^2$$

-
- Fill in the details and solve for I
-
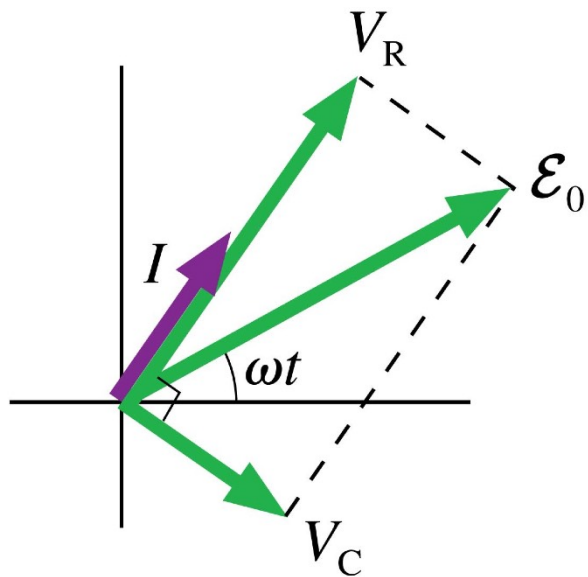
$$\begin{aligned} \mathcal{E}_0^2 &= V_R^2 + V_C^2 = (IR)^2 + (IX_C)^2 = (R^2 + X_C^2)I^2 \\ &= (R^2 + 1/\omega^2 C^2)I^2 \end{aligned}$$




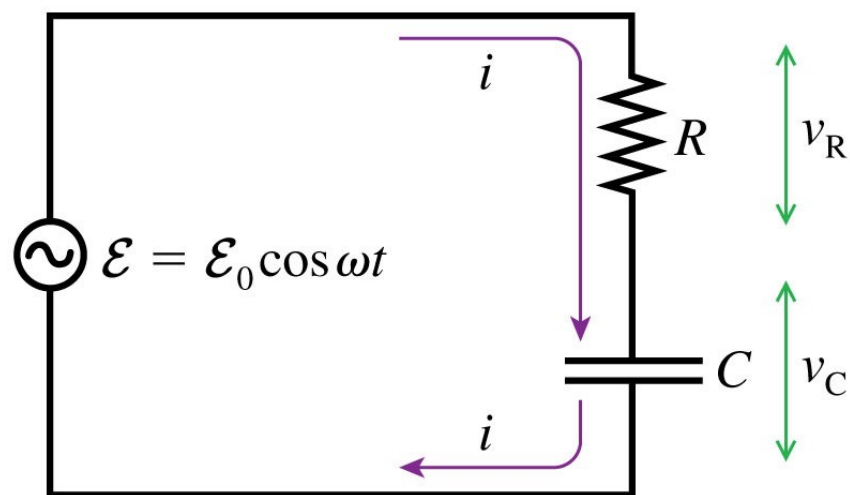

$$\mathcal{E}_0^2 = V_R^2 + V_C^2$$


-
- Fill in the details and solve for I
-
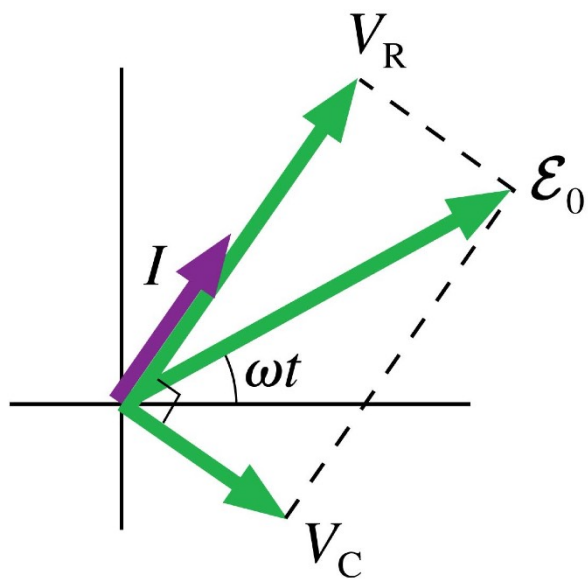
$$\begin{aligned} \mathcal{E}_0^2 &= V_R^2 + V_C^2 = (IR)^2 + (IX_C)^2 = (R^2 + X_C^2)I^2 \\ &= (R^2 + 1/\omega^2 C^2)I^2 \end{aligned}$$



$$V_R = IR = \frac{\mathcal{E}_0 R}{\sqrt{R^2 + X_C^2}} = \frac{\mathcal{E}_0 R}{\sqrt{R^2 + 1/\omega^2 C^2}}$$
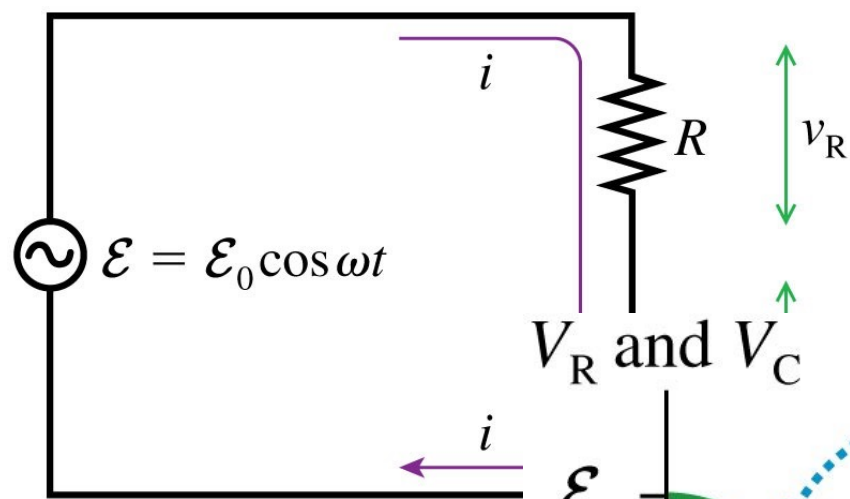
$$V_C = IX_C = \frac{\mathcal{E}_0 X_C}{\sqrt{R^2 + X_C^2}} = \frac{\mathcal{E}_0 / \omega C}{\sqrt{R^2 + 1/\omega^2 C^2}}$$



$$\mathcal{E}_0^2 = V_R^2 + V_C^2$$



•

• Fill in the details and solve for I

The capacitor voltage approaches \mathcal{E}_0 as ω approaches 0.


The resistor voltage approaches \mathcal{E}_0 as ω approaches ∞ .

$$\omega_c = \frac{1}{RC}$$

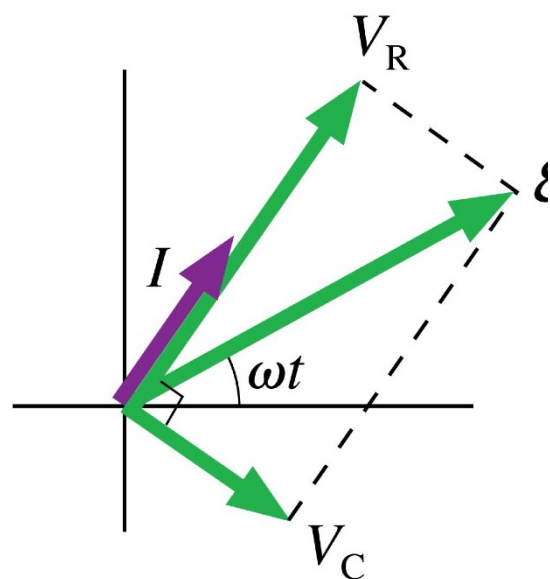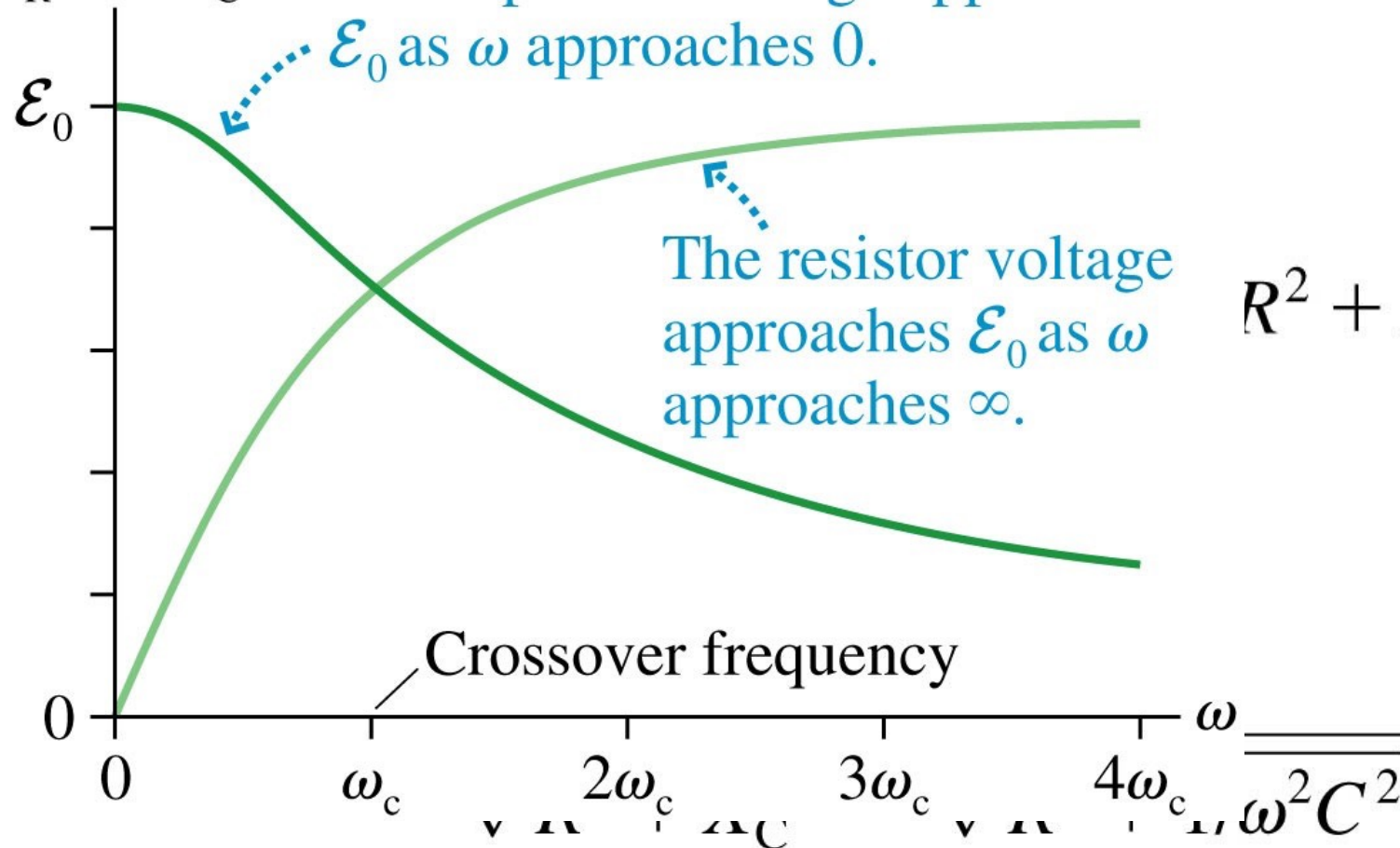

$$V_C = IX_C = \frac{\mathcal{E}_0 X_C}{\sqrt{R^2 + X_C^2}} = \frac{\mathcal{E}_0 / \omega C}{\sqrt{R^2 + 1/\omega^2 C^2}}$$

Filters

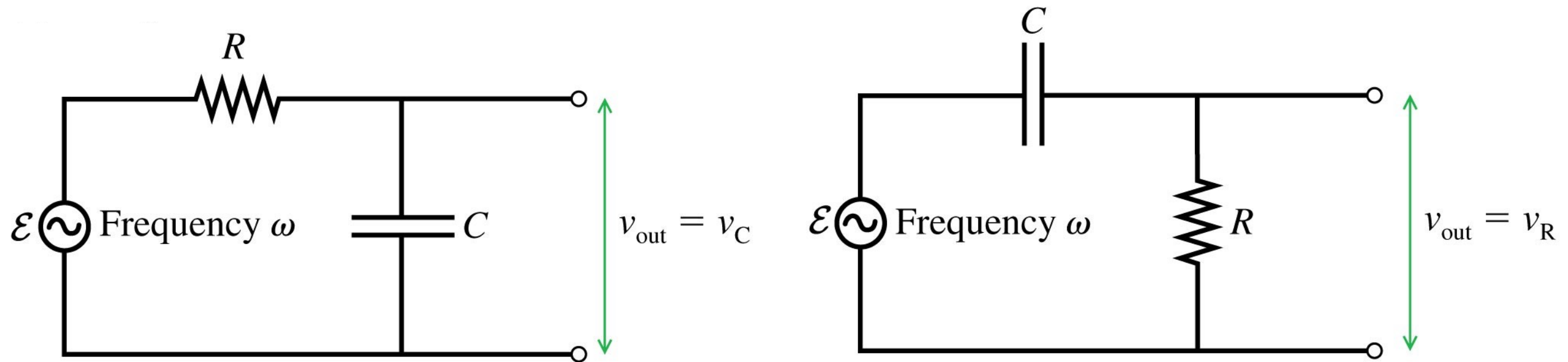

Which circuit will transmit high frequency signals through?