



PH 220


Lance Nelson

Demo Ideas:

- 1 - Blow a fuse: Connect a fuse to group of lightbulbs all wired in parallel. One by one, add lightbulbs (in parallel) until the fuse blows.
- 2- Temperature effects on the resistance of a wire. Wind a long wire around a glass rod (insulating) and connect it to a lightbulb. Turn on the power supply and observe that the light burns dimly. Then stick the rod in liquid nitrogen and observe the lightbulb burn brighter. (I found a metal rod with some copper wire wound around it that works ok. The resistance of the copper wire isn't very big so it's not a dramatic effect, but it works.)


Deeper Thinking

Electron current

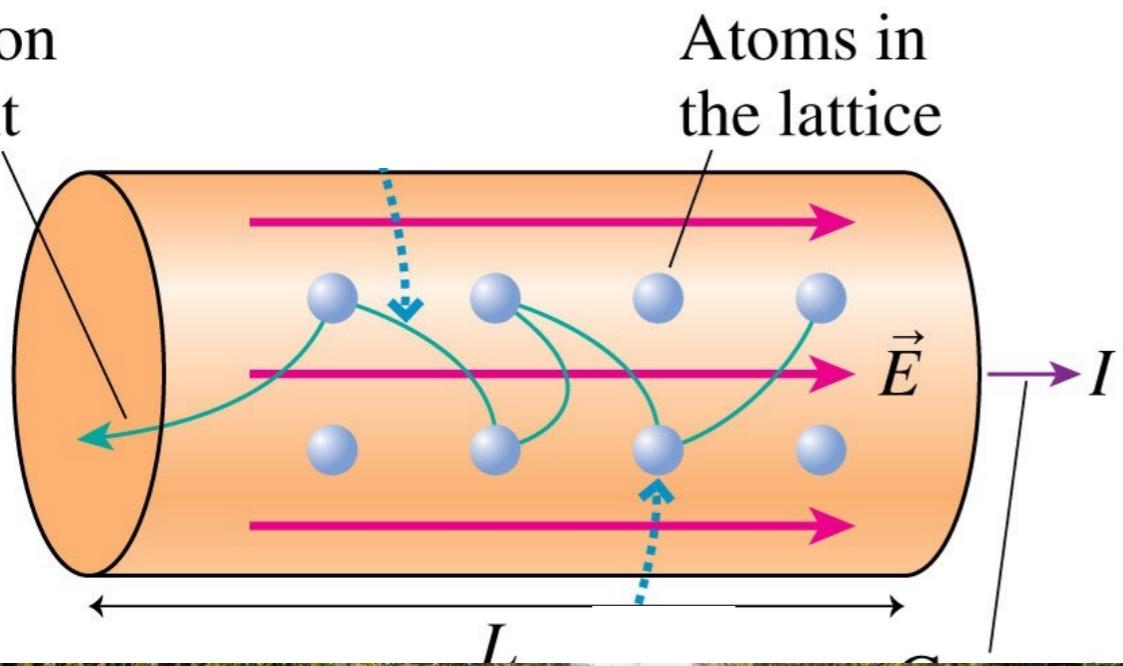


$$P_{\text{res}} = I \Delta V = I^2 R = \frac{\Delta V^2}{R}$$

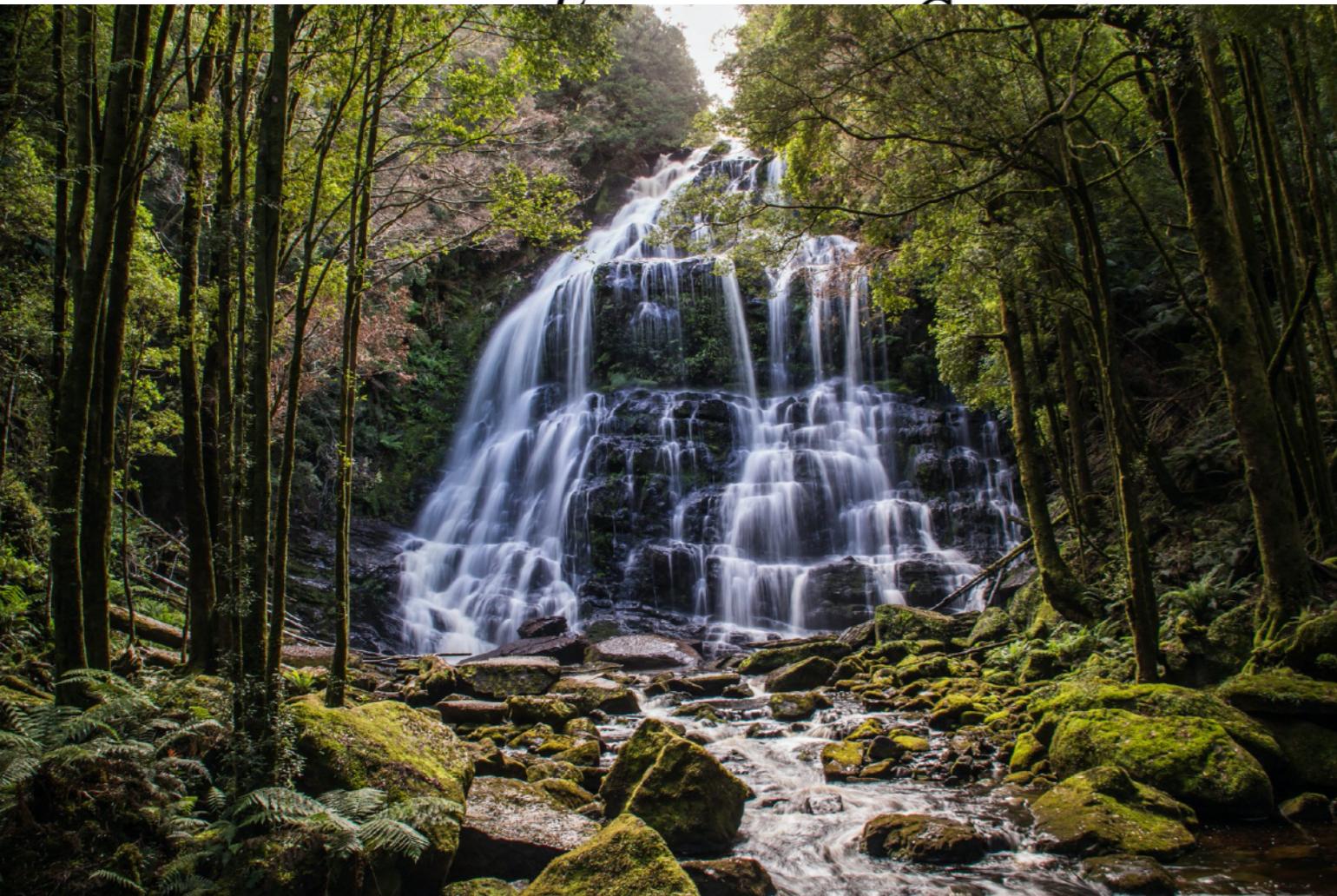Explain how an increase/decrease of the variable will affect the power dissipated. (Don't just follow the math, explain it conceptually too)




Deeper Thinking

Electron current

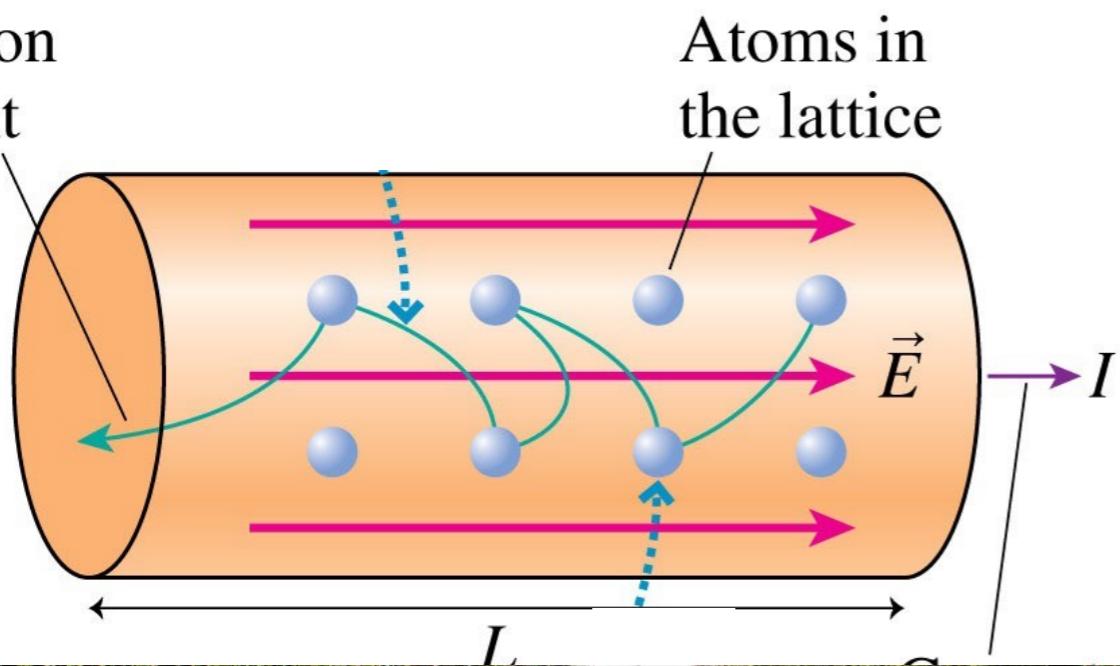


$$P_{\text{res}} = \boxed{1} I \Delta V = I^2 R = \frac{\boxed{2} \Delta V^2}{R}$$

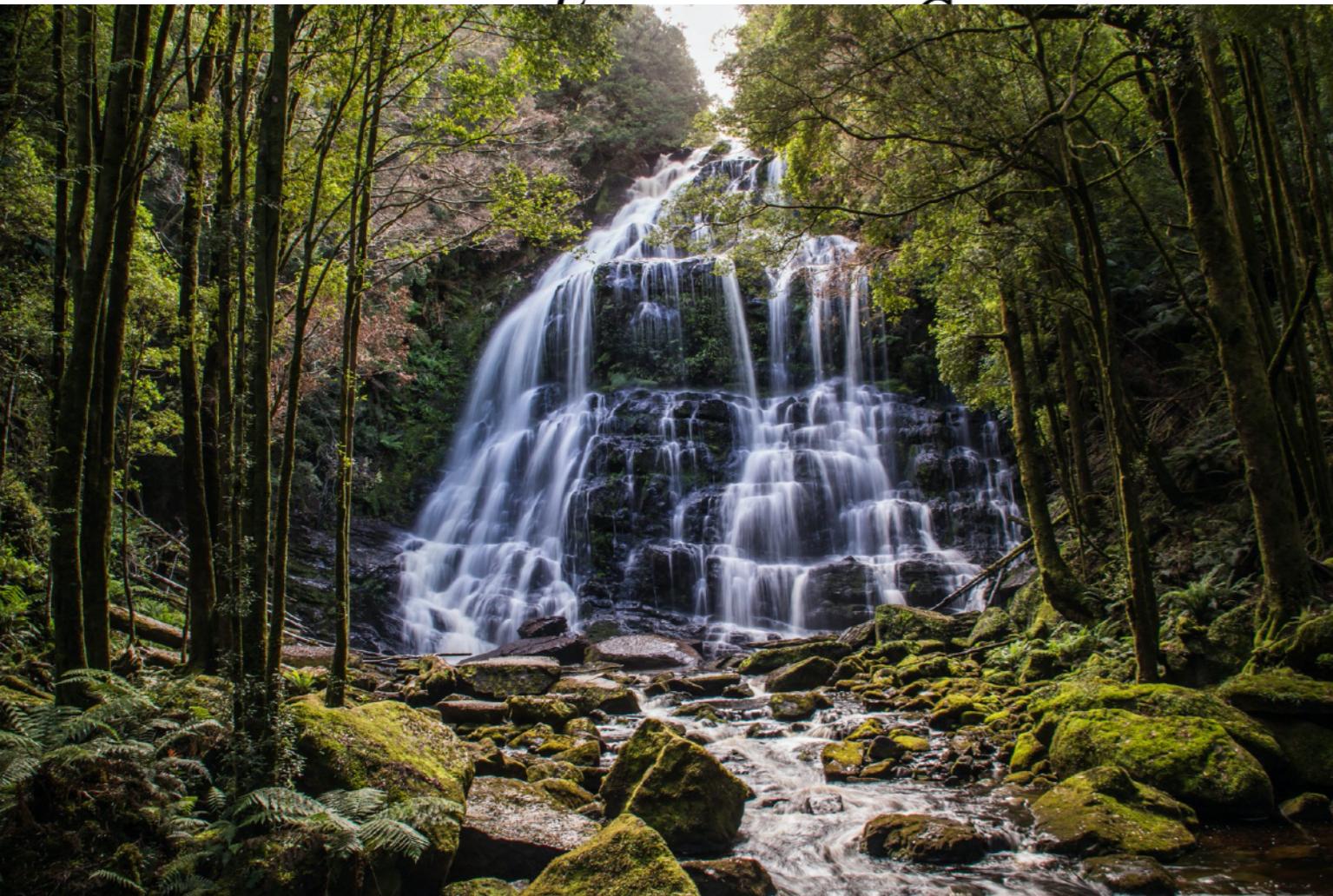Explain how an increase/decrease of the variable will affect the power dissipated. (Don't just follow the math, explain it conceptually too)



Series Resistors

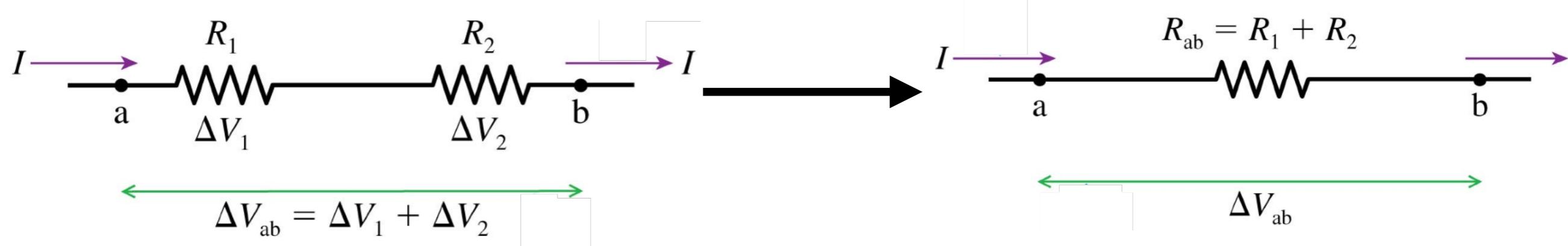
Write the potential difference between a and b in terms of current and resistance.



Series Resistors

$$\Delta V_{ab} = \Delta V_1 + \Delta V_2 = IR_1 + IR_2 = I(R_1 + R_2)$$

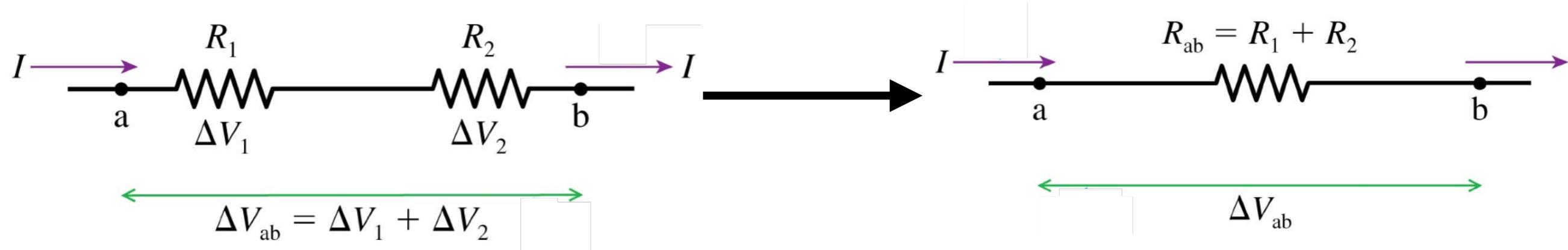Write the potential difference between a and b in terms of current and resistance.




Series Resistors

$$\Delta V_{ab} = \Delta V_1 + \Delta V_2 = IR_1 + IR_2 = I(R_1 + R_2)$$



$$R_{ab} = \frac{\Delta V_{ab}}{I} = \frac{I(R_1 + R_2)}{I} = R_1 + R_2$$

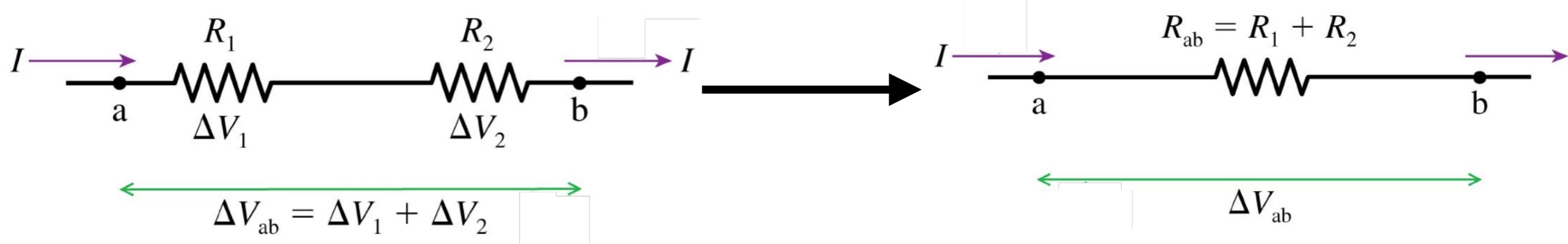Write the potential difference between a and b in terms of current and resistance.



Resistors in Parallel

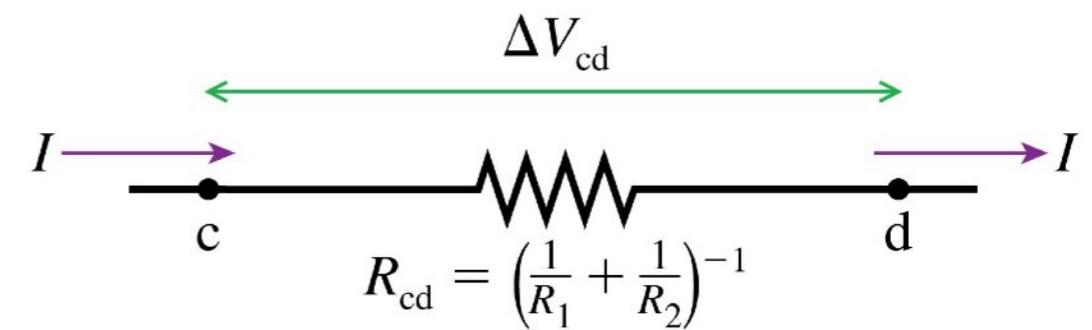
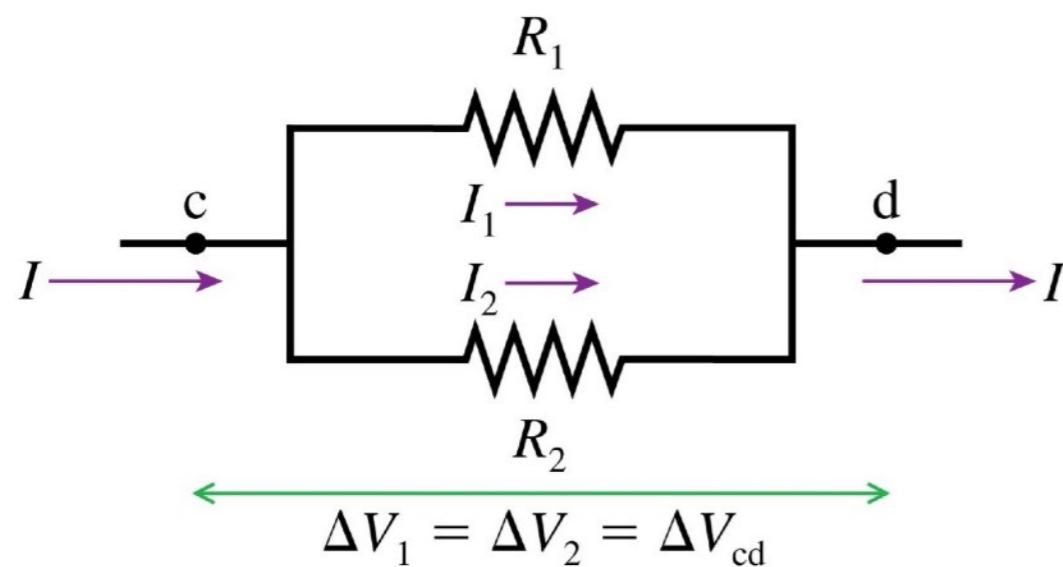
Write the current flowing through point c in terms of resistor voltages and resistances.



Resistors in Parallel

Write the current flowing through point c in terms of resistor voltages and resistances.
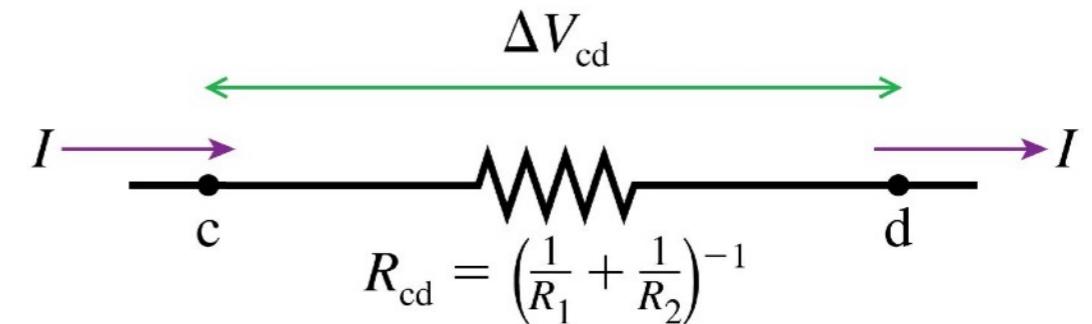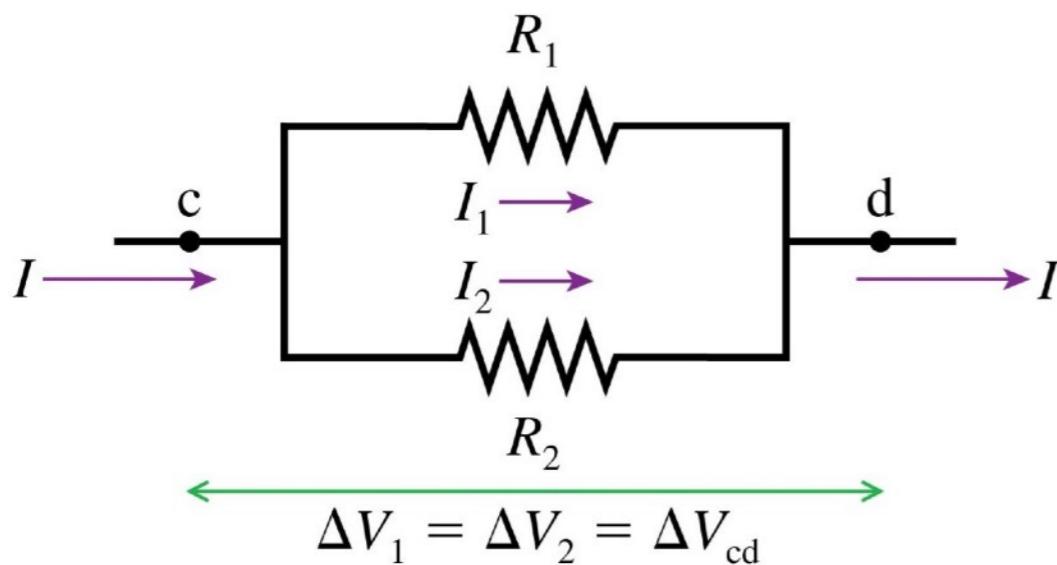
$$I = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2} = \frac{\Delta V_{cd}}{R_1} + \frac{\Delta V_{cd}}{R_2} = \Delta V_{cd} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$





Resistors in Parallel

Write the current flowing through point c in terms of resistor voltages and resistances.

$$I = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2} = \frac{\Delta V_{cd}}{R_1} + \frac{\Delta V_{cd}}{R_2} = \Delta V_{cd} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$
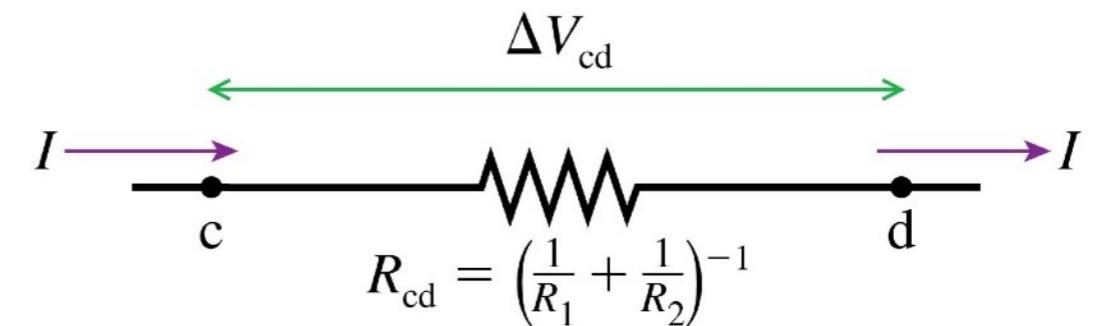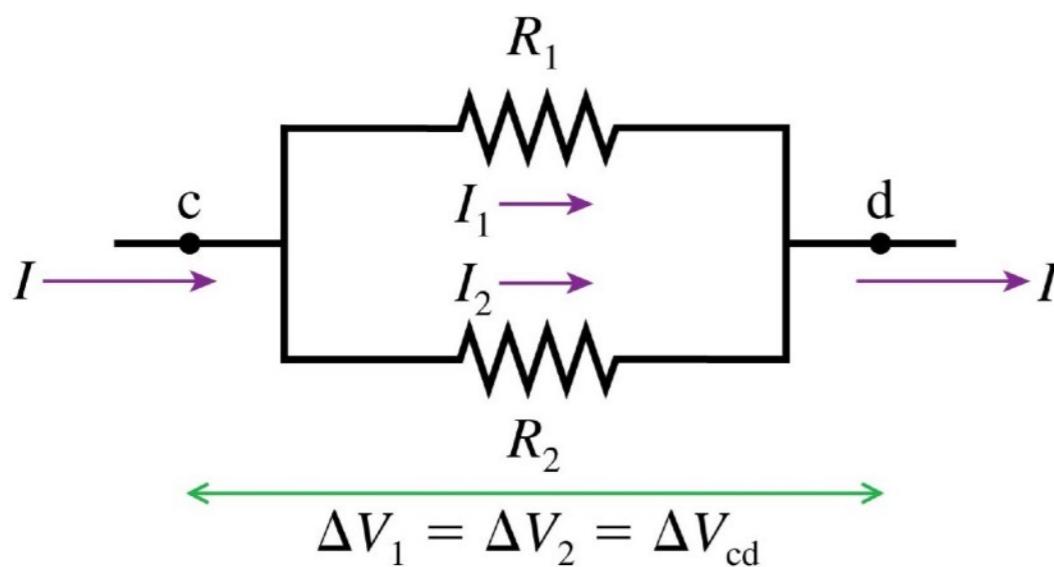
$$R_{cd} = \frac{\Delta V_{cd}}{I} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$



Circuit analysis tools

Describe the tool and the
math needed to use the
rule!

Power delivered to a resistor

Kirchoff's loop rules

Kirchoff's junction rules

Resistors in series

Resistors in parallel

Power delivered by a source


$$P_{\text{res}} = I\Delta V = I^2 R = \frac{\Delta V^2}{R}$$



Question #8

Which resistor dissipates more power?

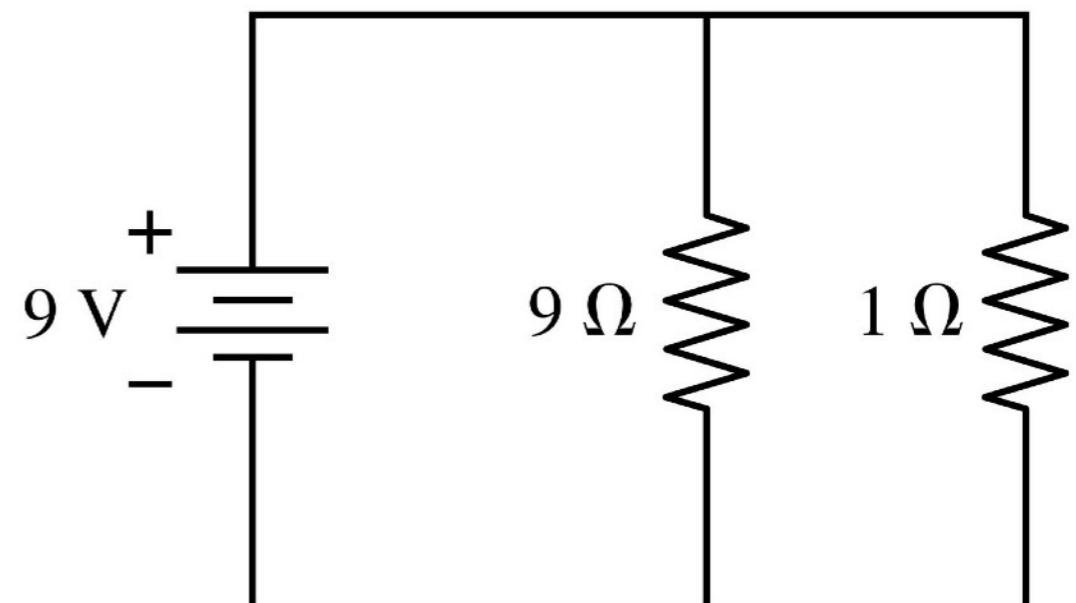- A. The $9\ \Omega$ resistor.
- C. The $1\ \Omega$ resistor.
- D. They dissipate the same power.




Question #8

$$P = \frac{(\Delta V)^2}{R}$$

Which resistor dissipates more power?

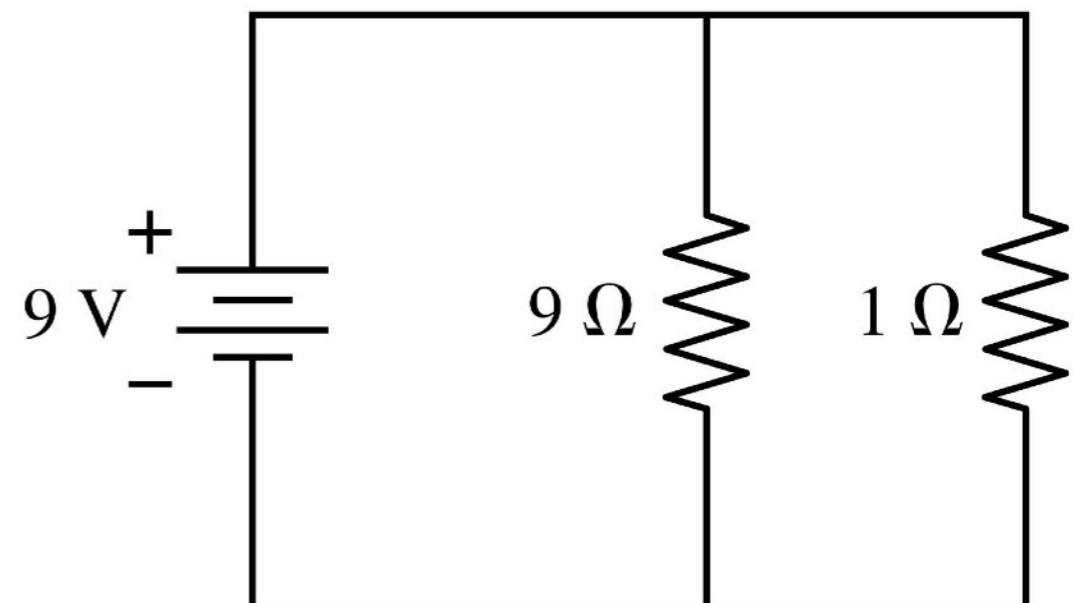
- A. The $9\ \Omega$ resistor.
- C. The $1\ \Omega$ resistor.
- D. They dissipate the same power.




Question #9

Which bulb is brighter?

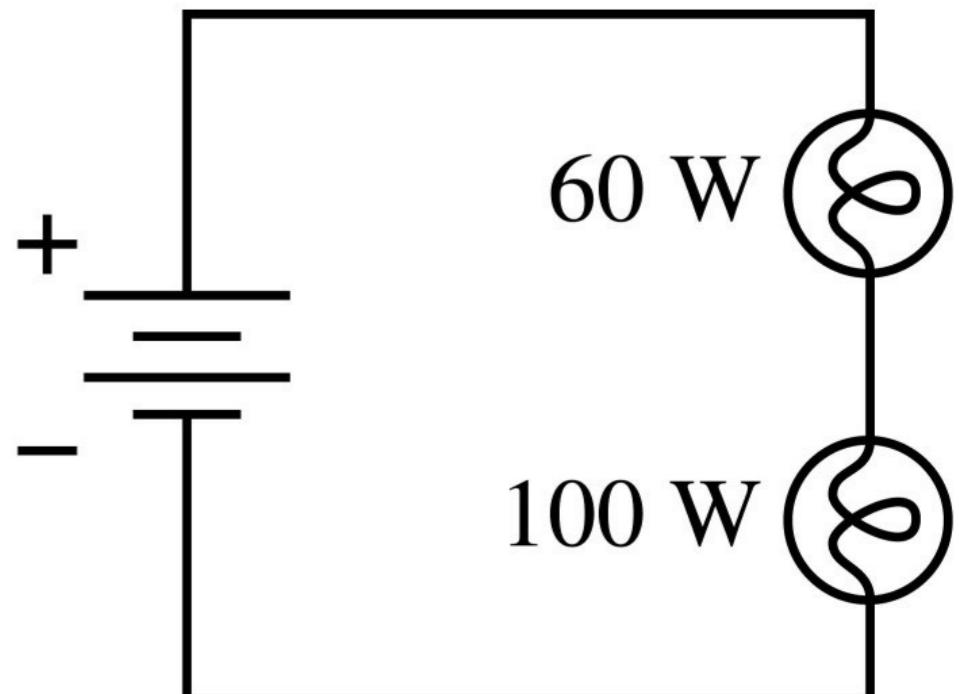- A. The 100 W bulb.
- B. The 60 W bulb.
- C. Their brightnesses are the same.
- D. There's not enough information to tell.




Lightbulb puzzle

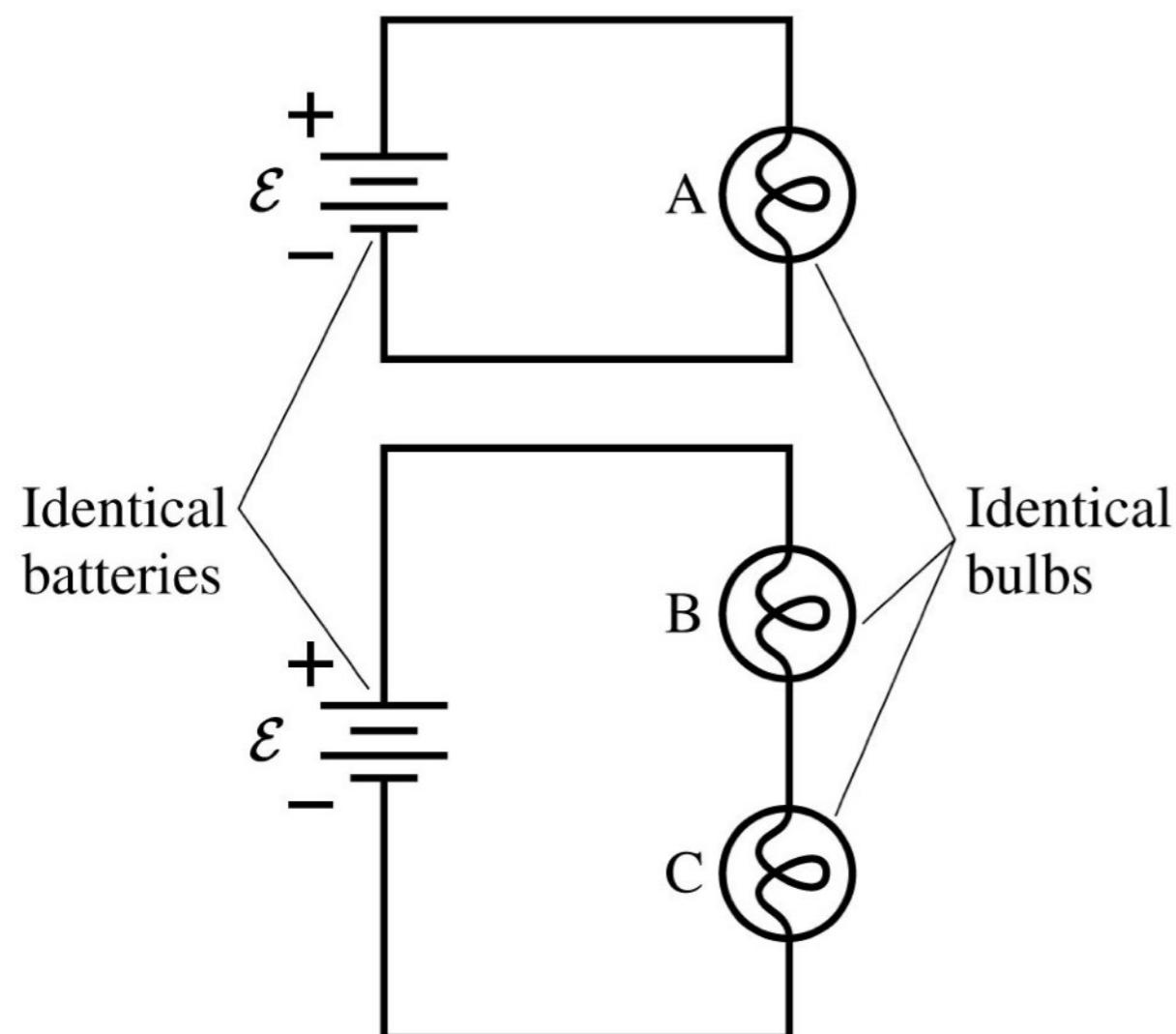


Rank the brightness of the bulbs
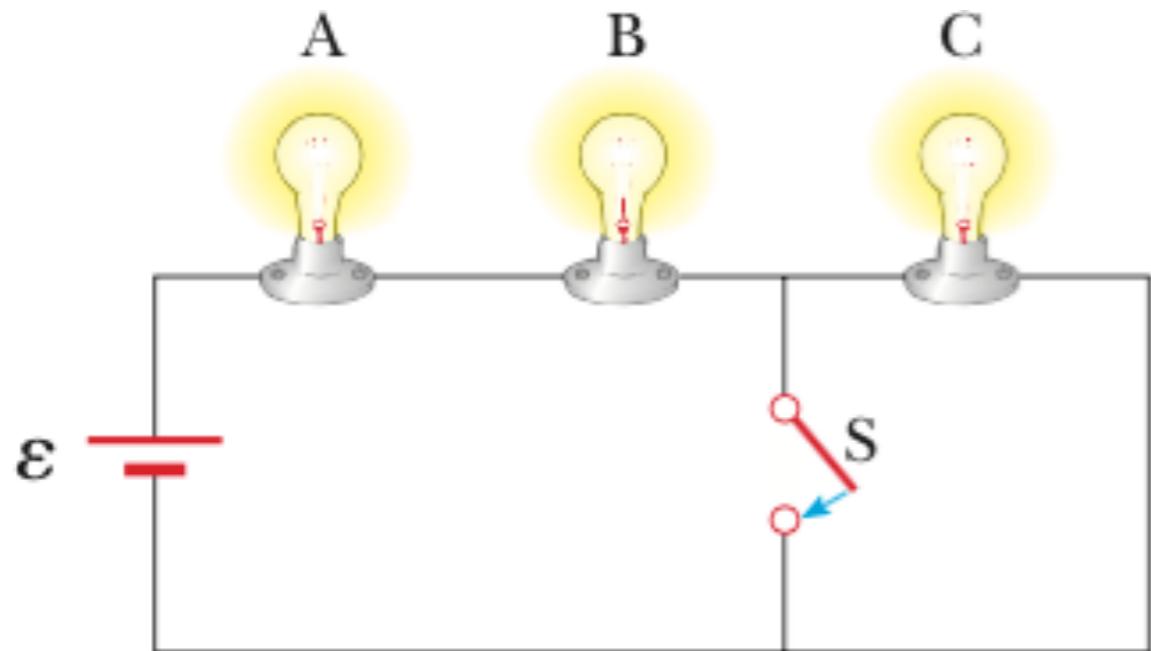
$$P_{\text{res}} = I \Delta V = I^2 R = \frac{\Delta V^2}{R}$$



What will happen to the brightness of the bulbs when the switch is closed

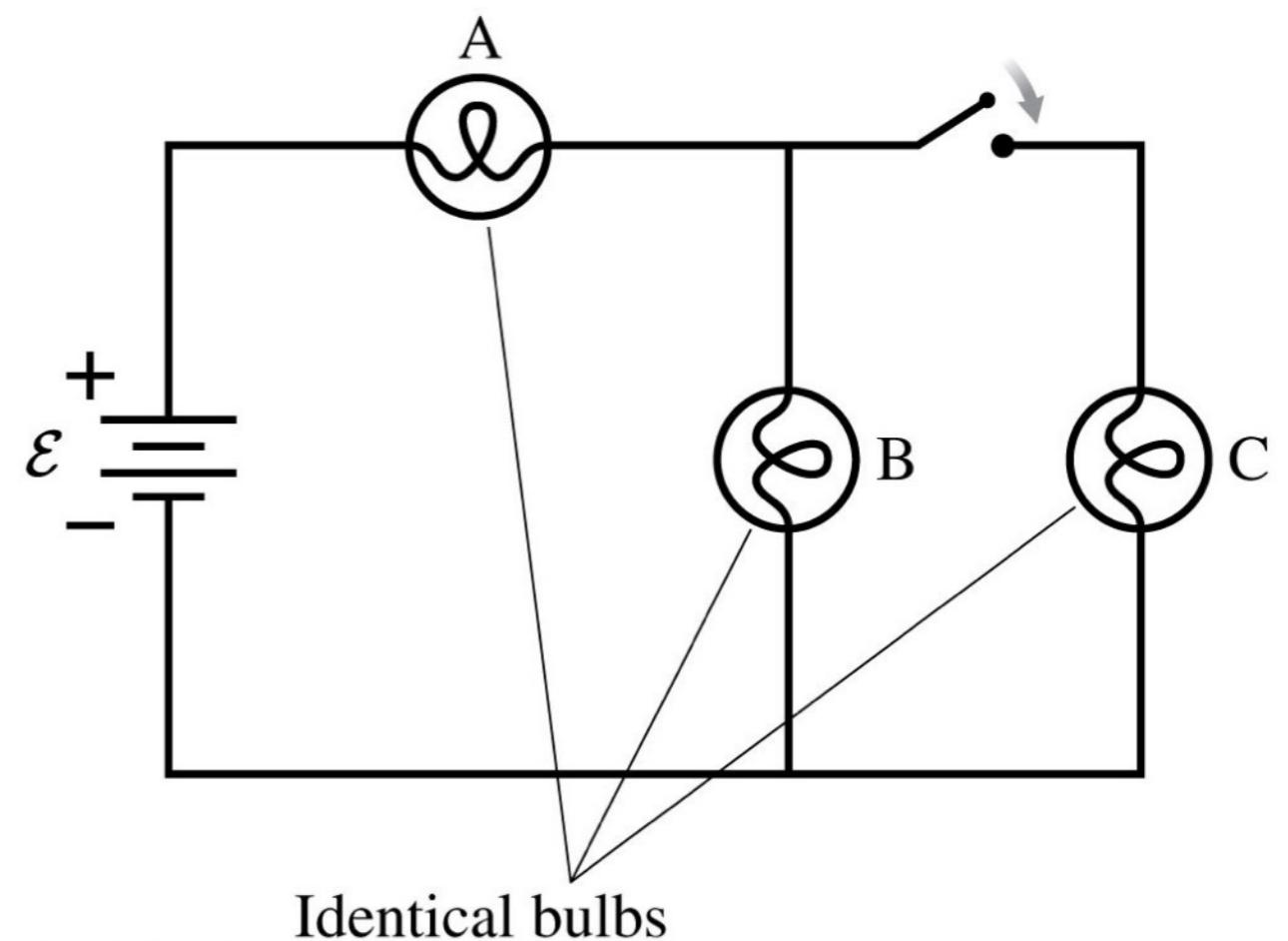
What happens to the brightness of the bulbs when the switch closes?




Question #10

The battery current I is

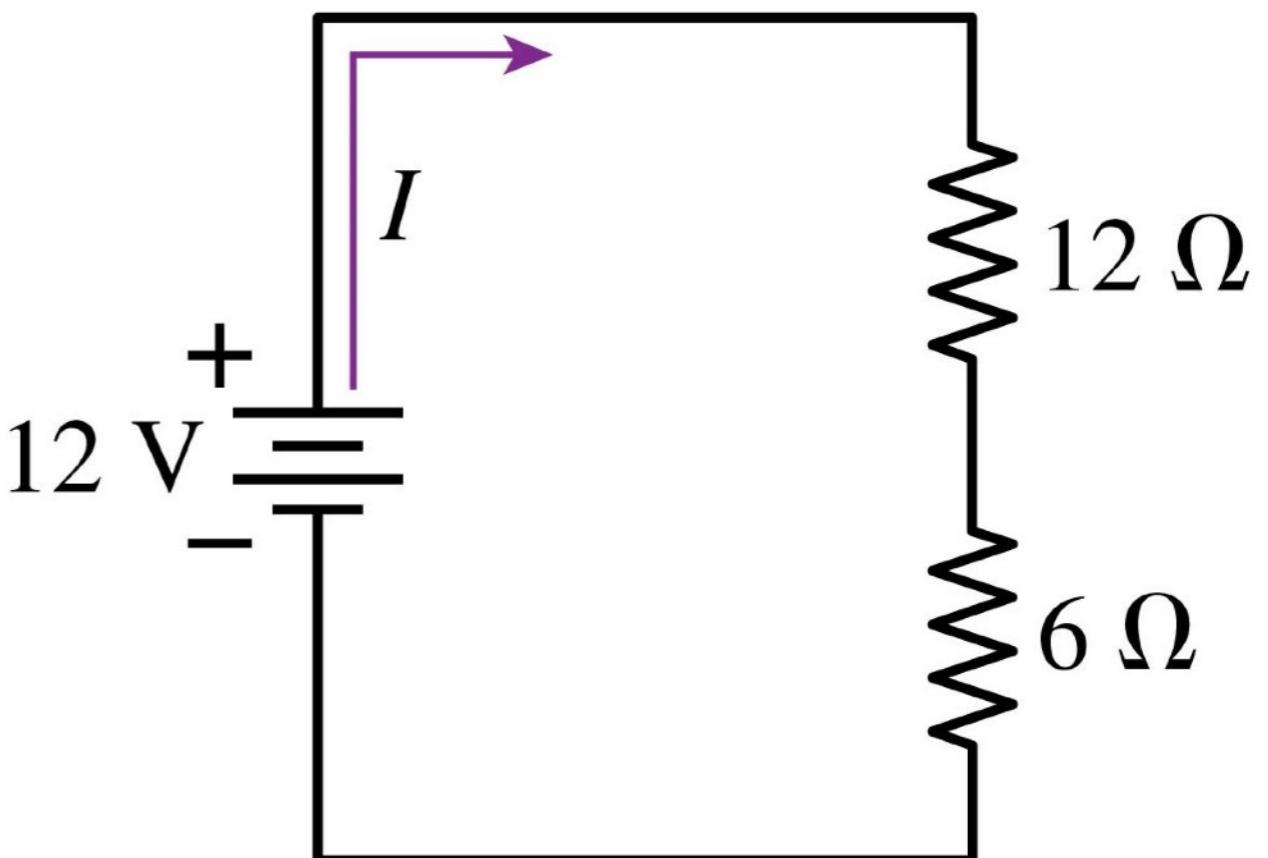- A. 3 A.
- B. 2/3 A.
- C. 1 A.
- D. 2 A.
- E. 1/2 A.



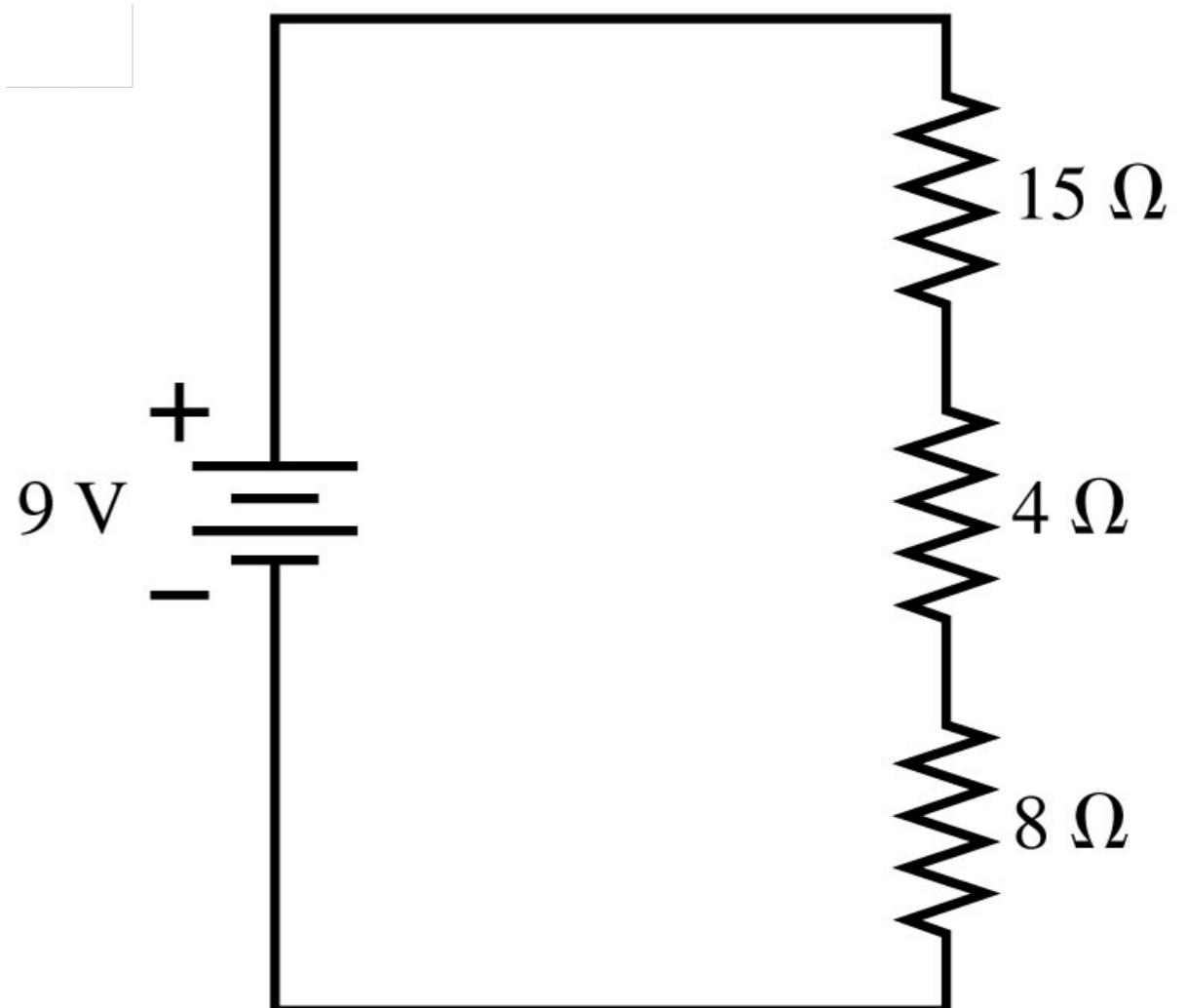
What will be the potential drop across each resistor?




Question #11

The battery current I is

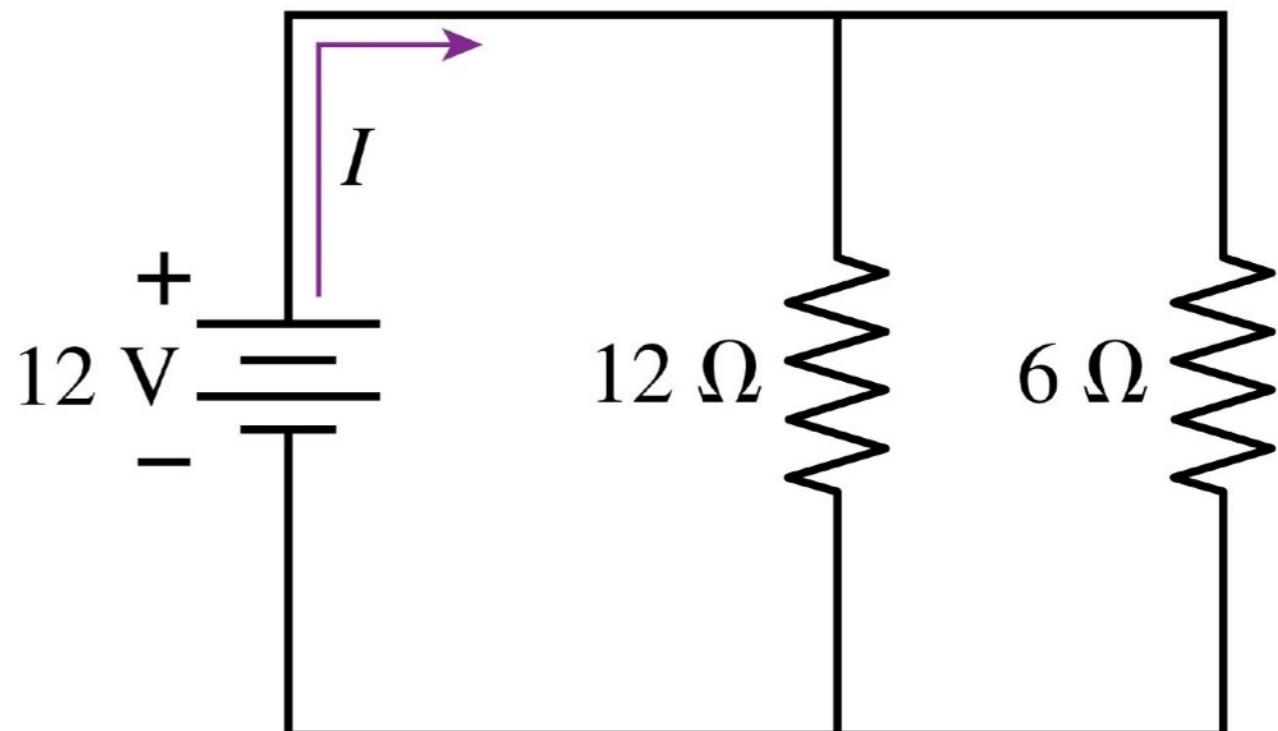- A. 3 A.
- B. 2 A.
- C. 1 A.
- D. $2/3$ A.
- E. $1/2$ A.




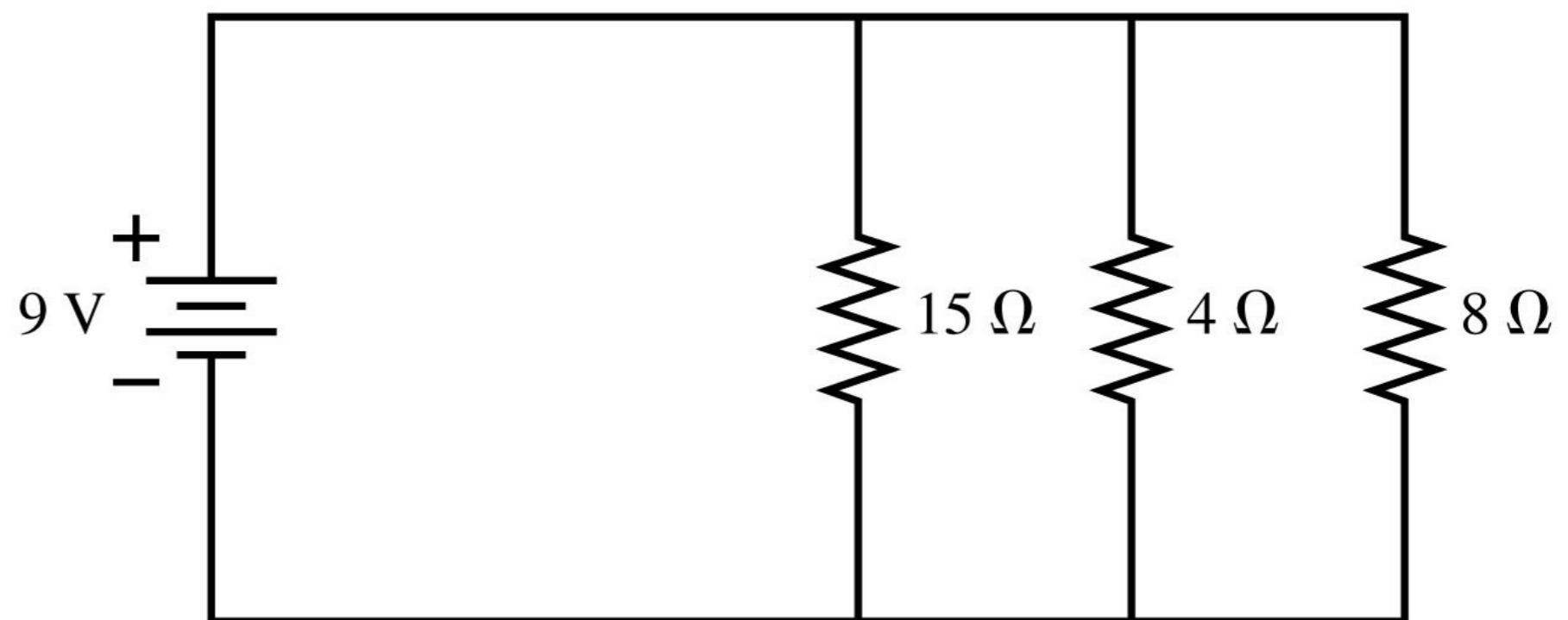Find the current and voltage for each resistor.




Question #12

Rank the currents in the circuit

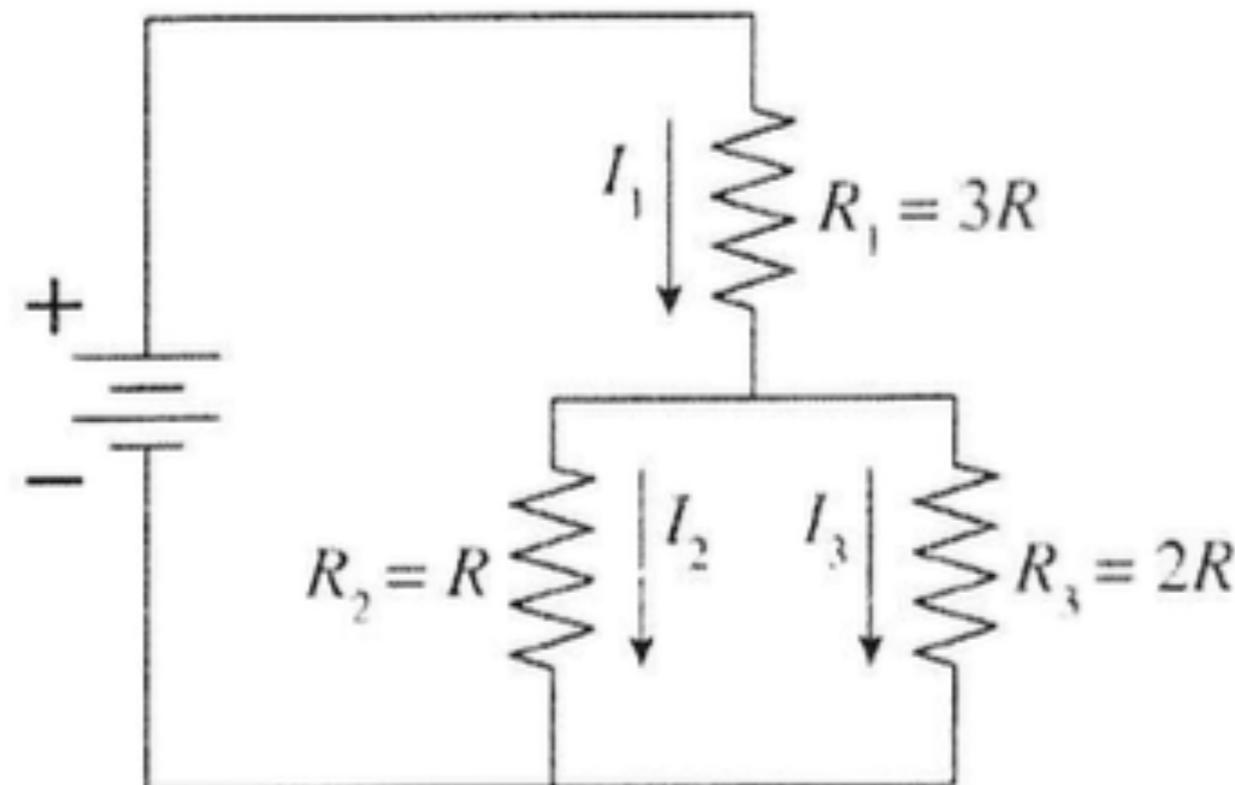


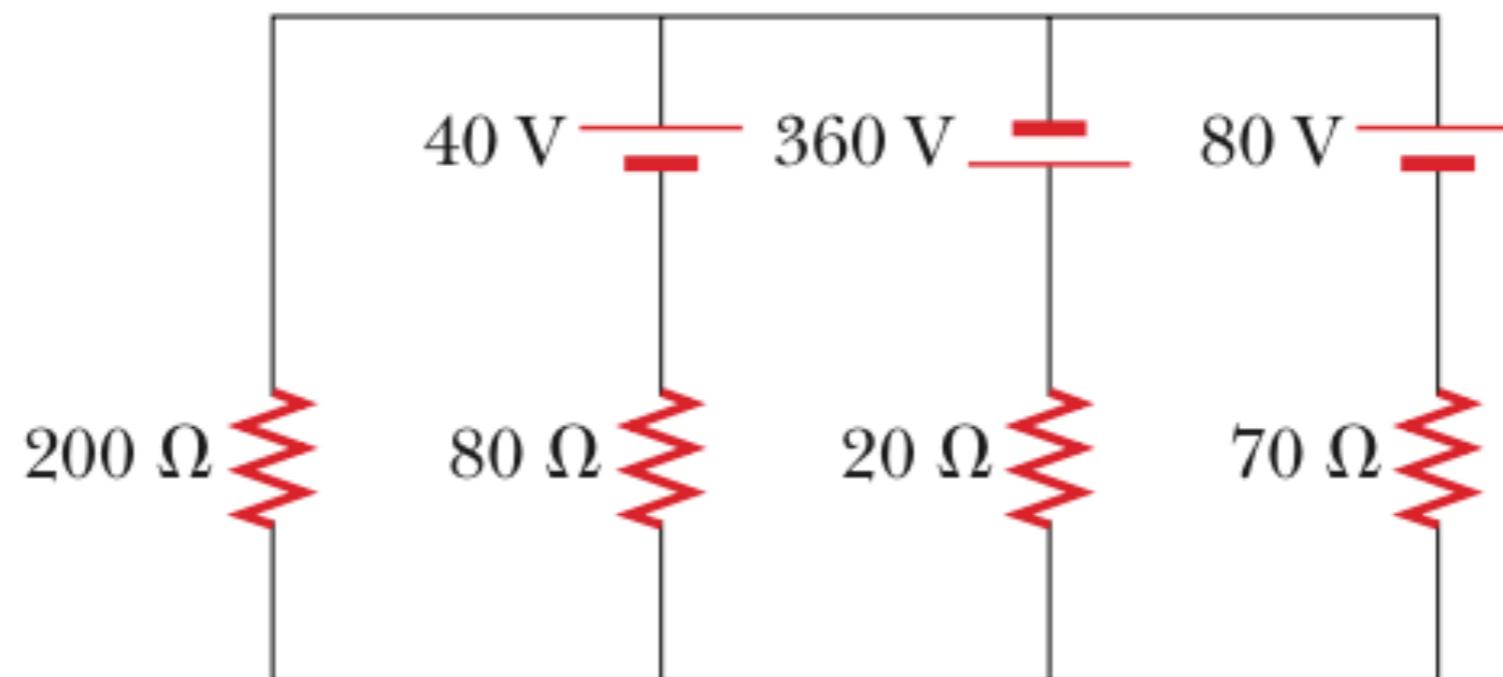- a) $I_1 = I_2 = I_3$
- b) $I_1 > I_2 = I_3$
- c) $I_1 < I_2 = I_3$
- d) $I_1 > I_2 > I_3$

Find the current through each resistor and the voltage across the 200 Ohm resistor.




Rank the brightness of the bulbs

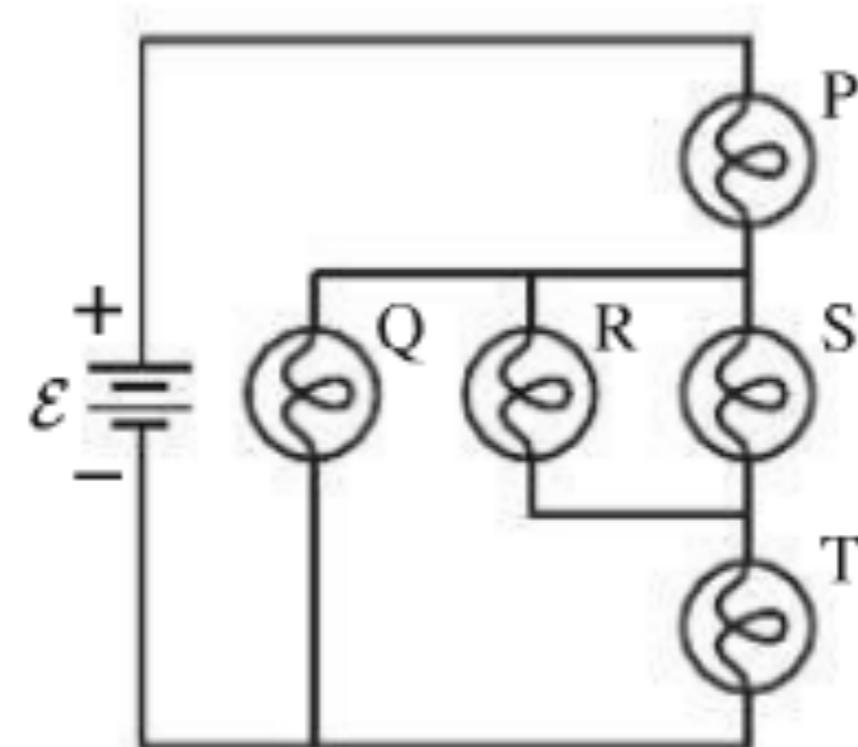


Real Batteries

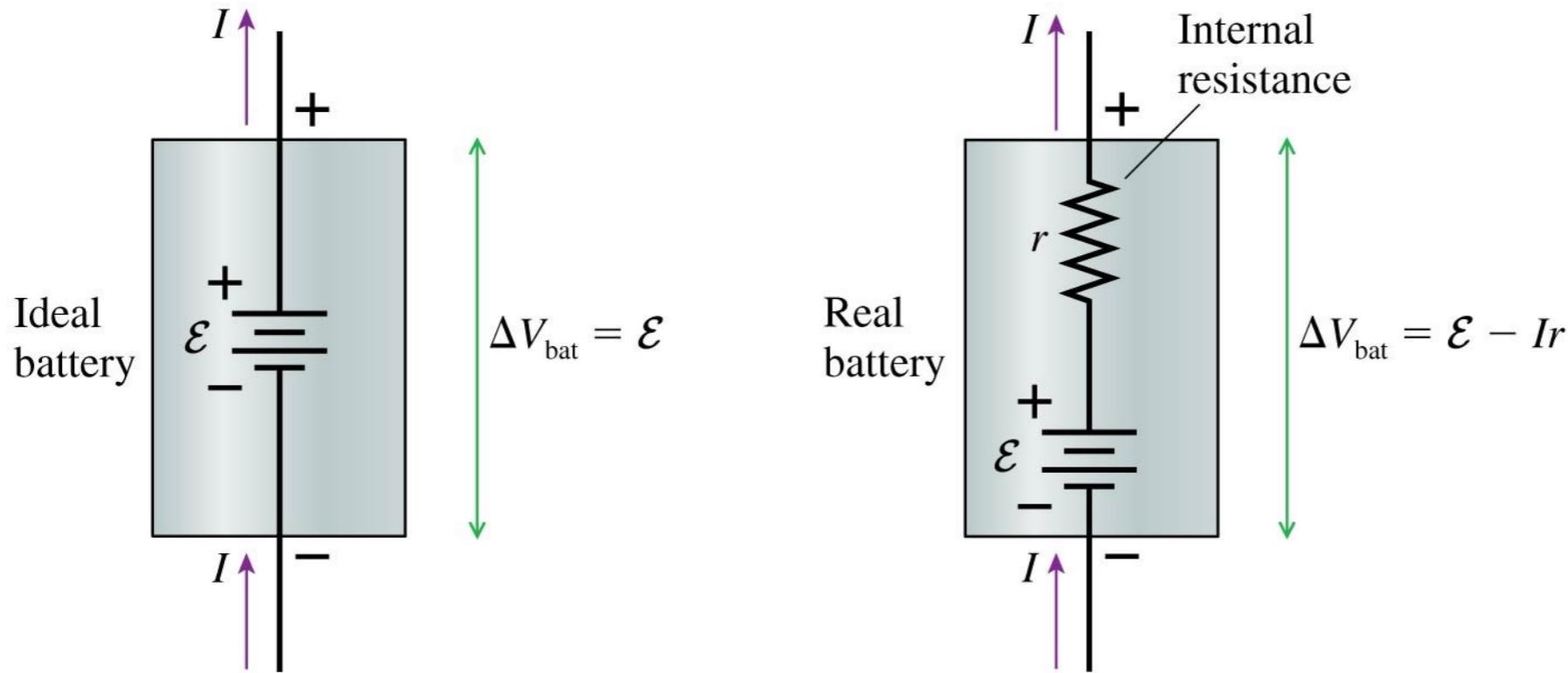The batterie's internal resistance limits the max current.



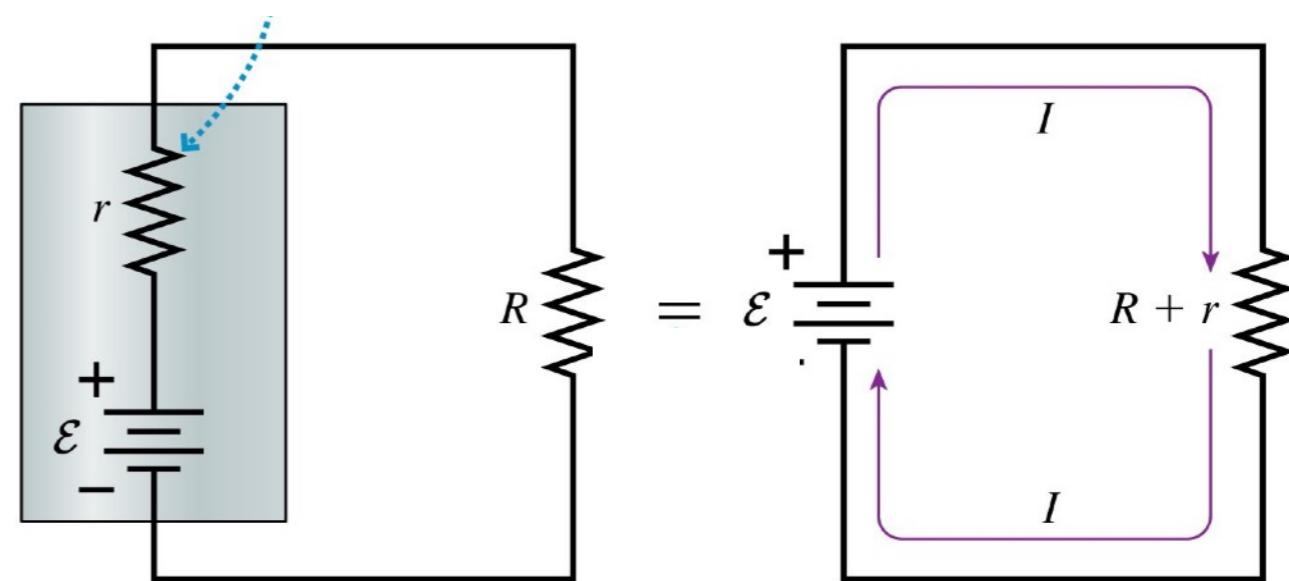
$$\Delta V_R = IR = \frac{\mathcal{E}}{R+r} R$$



Question #13

What does the voltmeter read?

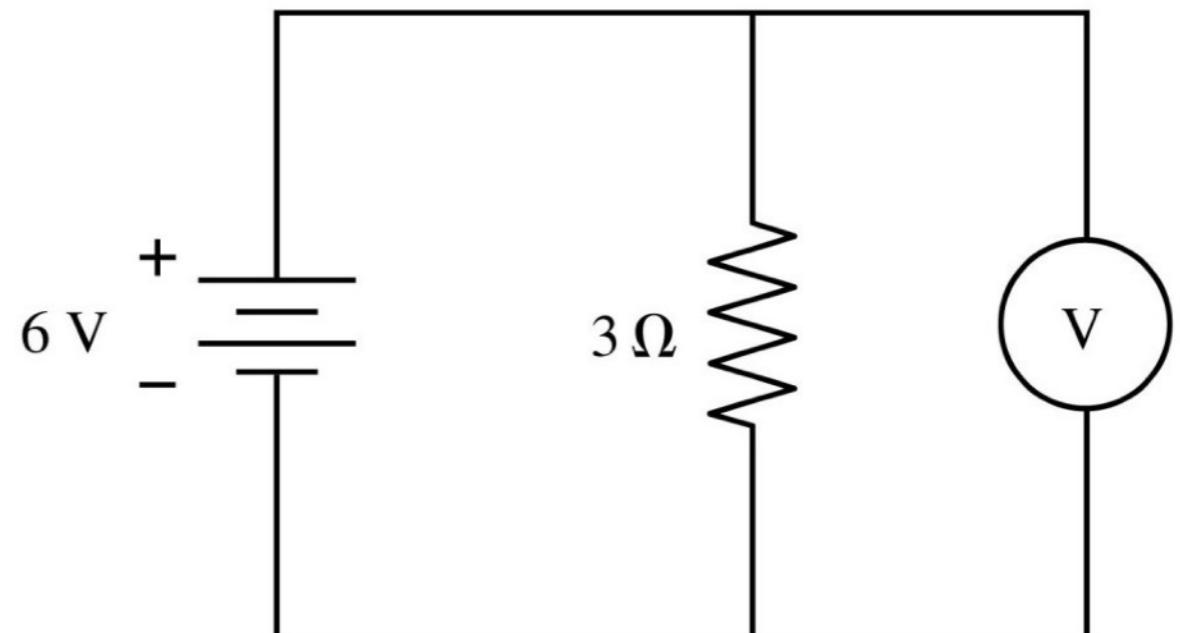
- A. 3 V.
- B. 6 V.
- C. 2 V.
- D. Some other value.
- E. Nothing because this will fry the meter.







Question #14

What does the ammeter read?

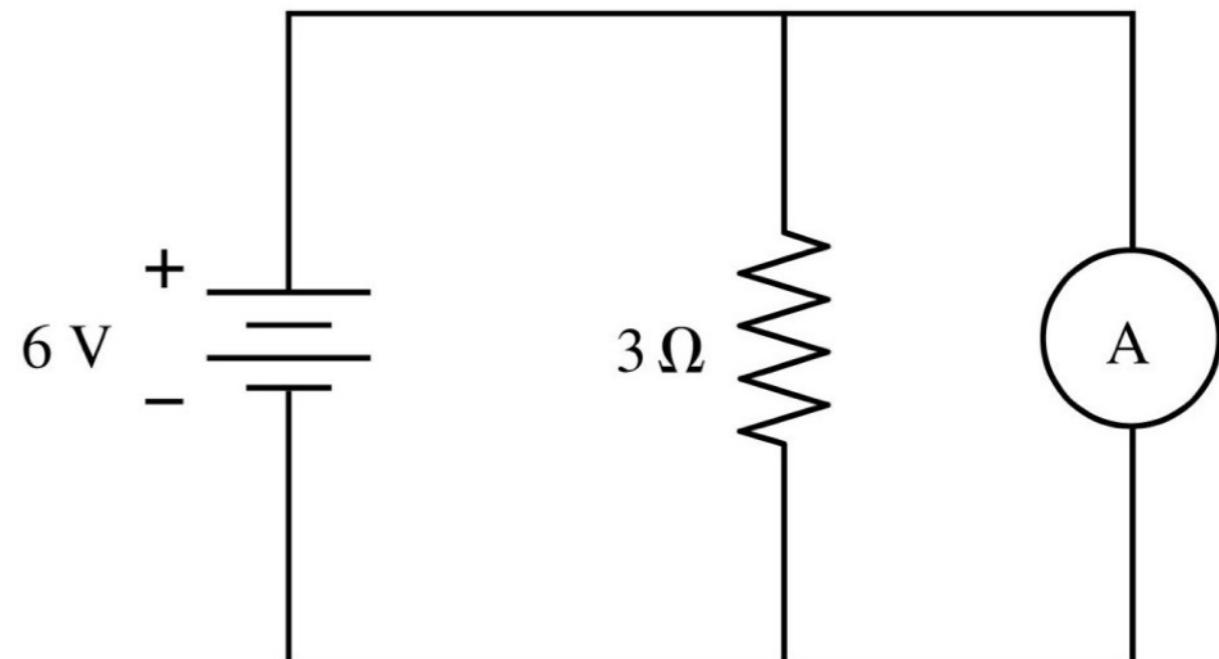- A. 6 A.
- B. Nothing because this will fry the meter.
- C. 2 A.
- D. Some other value.
- E. 3 A.




Ammeters and Voltmeters

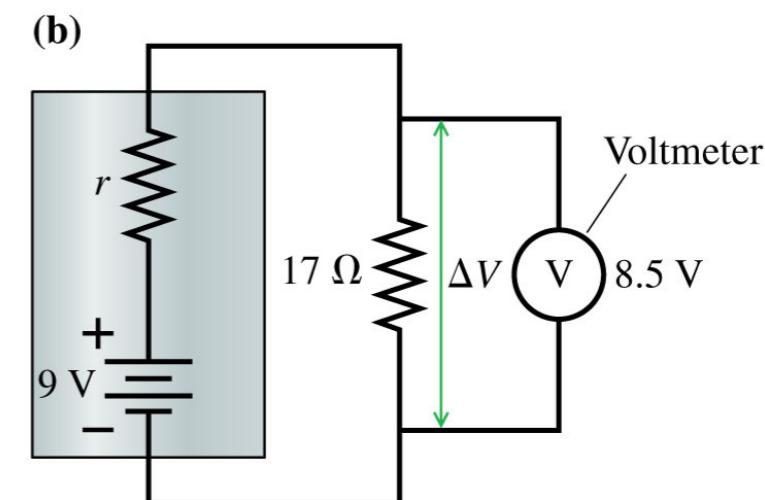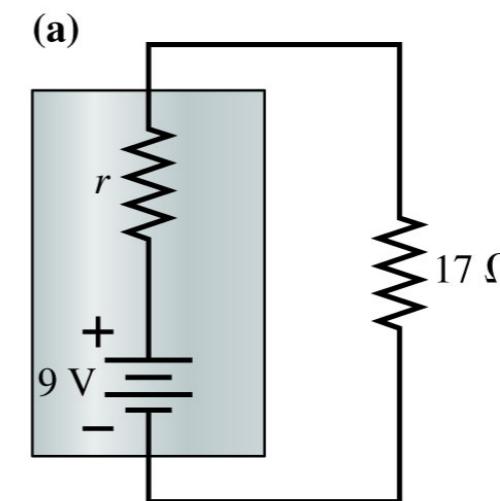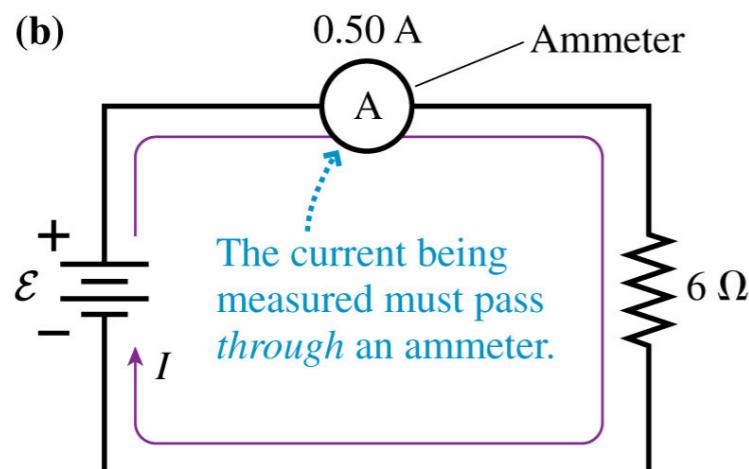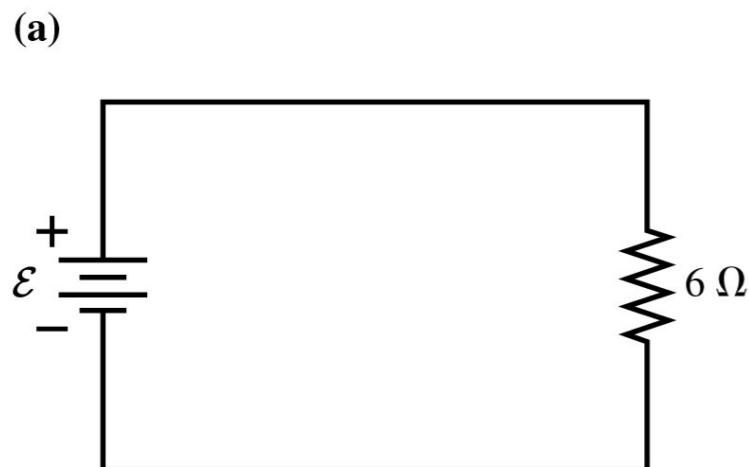


Getting Grounded

"Ouch!"

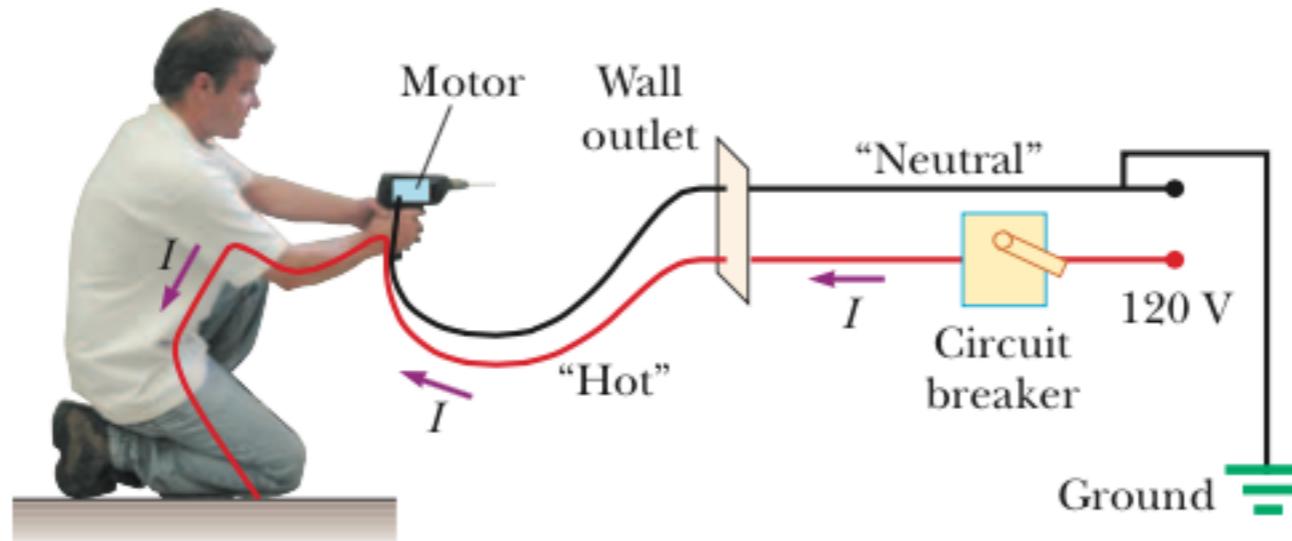

(a)

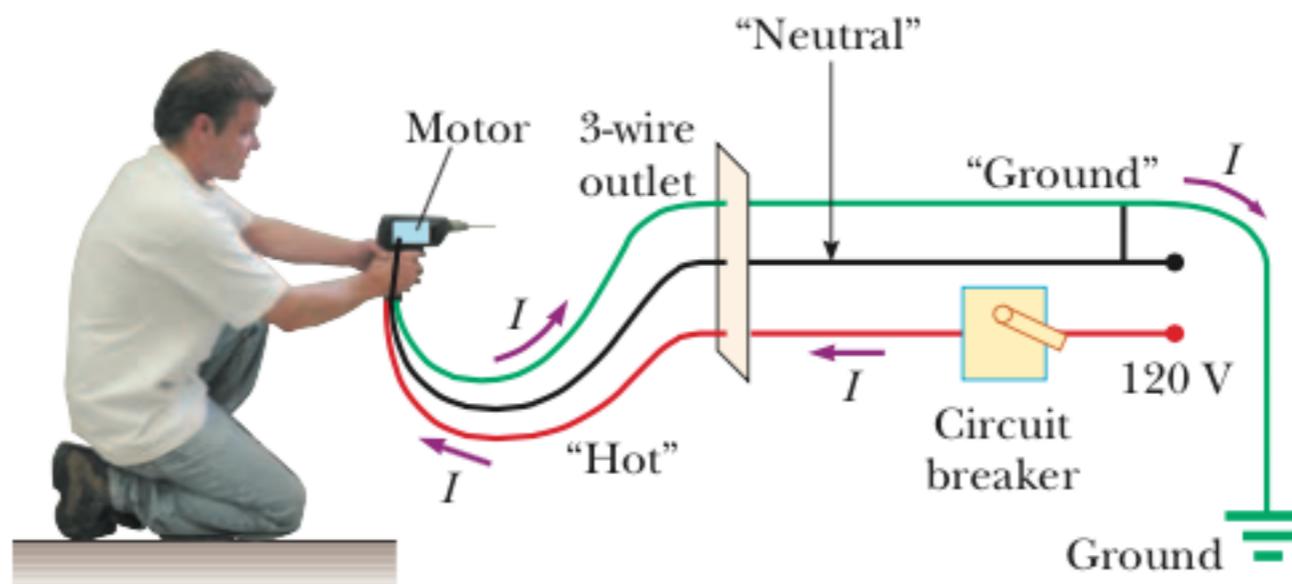

Grounding a circuit

